

Active Filters

ELEN-457

Jose Silva-Martinez and Edgar Sanchez-Sinencio

Spring 2003

Filters

- **Introduction**
- **Low-Gain Filters**
- **Infinite Gain Filters**
- **State Variable Filters**
- **Ladder Filters**
- **Other techniques (Follow the leader, GICs)**




Introduction: First-order Filter

$$H(s) = \frac{K1}{s + \omega_0}$$


$$H(j\omega) = \frac{K1}{(\omega_0) + j(\omega)}$$

$$|H(j\omega)| = \frac{K1}{\sqrt{(\omega_0)^2 + (\omega)^2}}$$

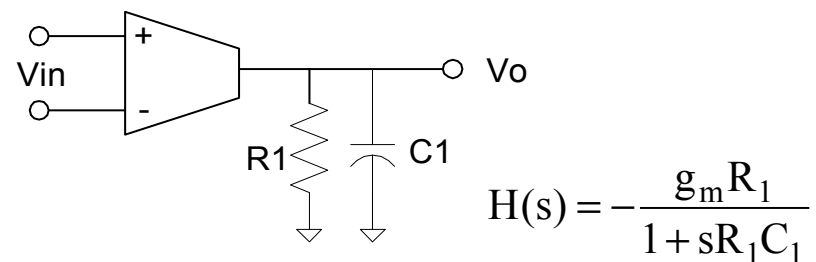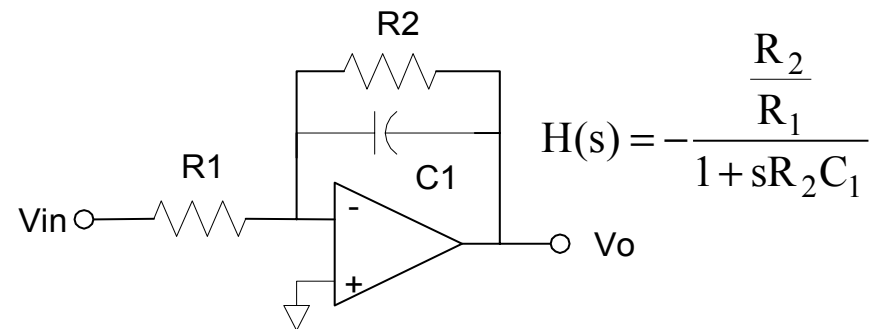
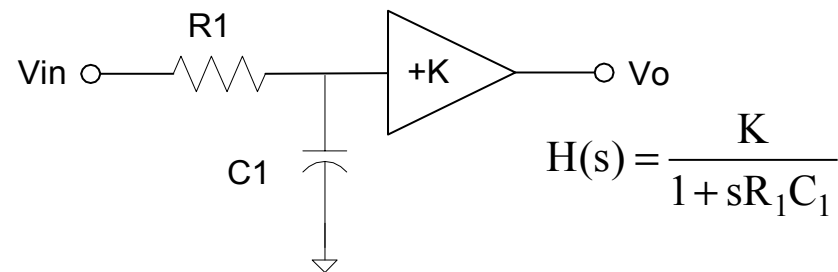
$$\text{Phase}(H(j\omega)) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$




Introduction: First-order Filter

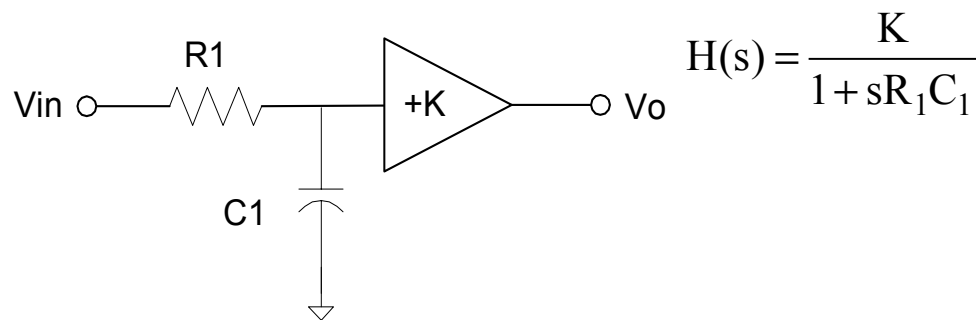


$$H(s) = \frac{K}{1 + sR_1C_1}$$

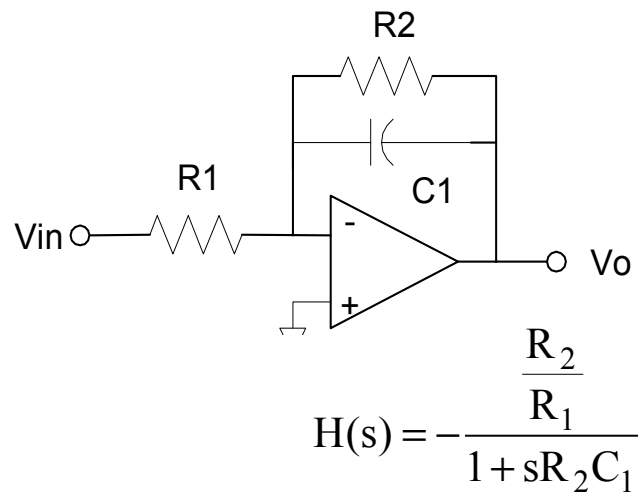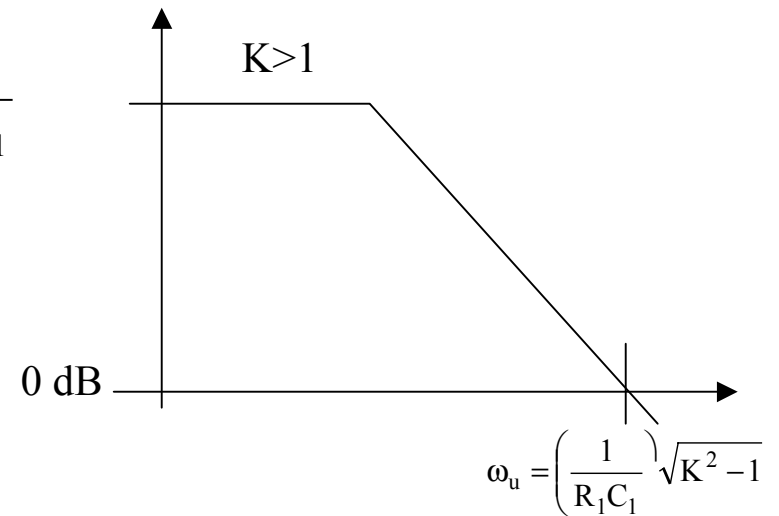

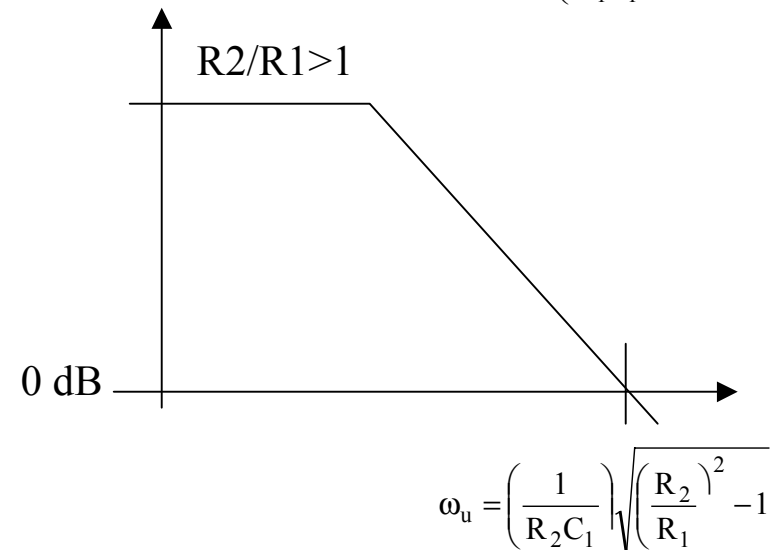
$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C_1}$$




Introduction: First-order Filter

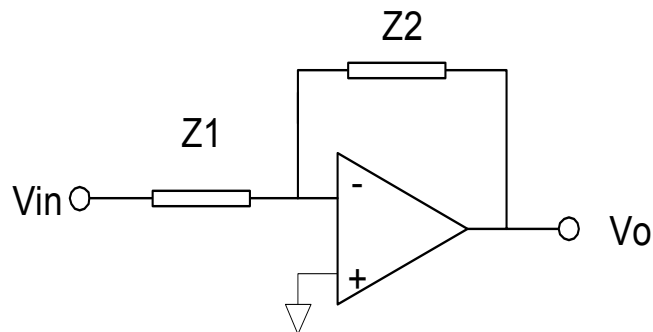
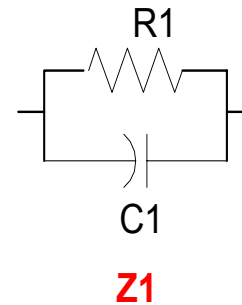
$$H(s) = -\frac{Z2}{Z1} = -\frac{Y1}{Y2}$$




$$Y1 = g_1 + sC_1$$

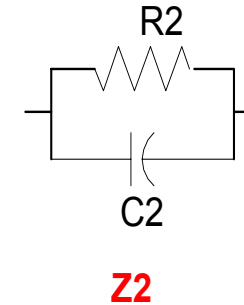


$$Y2 = g_2 + sC_2$$
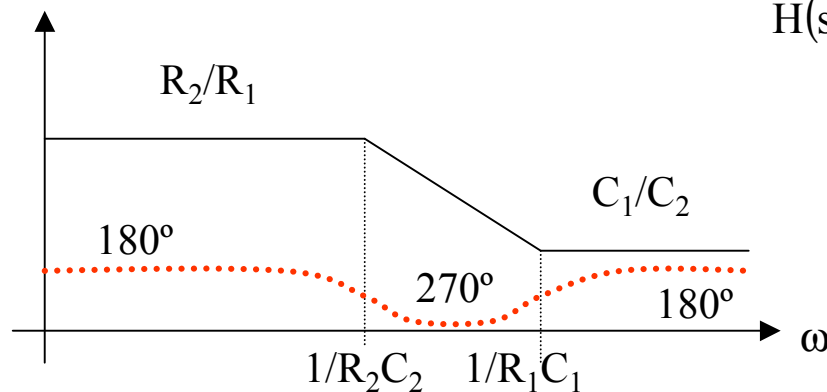
$$H(s) = -\frac{g_1 + sC_1}{g_2 + sC_2} = -\left(\frac{R_2}{R_1}\right) \left(\frac{1 + sR_1C_1}{1 + sR_2C_2}\right)$$



- **LH Pole** => **negative (lag) excess phase**
- **LH Zero** => **positive (lead) excess phase**

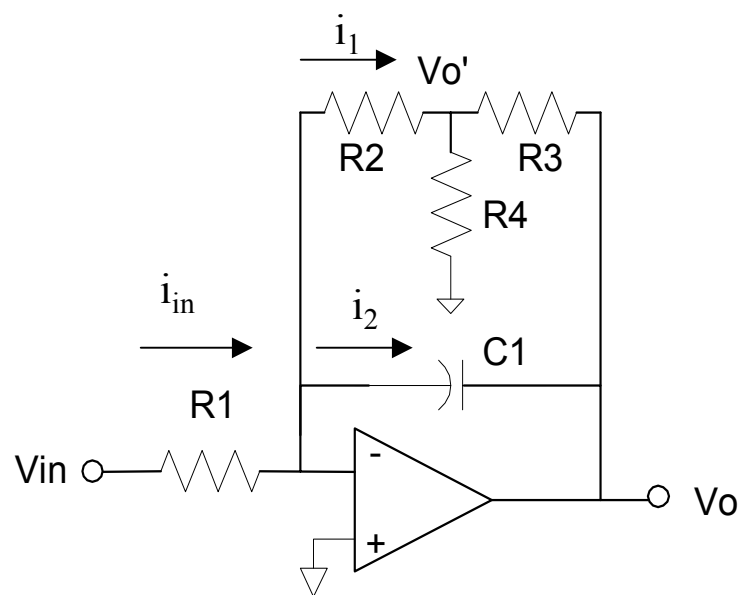
Introduction: Large resistor implementation



Notice that
$$V_{O'} = \frac{R_2 \parallel R_4}{R_3 + (R_2 \parallel R_4)} V_O = \alpha V_O$$

$$i_{in} = g_1 v_{in}$$
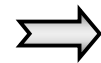
$$i_1 = -g_2 v_{O'} \quad ; \quad i_2 = -sC_1 v_O$$



$$i_{in} = g_1 v_{in} = (\alpha g_2 + sC_1) v_O$$

$$H(s) = -\frac{g_1}{\alpha g_2} \frac{1}{1 + s \left(\frac{C_1}{\alpha g_2} \right)} = -\frac{R_2}{\alpha R_1} \frac{1}{1 + s \left(\frac{R_2 C_1}{\alpha} \right)}$$

$$\alpha = \frac{R_2 R_4}{R_3 (R_2 + R_4) + (R_2 R_4)} = \frac{1}{\left(\frac{R_3}{R_2} + \frac{R_3}{R_4} \right) + 1}$$

- **Effective R_2 is R_2/α**
- **The smaller α the larger the equivalent resistance**
- **The attenuation factor α can be easily reduced**


Biquadratic Function: Frequency Domain Analysis

$$H(s) = \frac{K\omega_0^2}{s^2 + BWs + \omega_0^2}$$

$$H(j\omega) = \frac{K\omega_0^2}{(\omega_0^2 - \omega^2) + j(BW\omega)}$$

$$|H(j\omega)| = \frac{K\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (BW\omega)^2}}$$
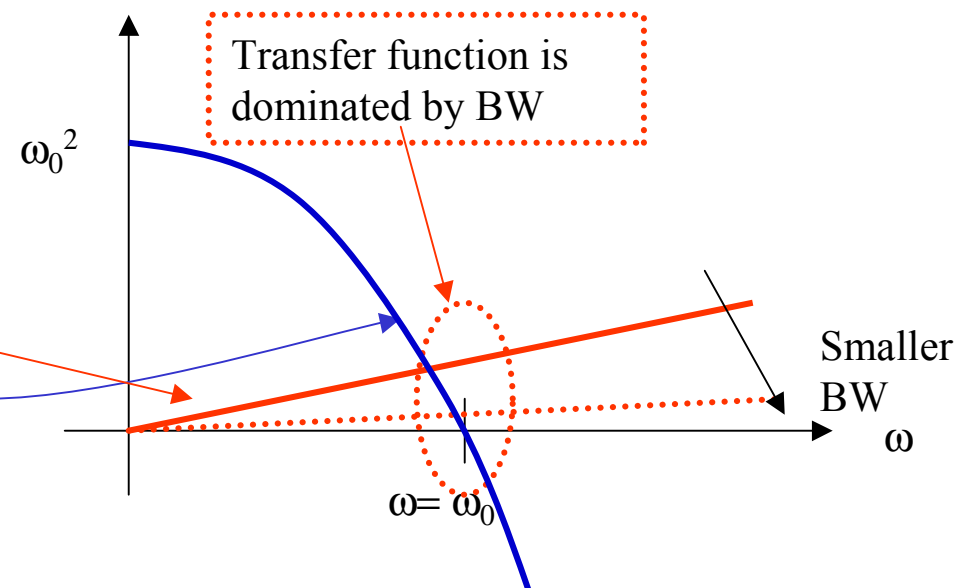
$$\text{Phase}(H(j\omega)) = \tan^{-1}\left(\frac{\text{im}(H(j\omega))}{\text{real}(H(j\omega))}\right)$$



Any small parameter variation around $\omega = \omega_0$ produces huge variations on the overall transfer function.

Narrow-band filters (small BW) are more critical!!


Frequency Domain

$$H(s) = \frac{K\omega_0^2}{s^2 + BWs + \omega_0^2}$$

$$|H(j\omega)| = \frac{K\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (BW\omega)^2}}$$

$$\text{Phase}(H(j\omega)) = \tan^{-1}\left(\frac{\text{im}(H(j\omega))}{\text{real}(H(j\omega))}\right)$$
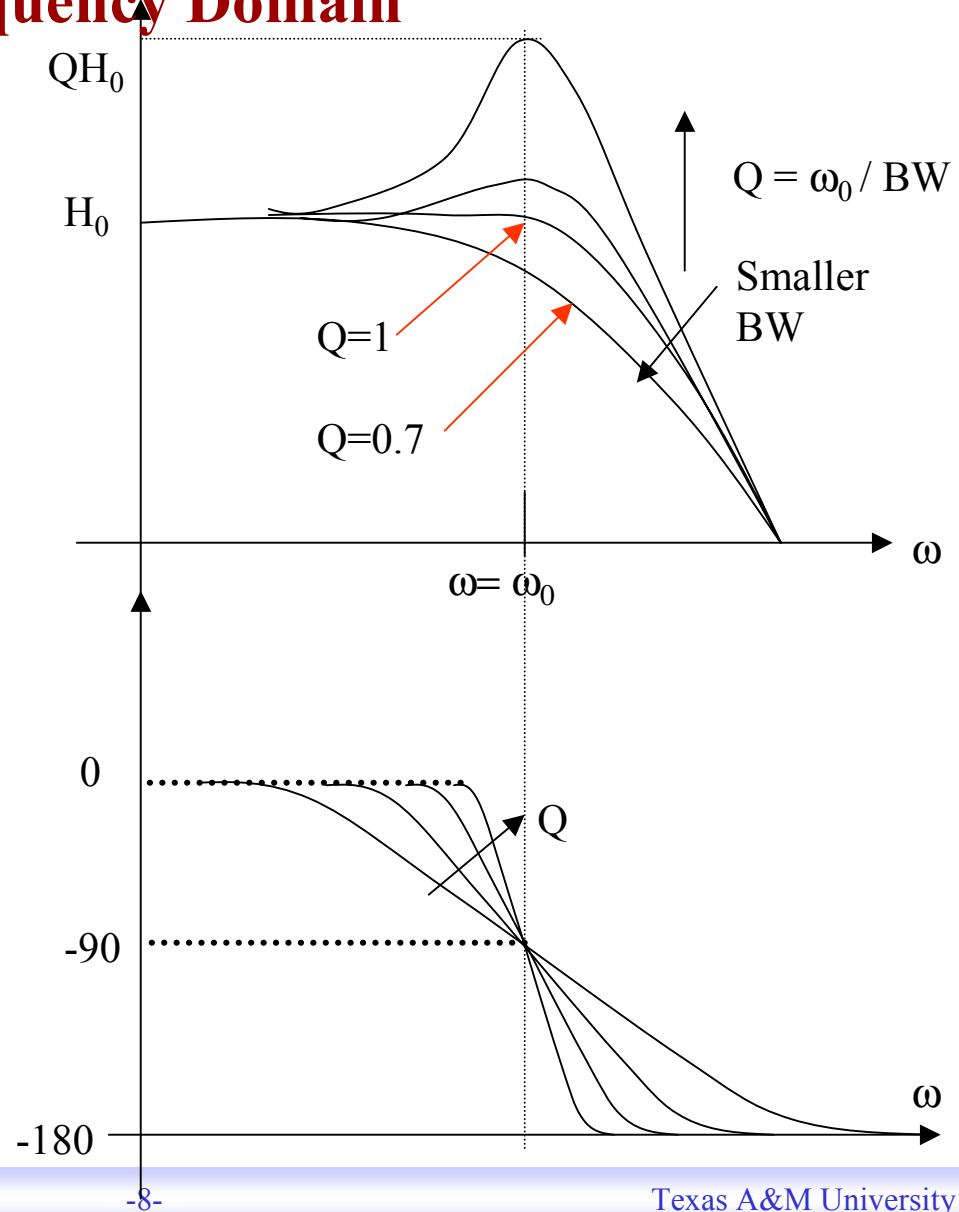
$$\text{Phase}(H(j\omega)) = -\tan^{-1}\left(\frac{BW\omega}{\omega_0^2 - \omega^2}\right)$$



SENSITIVITY

$$\frac{f}{x} = \left(\frac{x}{f} \right) \frac{\partial}{\partial x} f \cong \left(\frac{x}{\Delta x} \right) \left(\frac{\Delta f}{f} \right) = \frac{\Delta f}{\frac{f}{x}} \quad \text{Practical implication} \Rightarrow \boxed{\frac{\Delta f}{f} = \left(\frac{f}{x} \right) \frac{\Delta x}{x}}$$

If you know the sensitivity function, then you can evaluate the effect on f of variations in parameter x !

Notice that sensitivity relates the normalized (percentage) errors; e.g. for a sensitivity function of 10, variations of 10% in x produces f variations of 100%. Sensitivity of 0.1 will produce a variation of 1%.

SENSITIVITY: properties

$$\frac{df}{dx} = \frac{f}{x}$$

$$\frac{dx}{dx} = 1$$

$$\frac{d^n f}{dx^n} = n$$

$$\frac{dx}{dx} = 1$$

$$\frac{df}{dx} = \left(\frac{1}{n} \right) \frac{f}{x}$$

$$\frac{\partial \Pi(f_1, \dots, f_n)}{\partial x} = \sum \left(\frac{f_1}{x} + \dots + \frac{f_n}{x} \right)$$

$$\frac{df_i}{dx} = \frac{\left(\frac{f_i}{x} \right)}{f_i}$$

$$\frac{dkx}{x} = \frac{x}{kx} = 1$$

$$\frac{dx}{kx} = \frac{1}{k}$$

$$\frac{d^n x}{dx^n} = n$$

$$\frac{dx}{x} = \frac{f}{g} - \frac{g}{f}$$

$$\frac{df}{g} = \frac{f}{g} - \frac{g}{f}$$

$$\frac{dx}{x} = \frac{x}{x} = 1$$

EXAMPLE 1:

$$BW = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_2}$$

$$\frac{BW}{R_1} = \frac{\frac{1}{R_1 C_1}}{BW} = -\frac{1}{BW} = -\frac{1}{1 + \frac{R_1 C_1}{R_2 C_2}}$$

EXAMPLE 2: Sallen & Key

$$BW = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} (1-K)$$

$$\frac{BW}{K} = \frac{1-K}{R_2 C_2} \frac{1-K}{K} = \frac{1-K}{R_2 C_2} \left(\frac{-K}{1-K} \right)$$

$$= -\frac{K}{\frac{R_2 C_2}{R_1 C_1} + \frac{C_2}{C_1} + (1-K)}$$

SENSITIVITY: properties

EXAMPLE3:

$$BW = \frac{g_{eq}}{C_1} = \frac{g_1 + g_2}{C_1}$$

$$\frac{BW}{g_1} = \frac{g_1}{g_1 + g_2} < 1$$

Little sensitive

$$BW = \frac{g_{eq}}{C_1} = \frac{g_1 - g_2}{C_1}$$

$$\frac{BW}{g_1} = \frac{g_1}{g_1 - g_2} = \frac{1}{1 - \frac{g_2}{g_1}} > 1$$

Very sensitive to conductance mismatches
This is the case if you use negative resistors for gain enhancement!!

The use of negative elements is attractive because you can drastically reduce the spread of the components (due to the subtraction).

Unfortunately the sensitivity increases drastically!!

➔ TRADEOFF: Spread \longleftrightarrow Sensitivity

For low sensitivity

$$\frac{f}{x} \leq 1$$

SENSITIVITY: properties


EXAMPLE 4:

$$H(s) = \frac{K\omega_0^2}{s^2 + BWs + \omega_0^2}$$

$$|H(j\omega)| = \frac{K\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (BW\omega)^2}}$$


$$\begin{aligned} \left. \frac{|H(j\omega)|}{\omega_0} \right|_{\omega=\omega_0} &= 2 - \frac{1}{2} \left(\frac{(\omega_0^2 - \omega^2)^2}{(\omega_0^2 - \omega^2)^2 + (BW\omega)^2} \right) \left(\frac{4\omega_0^2}{\omega_0^2 - \omega^2} \right) = 2 \left(1 - \frac{(\omega_0^2 - \omega^2)\omega_0^2}{(\omega_0^2 - \omega^2)^2 + (BW\omega)^2} \right) \\ &= 2 \left(\frac{(BW\omega)^2 - (\omega_0^2 - \omega^2)\omega^2}{(\omega_0^2 - \omega^2)^2 + (BW\omega)^2} \right) \end{aligned}$$

$$\left. \frac{|H(j\omega)|}{BW} \right|_{\omega=BW} = \frac{1}{2} \left(\frac{2(BW\omega)^2}{(\omega_0^2 - \omega^2)^2 + (BW\omega)^2} \right) = \frac{(BW\omega)^2}{(\omega_0^2 - \omega^2)^2 + (BW\omega)^2}$$

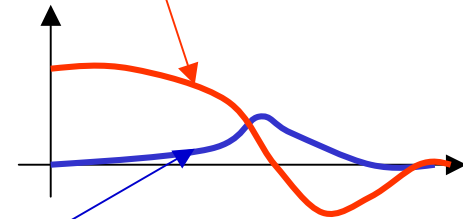

These results are general!!

Low-Gain Filters: Sallen-Key

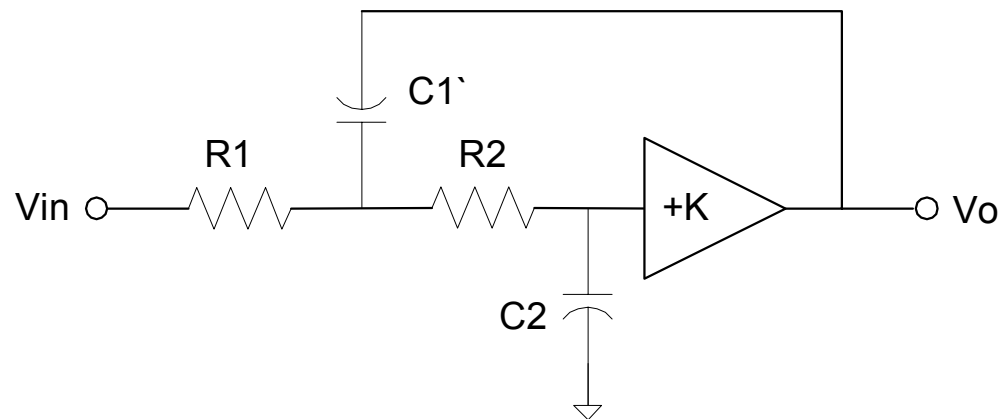

- Why this topology
- behaves as LPF?
- How stable is this circuit if K is precise?
- Practical Limits?
- How to design a filter?


$$H(s) = \frac{K \left(\frac{1}{R_1 R_2 C_1 C_2} \right)}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} (1-K) \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

At $\omega=0$, capacitors are open circuits and $H(s)=K$

At $\omega \sim \omega_0$, all impedances are important

At $\omega=\infty$, capacitors are dominant

Low-Gain Filters: Sallen-Key

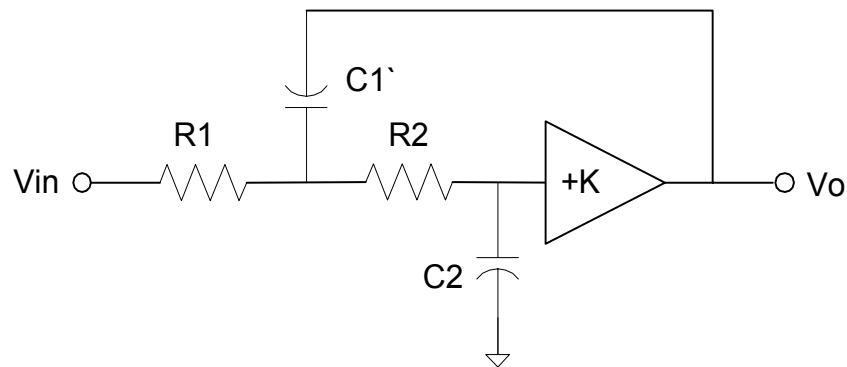

Lowpass

$$H(0) = K$$

$$\omega_0^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$H(\omega = \omega_0) = \frac{K}{\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} (1-K) \right)}$$

$$BW = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} (1-K)$$


$$H(s) = \frac{K \left(\frac{1}{R_1 R_2 C_1 C_2} \right)}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} (1-K) \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

At $\omega=0$, $H(s)=K$

At $\omega \sim \omega_0$, all impedances are important

Meaning of $-K$? Positive feedback!!!

Low-Gain Filters: Sallen-Key

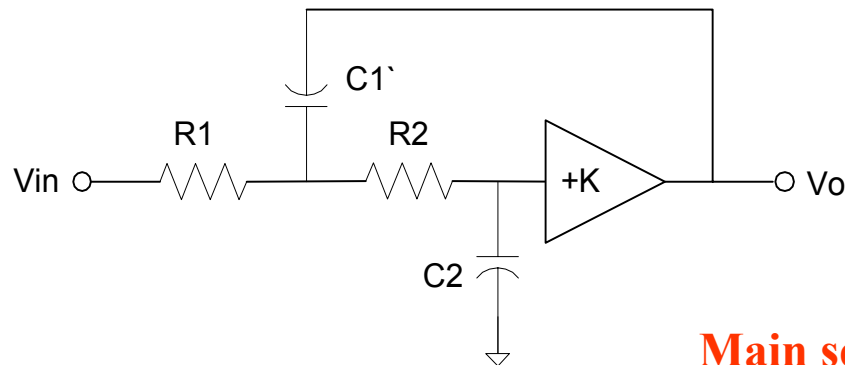

$$H(s) = \frac{K \left(\frac{1}{R_1 R_2 C_1 C_2} \right)}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} (1-K) \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

Main sensitivities:

$$H(0) = K$$

$$\omega_0^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$H(\omega = \omega_0) = \frac{K \omega_0}{\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} (1-K) \right)}$$

$$BW = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} (1-K)$$


**Can you design low sensitive narrow-band filters?
If not, why not?**

$$|H(j0)| = 1$$

$$\frac{K}{\omega_0} = -\frac{1}{2}$$

$$\begin{aligned} \frac{|H(\omega_0)|}{K} &= 1 - \frac{1}{BW} \left(\frac{-K}{R_2 C_2} \right) \\ &= 1 + \frac{1}{\frac{R_2 C_2}{R_1 C_1} + \frac{C_2}{C_1} + 1 - K} \end{aligned}$$

Low-Gain Filters: Sallen-Key BP filter

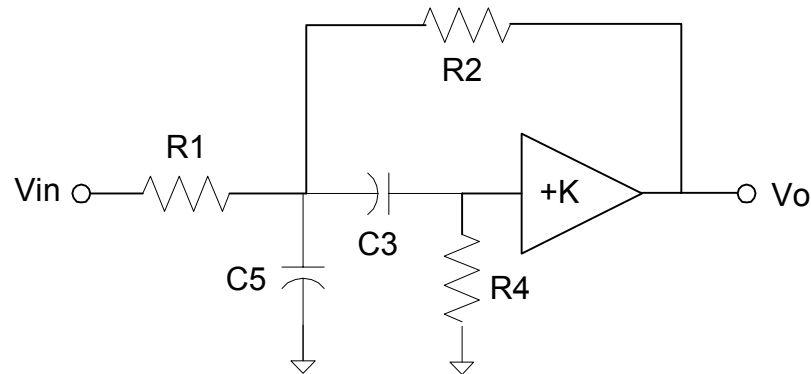

$$H(s) = \frac{sK \left(\frac{1}{R_1 C_5} \right)}{s^2 + \left(\frac{1}{R_1 C_5} + \frac{1}{R_4 C_5} + \frac{1}{R_4 C_3} + \frac{1-K}{R_2 C_5} \right) s + \frac{1}{R_4 C_3 C_5} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)}$$

Typical design approach : C3=C5, K=2

$$\omega_0^2 = \frac{1}{R_4 C_3 C_5} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$H(\omega = \omega_0) = \frac{K \left(\frac{1}{R_1 C_5} \right)}{\frac{1}{R_1 C_5} + \frac{1}{R_4 C_5} + \frac{1}{R_4 C_3} + \frac{1-K}{R_2 C_5}}$$

$$BW = \frac{1}{R_1 C_5} + \frac{1}{R_4 C_5} + \frac{1}{R_4 C_3} + \frac{1-K}{R_2 C_5}$$

$$|H(j\omega)| = 1$$

K


$$\omega_0 = -\frac{1}{2}; \quad \omega_0 < -\frac{1}{2}$$

$R_4, C_{3,5}$

R_1, R_2

$$\frac{BW}{K} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_4} + \frac{R_2 C_5}{R_4 C_3} + 1 - K}$$

Low-Gain Filters: Sallen-Key BP filter

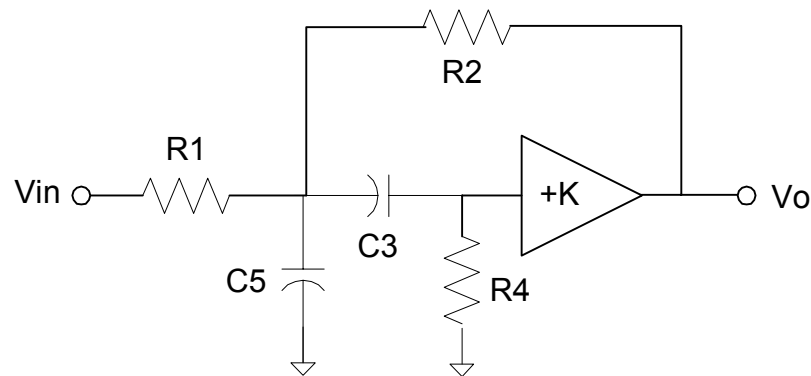

$$f_0 = 10\text{kHz}$$

$$\text{BW} = 1\text{kHz}$$

$$Q = 10$$

Peak gain?

**Typical design approach : $C_3=C_5$,
 $R_1=R_2=R_3$**

$$\omega_0^2 = \frac{2}{R_1^2 C_3^2}$$

$$R_1 C_3 = 2.25 \times 10^{-5}$$

$$H_{\text{peak}} = \frac{K}{4-K}$$

$$K = 3.8565$$

$$Q = \frac{\sqrt{2}}{4-K}$$



$$H_{\text{peak}} \sim 27 !!$$


$$\frac{\text{BW}}{K} = \frac{1}{4-K}$$



$$\frac{\text{BW}}{K} = 7.07 !!$$

Can you design same filter using $K=2$? Sensitivities?

Low-Gain Filters: Sallen-Key HP filter

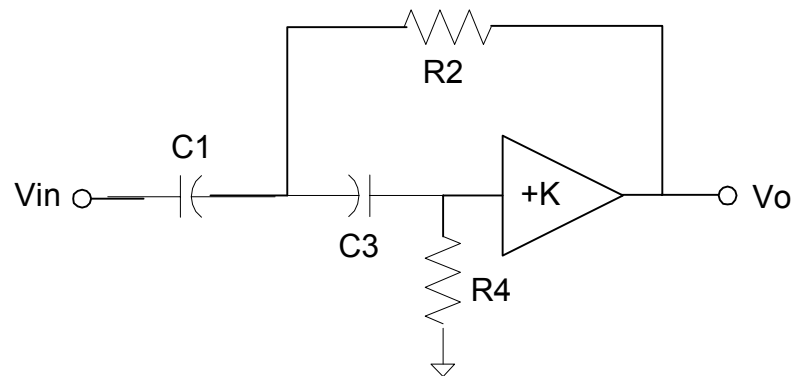

$$H(s) = \frac{s^2 K}{s^2 + \left(\frac{1}{R_4 C_3} + \frac{1}{R_4 C_1} + \frac{1-K}{R_2 C_1} \right) s + \frac{1}{R_2 R_4 C_1 C_3}}$$

$$\omega_0^2 = \frac{1}{R_2 R_4 C_1 C_3}$$


$$H(\omega = \infty) = K$$

$$H(\omega = \omega_0) = \frac{K \omega_0}{\frac{1}{R_4 C_3} + \frac{1}{R_4 C_1} + \frac{1-K}{R_2 C_1}}$$

$$BW = \frac{1}{R_4 C_3} + \frac{1}{R_4 C_1} + \frac{1-K}{R_2 C_1}$$


Sensitivities are similar for all these topologies

High-Gain Filters: Multiple Feedback

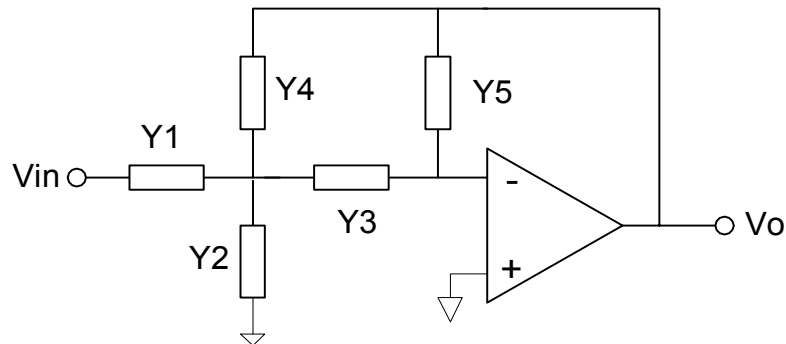

$$H(s) = \frac{-Y_1 Y_3}{Y_5 (Y_1 + Y_2 + Y_3 + Y_4) + Y_3 Y_4}$$

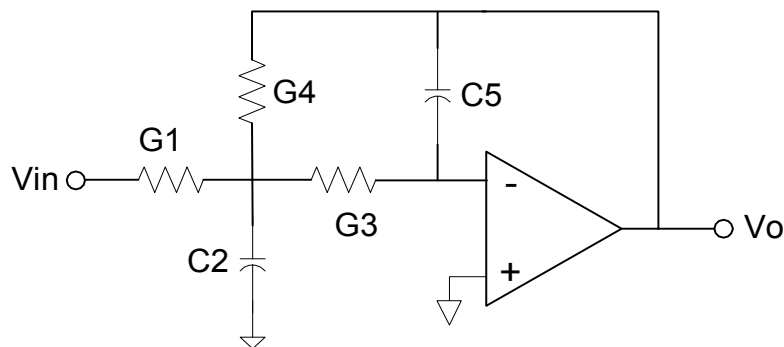- For LP filter: Y_1 and Y_3 must be conductance and Y_5 must be capacitor
- For BP filter: Y_1 or Y_3 must be capacitors
- For HP filter: Y_1 , Y_3 and either Y_4 or Y_5 must be capacitors as
- Notice that all sensitivities are less than 1! (why?)



Low-pass filter

$$H(s) = \frac{-G_1 G_3}{s^2 C_5 C_2 + s C_5 (G_1 + G_3 + G_4) + G_3 G_4}$$


$$\omega_0^2 = \frac{1}{C_5 C_2 R_3 R_4}$$

$$BW = \frac{1}{(R_1 \parallel R_3 \parallel R_4) C_2}$$

**All sensitivities
are = < 1 !!!**

High-Gain Filters: Multiple Feedback
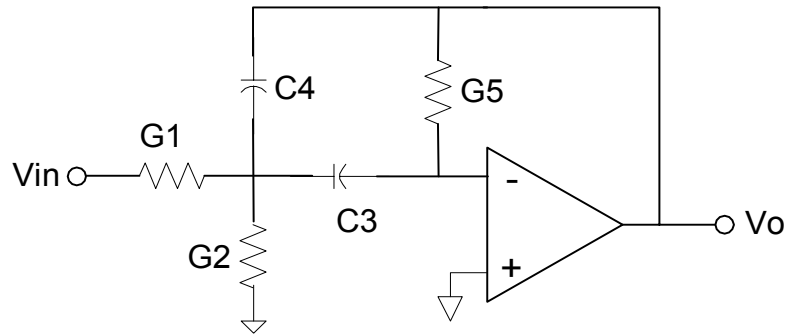
$$H(s) = \frac{-Y_1 Y_3}{Y_5(Y_1 + Y_2 + Y_3 + Y_4) + Y_3 Y_4}$$




Band-pass filter

$$H(s) = \frac{-sG_1 C_3}{s^2 C_3 C_4 + sG_5(C_3 + C_4) + G_2 G_5}$$

$$\omega_0^2 = \frac{1}{C_5 C_2 R_2 R_5}$$

**Sensitivities
are = < 1**
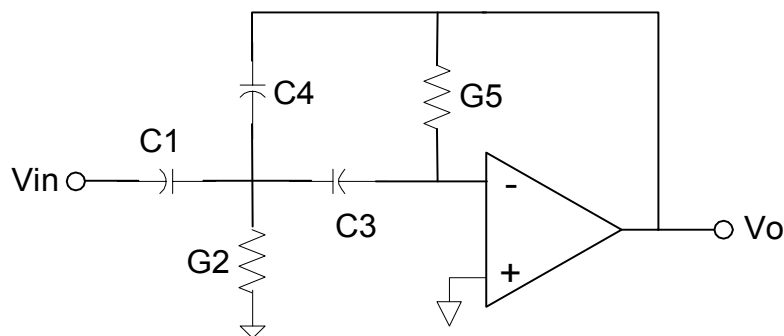
$$BW = \frac{1}{\left(\frac{C_3 C_4}{C_3 + C_4}\right) R_5}$$



High-pass filter

$$H(s) = \frac{-s^2 C_1 C_3}{s^2 C_3 C_4 + sG_5(C_1 + C_3 + C_4) + G_2 G_5}$$

$$\omega_0^2 = \frac{1}{C_3 C_4 R_2 R_5}$$

**Sensitivities
are = < 1**

$$BW = \frac{1}{\left(\frac{C_3 C_4}{C_1 + C_3 + C_4}\right) R_5}$$