

## HOMWORK ASSIGNMENT #5

1. ( For 622) Design a BP filter using transconductance -mode building blocks. The filter is a 4<sup>th</sup> order filter composed of equal second order BP with the following specifications  $H(j\omega)=1.4142$ ,  $f_0=1.1\text{GHz}$ ,  $\text{BW}=65\text{MHz}$ ,  $V_{dd}=-V_{ss}=1.65\text{V}$  and  $0.35\mu\text{m}$  CMOS technology.
2. ( For 458) Same as above but do not design at the transistor level, use OTA macro-model and identify the values of the  $G_m$  and excess phase for the OTA requirements
3. Using a second-order or fourth order BP of previous problem, design an oscillator for  $f_0= 1.1\text{GHz}$ . Describe the design procedure and the comparator used, search for current comparators in the literature. For 622 include transistor level design, for 458 only macromodel level with non-idealities.
4. Design a 5-th Order Active RC Inverse Chebyshev for  $19.7\text{ MHz}$  at the transistor ( system for 458) level meeting the draft IEEE 802.11n. Use  $0.13\mu\text{m}$  technology. DC gain of  $2\text{db}$ .  $V_{dd} = 1.8\text{v}$ . Compare your results with the previously reported filter in JSCC, Nov 2007.