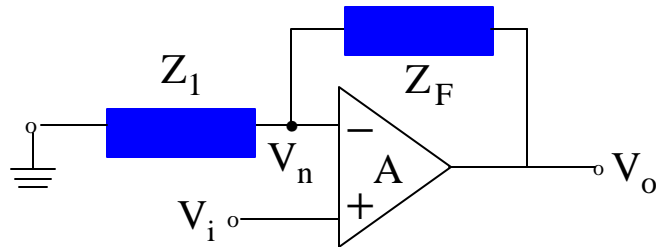


# Fully Balanced, Fully Differential Circuits



# Fully Differential Fully Balanced Circuits

What is the problem with single-input / single-output?



$$V_n = \frac{V_o Z_1}{Z_1 + Z_F}$$

$$V_i - V_n = \frac{V_o}{A} \Big|_{A \rightarrow \infty} = 0$$


For  $V_i = V_{id} + V_{icm}$

$$V_o = \left( 1 + \frac{Z_F}{Z_1} \right) (V_{id} + V_{icm})$$



No elimination of common-mode signal.

How to solve this problem?

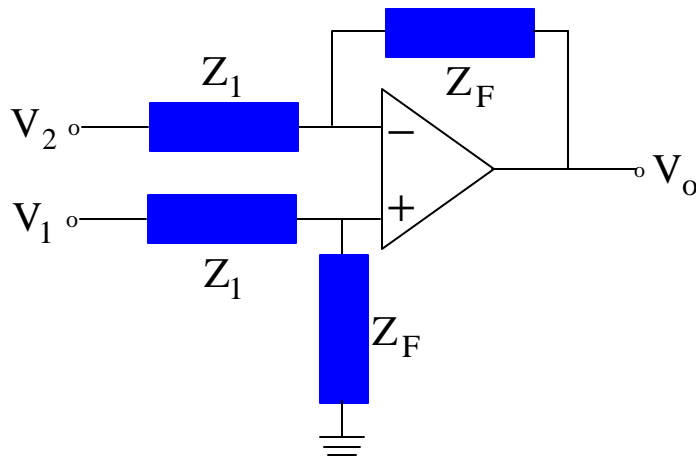

$$\text{For } V_i = V_{id} + V_{icm} = (V_1 - V_2) + \frac{(V_1 + V_2)}{2}$$


$$V_o = \frac{Z_F}{Z_1} (V_1 - V_2)$$



No common-mode output.


How to obtain a fully differential circuit?  
 We will discuss two potential approaches

Approach 1

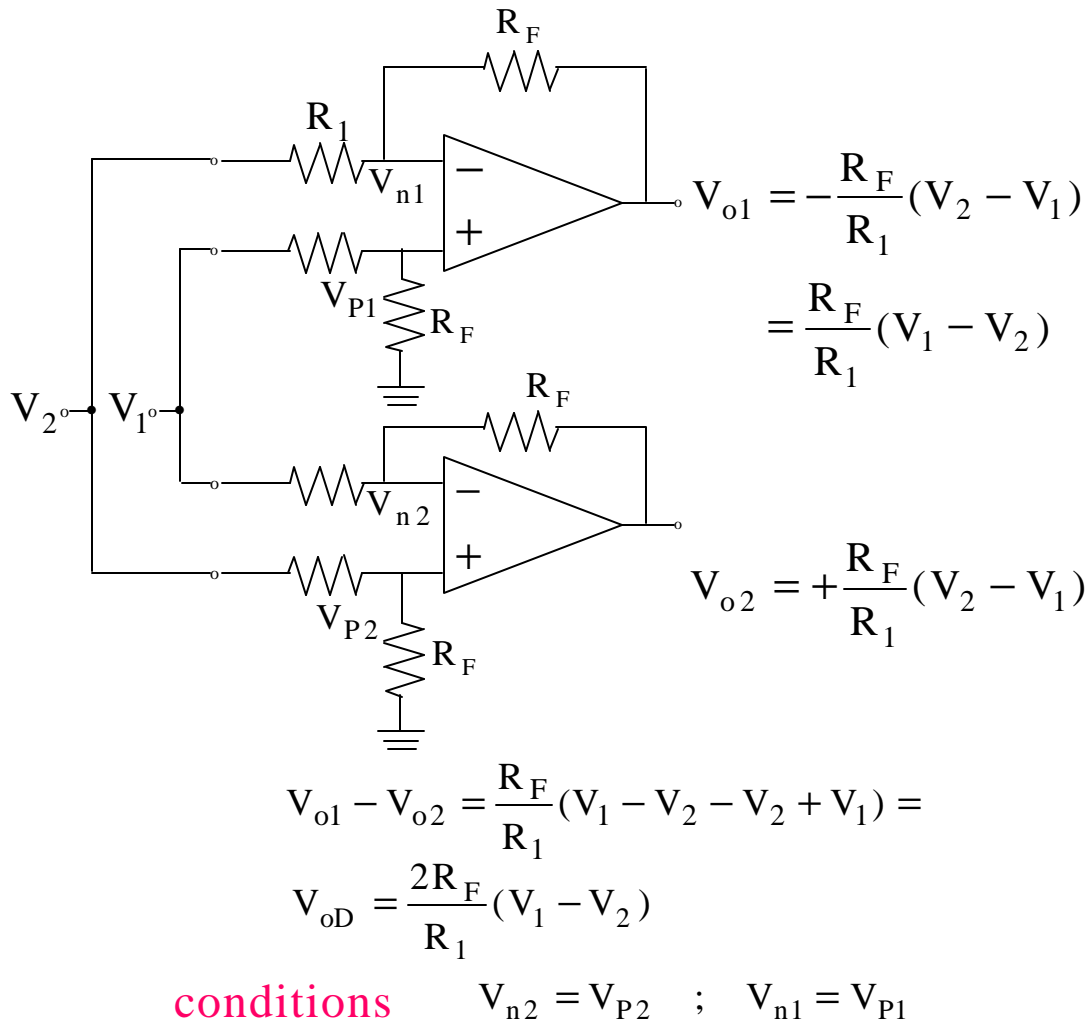

Remark: sensitive to CM signals

Approach 2

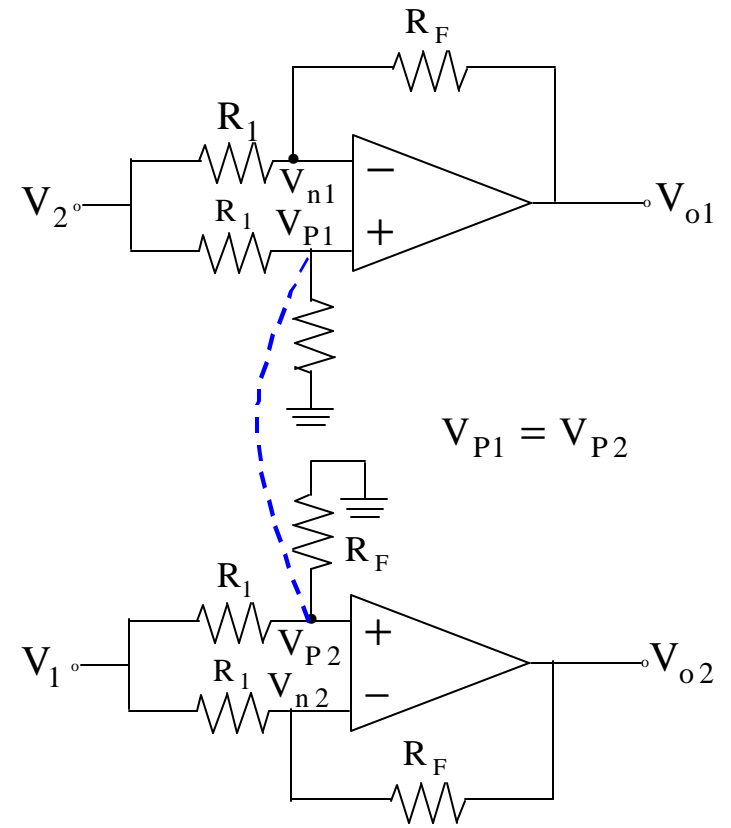

Remark:  
 More robust to reject  
 common-mode signals


# First-Order FB Low Pass with Op Amp

\*


```

.subckt opamp non inv out
rin non inv 100K
egain 1 0 (non, inv) 200K
ropen 1 2 2K
copen 2 0 15.9155u
eout 3 0 (2, 0) 1
rout 3 out 50
.ends

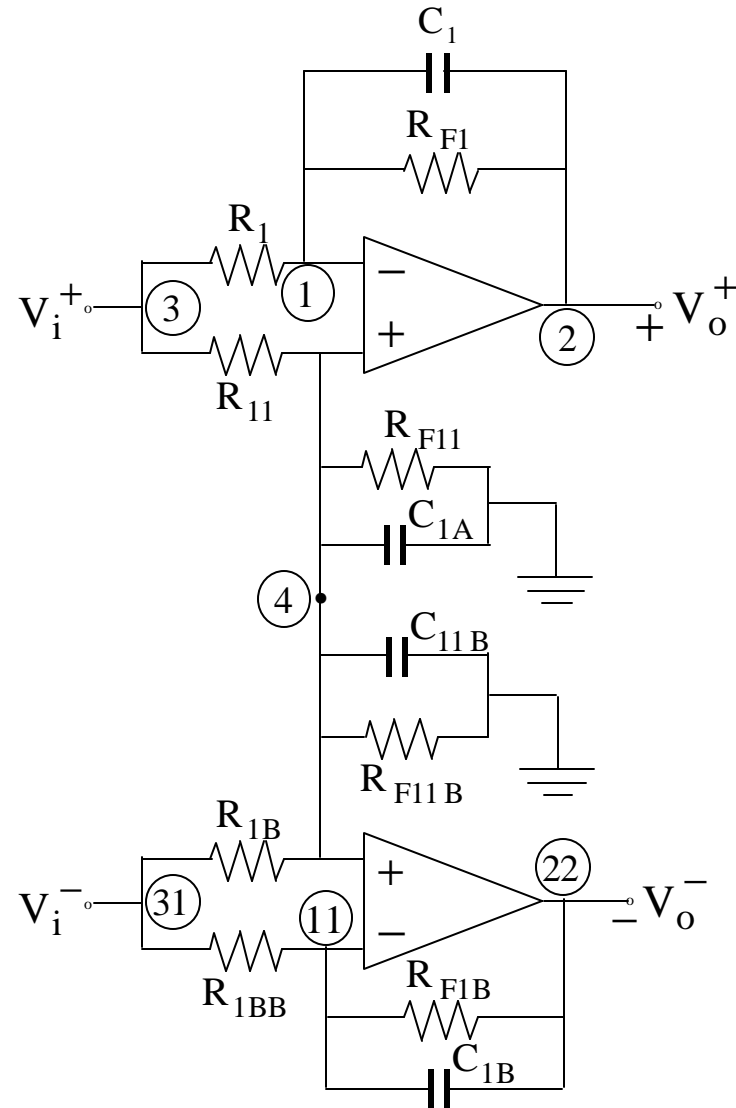
*vin 3 31 ac 1.0
vin 31 0 ac 1.0
x1 4 1 2 opamp
x2 4 11 22 opamp
R1 3 1 1K
R11 3 4 1K
R1B 31 4 1K
R1BB 31 11 1K
RF1 2 1 1K
RF1B 22 11 1K
RF11 4 0 1K
RF11B 4 0 1K
C1 2 1 0.159155u
C1B 22 11 0.159155u
C1A 4 0 0.159155u
C11B 4 0 0.159155u
rdummy 3 31 1
.ac dec 10 10Hz 10KHz
.probe
.end
    
```




## A Two-Integrator Active-RC Filter

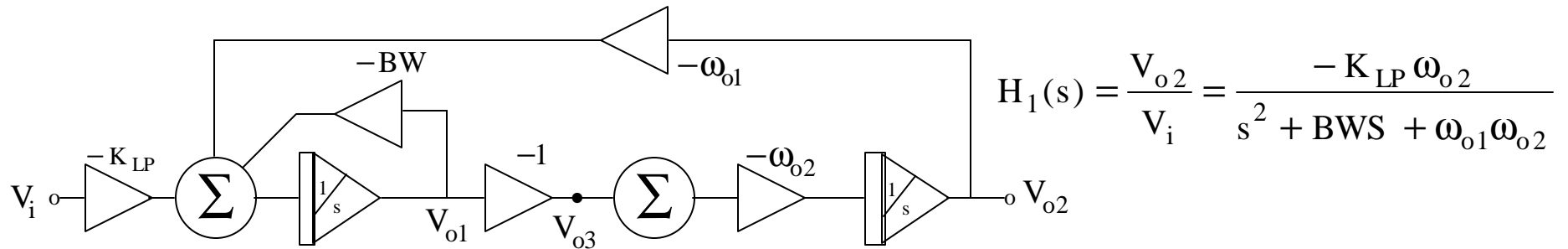

(a) Block Diagram

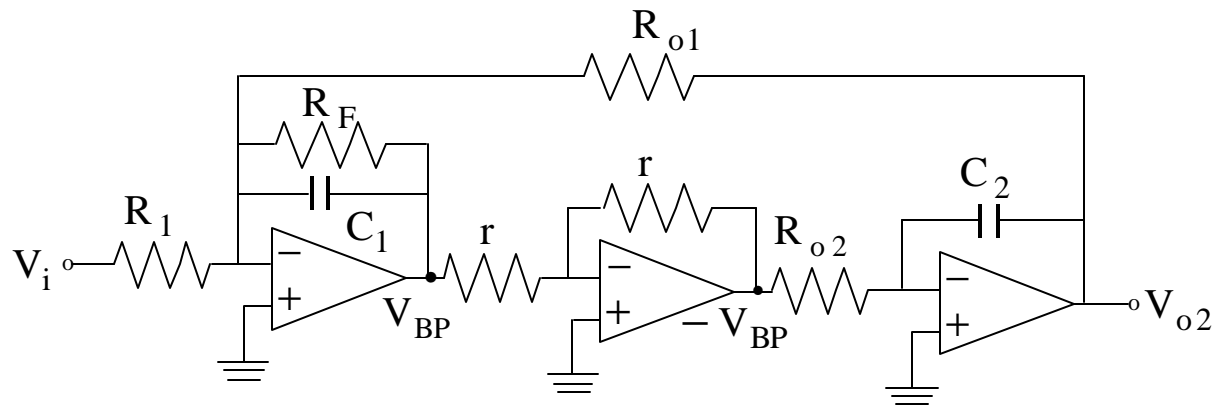

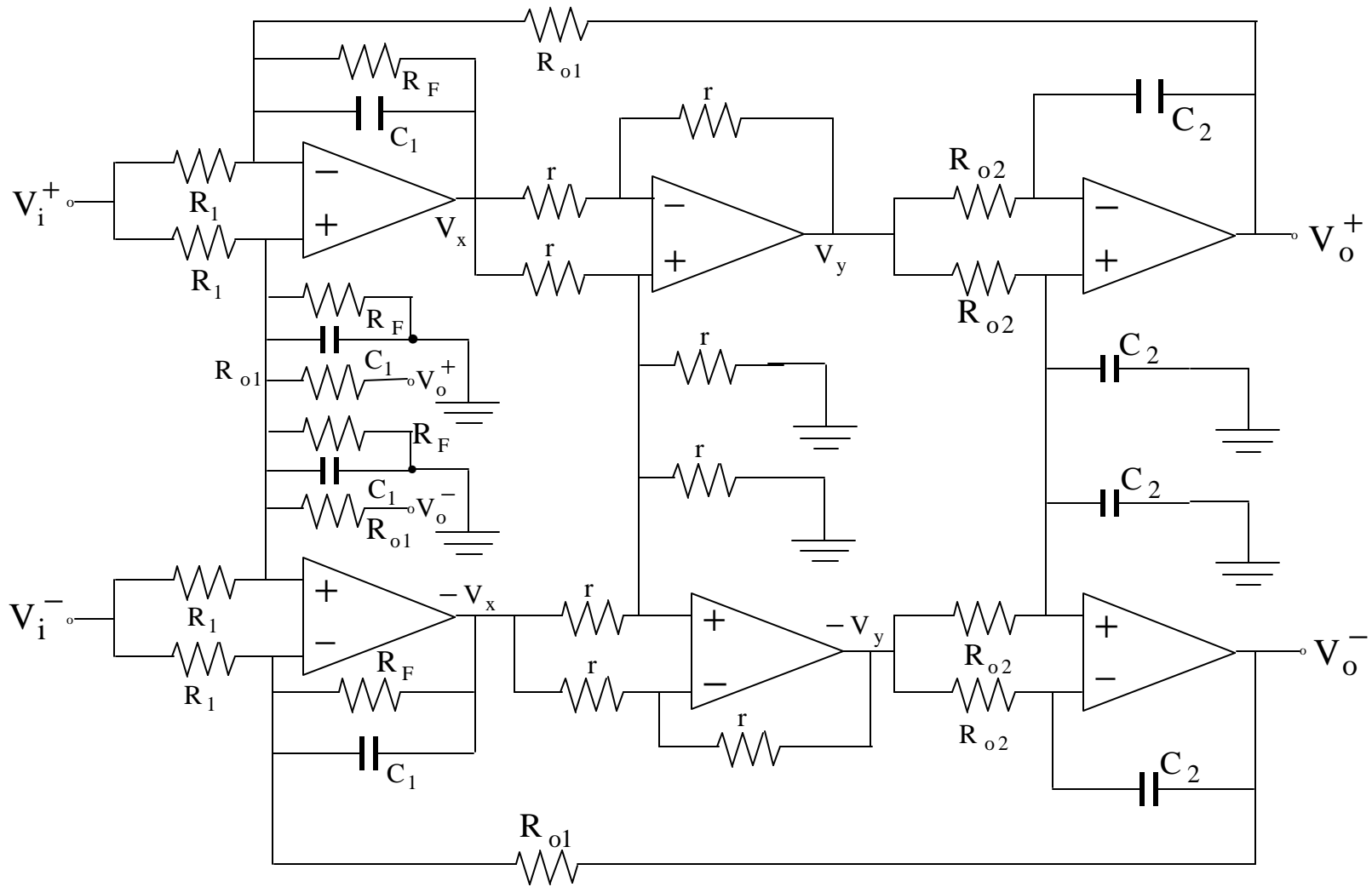(b) Active RC Implementation (single-ended)



(c) Fully Balanced, Fully-Differential (not simplified)

Second-Order FB Low Pass with Op Amp

```

*
.subckt opamp non inv out
rin non inv 100K
egain 1 0 (non, inv) 200K
ropen 1 2 2K
copen 2 0 15.9155u
eout 3 0 (2, 0) 1
rout 3 out 50
.ends

```

```


vin 3 31 ac 1.0
*vin 0 31 ac 1.0
*ein 3 0 (31, 0) 1
x1 4 1 2 opamp
x2 4 11 22 opamp
R1 3 1 1K R11 3 4 1K
R1B 31 4 1K
R1BB 31 11 1K
RF1 2 1 1K
RF1B 22 11 1K
RF11 4 0 1K
RF11B 4 0 1K
C1 2 1 0.159155u
C1B 22 11 0.159155u
C1A 4 0 0.159155u
C11B 4 0 0.159155u
RO1A 4 0 1K
RO1B 4 0 1K
rdummy 3 31 1
Ro11 22 101 1K

```

```


Ro11a 22 104 1K
Ro11b 2 211 1K
Ro111 2 211 1K
C2 102 101 0.159155u
C2a 104 0 0.159155u
C2b 104 0 0.159155u
C2bb 222 211 0.159155u
* FEEDBACK RESISTORS
RO1 1 102 1K
RO2 11 222 1K
x3 104 211 222 opamp
x4 104 101 102 opamp
.ac dec 50 10Hz 12KHz
.probe
.end

```

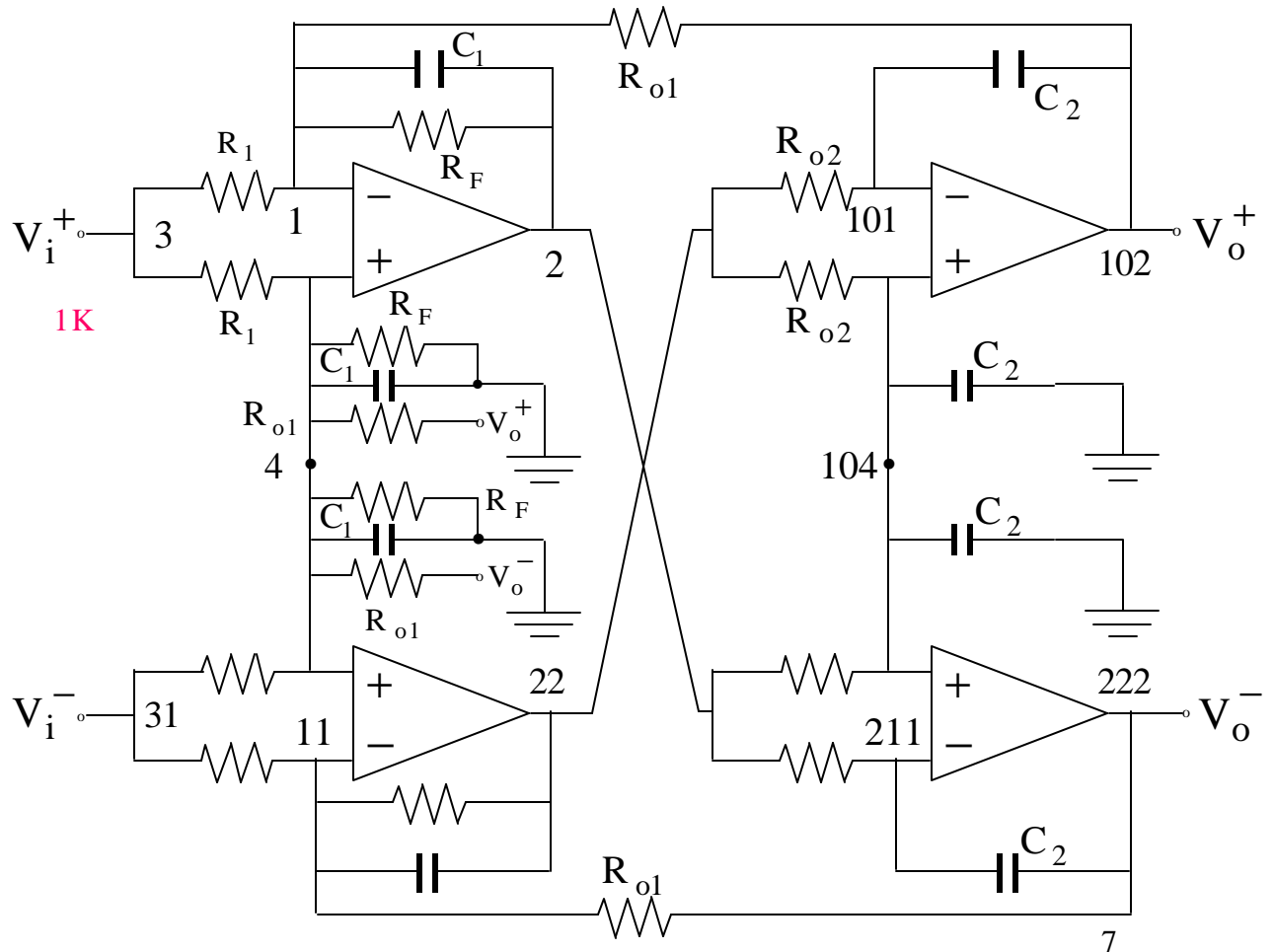


Fully Balanced Tow-Thomas Active RC: *CM output signals*

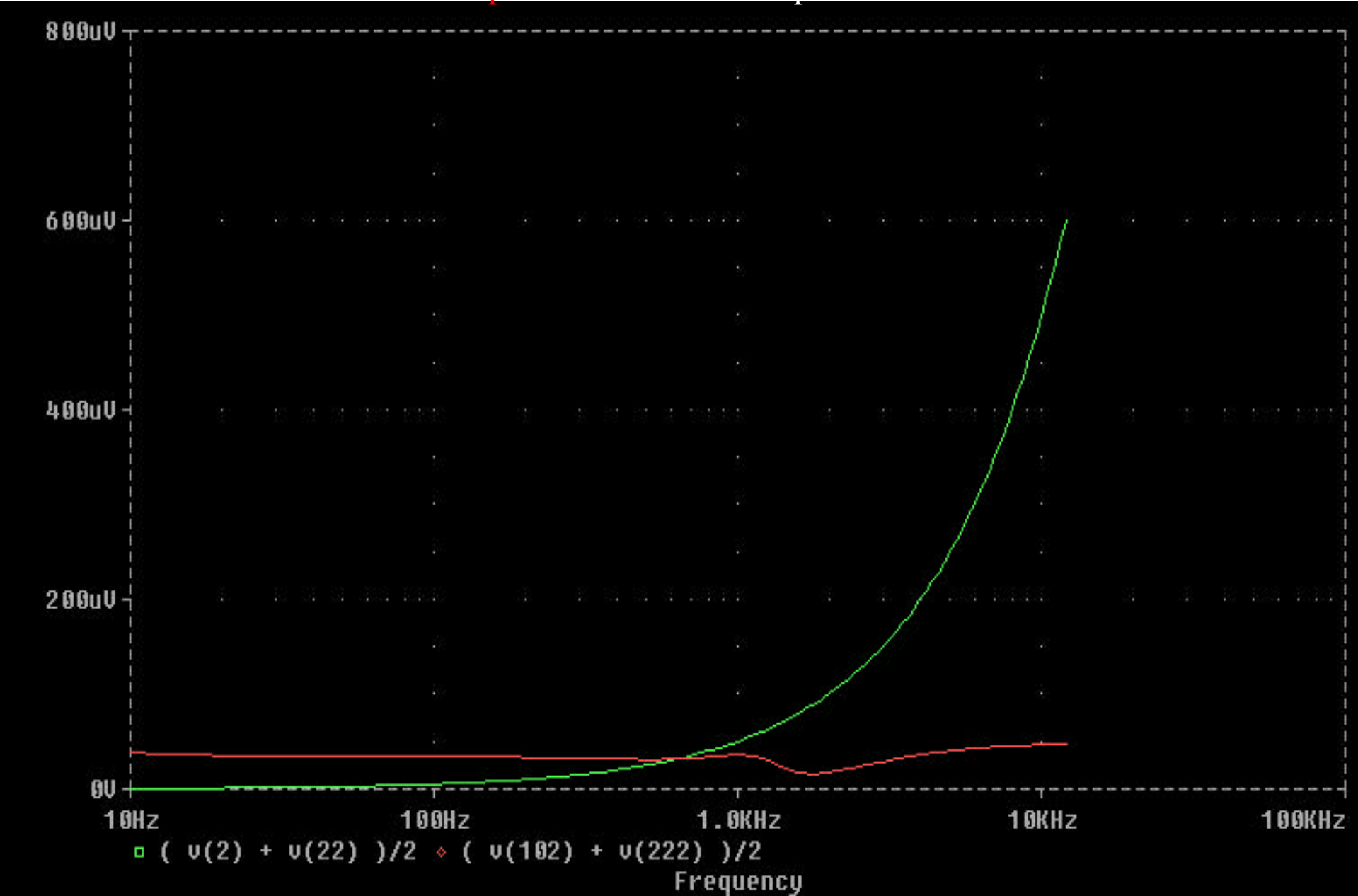$R_{o1}$  is connected between outputs and middle cm



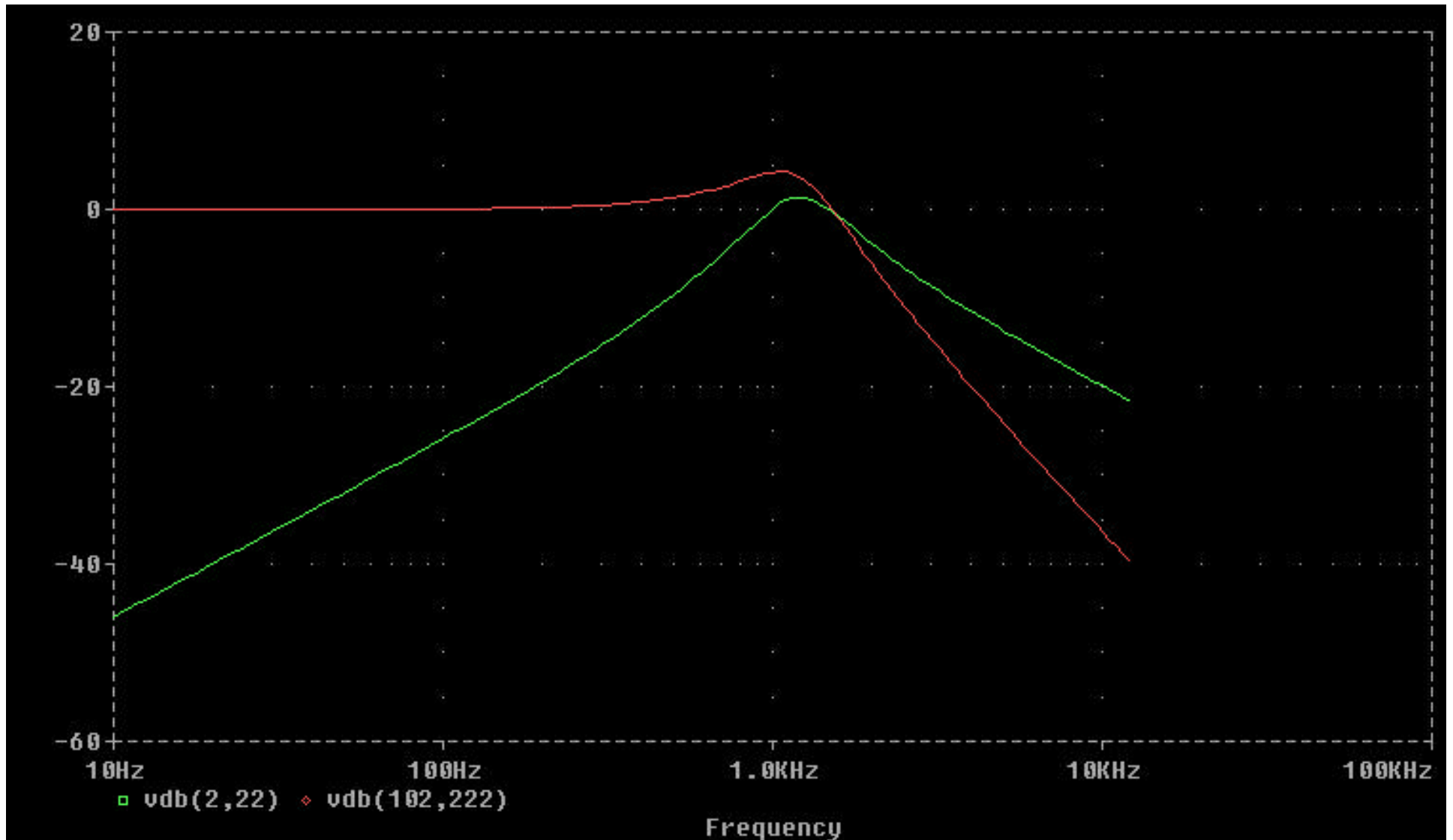
# Fully Balanced Active RC Fully Differential, : *Differential outputs*

Ro1 connected to the outputs and middle point cm, + terminal of Op Amps



For OTA the solution becomes

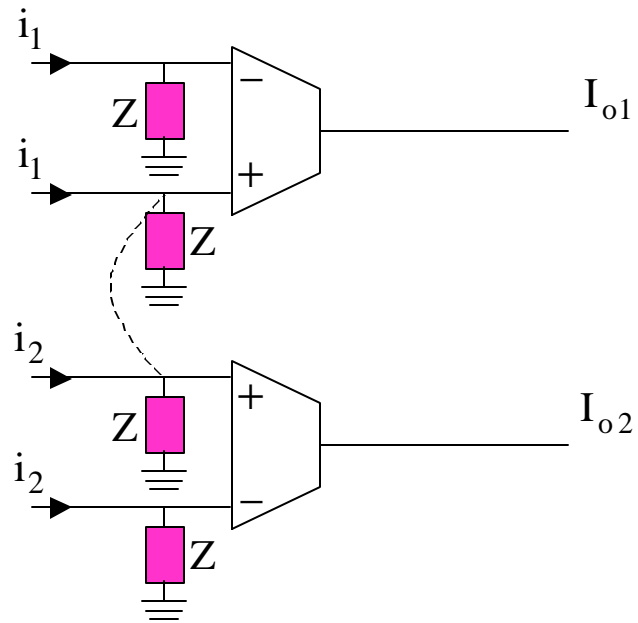

Every input should be in pairs of signal.