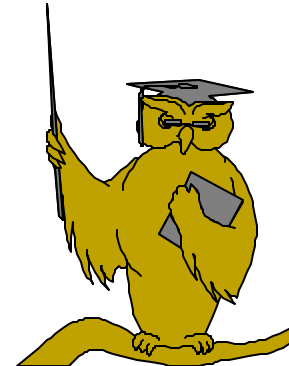


Switched- Capacitor Circuits





- Background on signals and systems
- Basic Building Blocks
 - Amplifiers
 - Integrators
- Biquadratic Filters
- References



Switched-Capacitor Techniques Advantages

- Reduced silicon area
- Good accuracy. Time constants are implemented with capacitor ratios ($\sim 0.1\%$)
- Don't require a low-impedance output stage (OTAs could be used)
- Could be implemented using digital circuit process technology
- Very useful in the audio range

Examples of Analog and Digital Signals

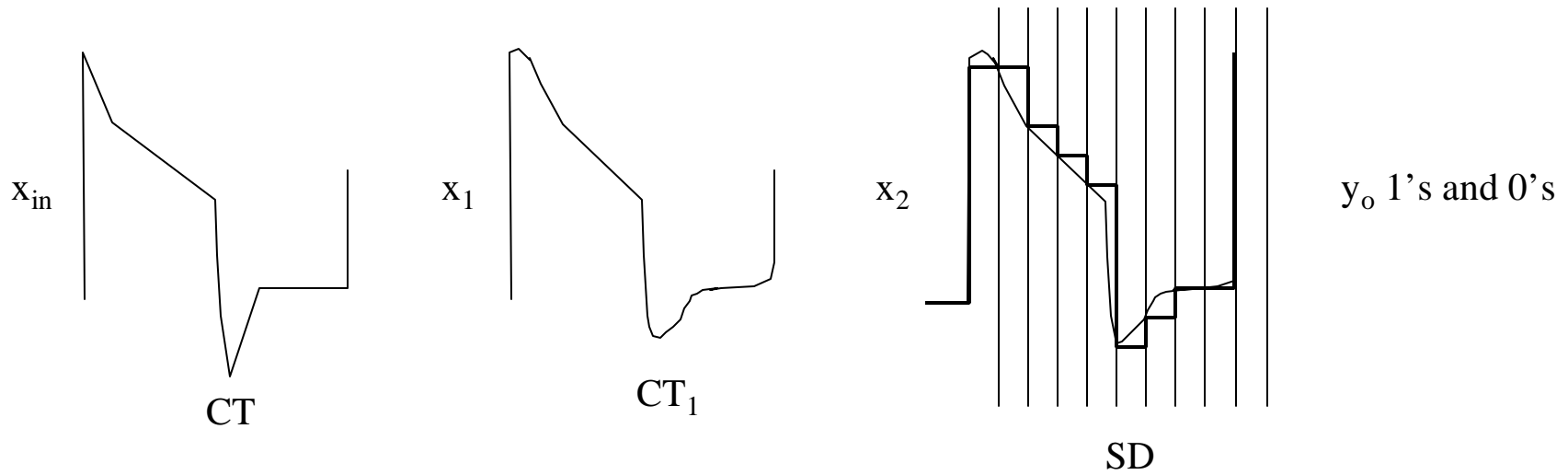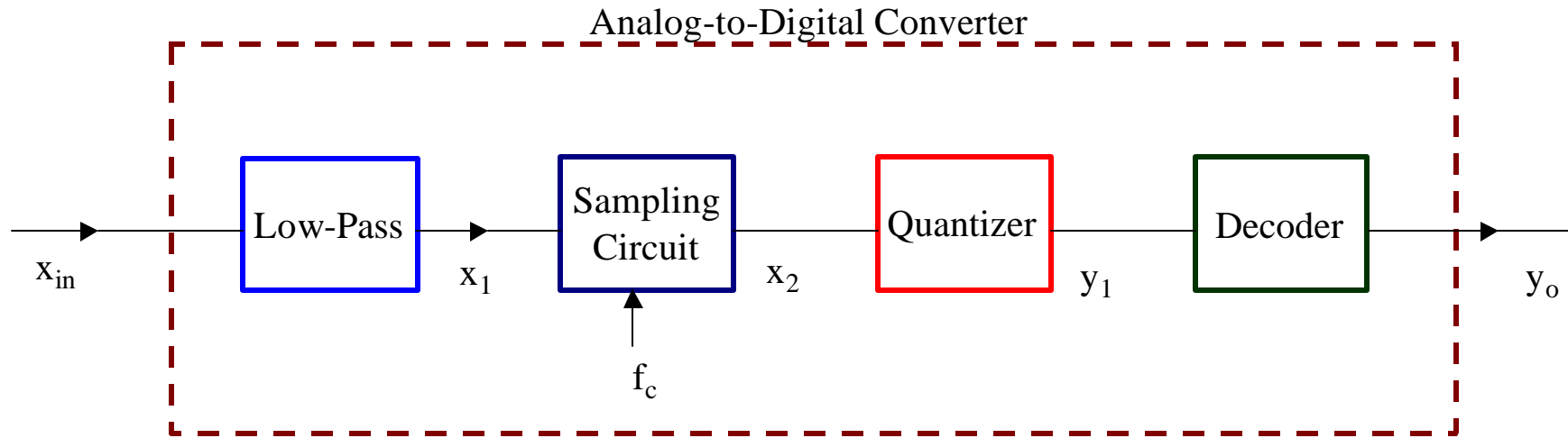

Analog Signal and Systems Concepts

Types of signals

Mathematical Description

- Continuous-Time (CT)
 - Continuous values in time
 - Continuous values in magnitude
- Sampled Data (SD)
 - Continuous values in magnitude
 - Discrete values in time
- Digital
 - Discrete values in magnitude
 - Discrete values in time

Laplace

Z-Transform


Z-Transform

Example of Basic Implementations

- First-order Low Pass


$$H(s) = \frac{K}{1 + s/\omega_p} ; \quad \frac{V_o(s)}{V_{in}(s)} = \frac{K\omega_p}{s + \omega_p} ; \quad \frac{dv_o(t)}{dt} + \omega_p v_o(t) = K\omega_p v_{in}(t)$$

Continuous-time

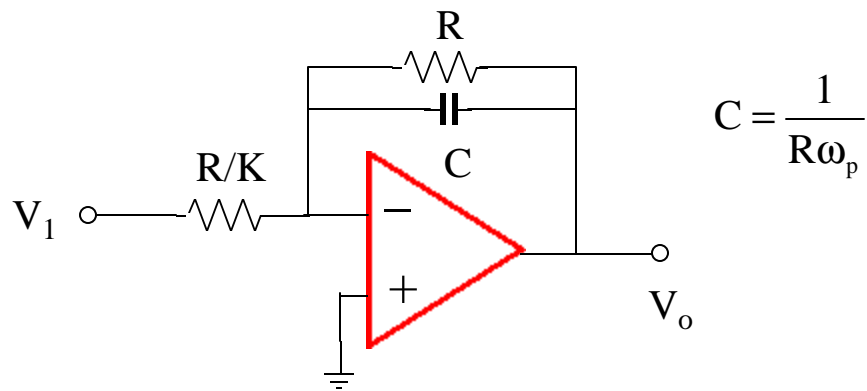


$$C = \frac{1}{R\omega_p}$$

s-plane

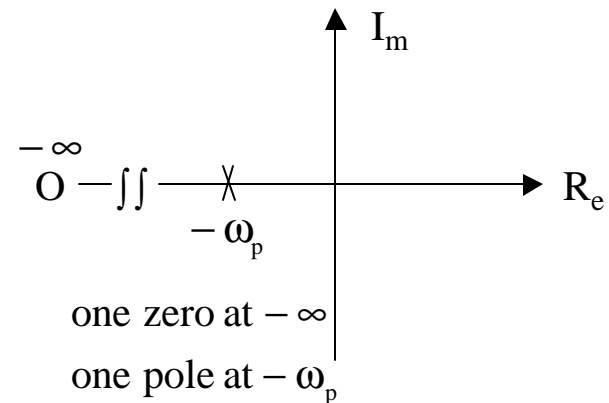


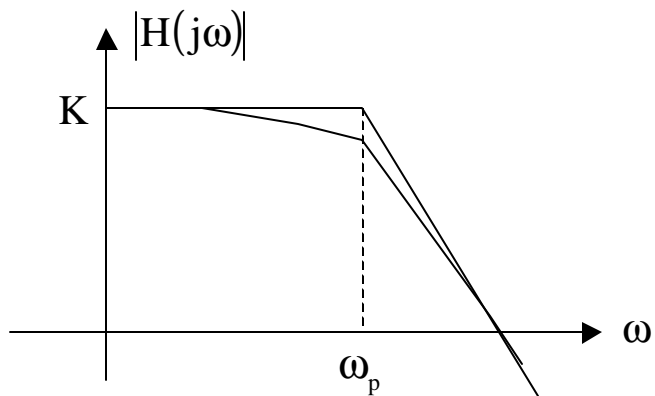Stability implies to have poles in the left-half plane (LHP)



Frequency Response

$$H(s) \Big|_{s=j\omega} = H(j\omega) = \frac{-K}{1+j\omega/\omega_p} = \frac{K}{[1+(\omega/\omega_p)^2]^{1/2}} \angle -\tan^{-1} \omega/\omega_p$$

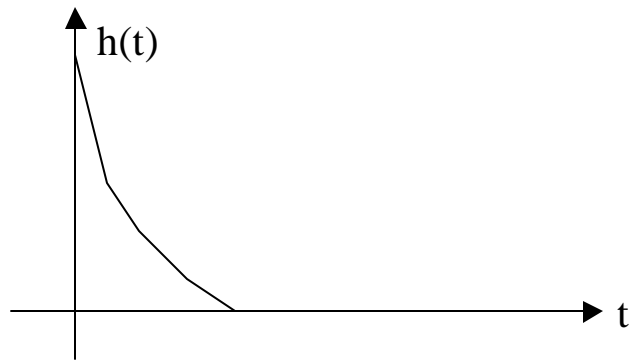

Impulse Response

$$h(t) = K\omega_p e^{-\omega_p t}$$

- **First-Order Low-Pass Sampled-Data** (i.e., Switched-Capacitor)

$$H(z) = \frac{V_o(z)}{V_{in}(z)} = \frac{K_1}{1 - z^{-1}/\omega_{pl}} = \frac{K_1 \omega_{pl}}{\omega_{pl} - z^{-1}} ;$$

$$[\omega_{pl} - z^{-1}]V_o(z) = K_1 \omega_{pl} V_{in}(z)$$

$$\omega_{pl} V_o(z) - z^{-1} V_o(z) = K_1 \omega_{pl} V_{in}(z)$$

Taking the inverse z-transform

$$\omega_{pl} v_o(nT) - v_o(n-1)T = K_1 \omega_{pl} v_{in}(nT)$$


$$v_o(n-1)T - \omega_p v_o(nT) = -K_1 \omega_{pl} v_{in}(nT)$$

This difference equation represents the first-order low pass in the Z-domain.


Note that

$$Z^{-1}X_o(z) \Rightarrow x_o(n-1)T$$

$$Z^{-b}X_o(z) \Rightarrow x_o(n-b)T$$

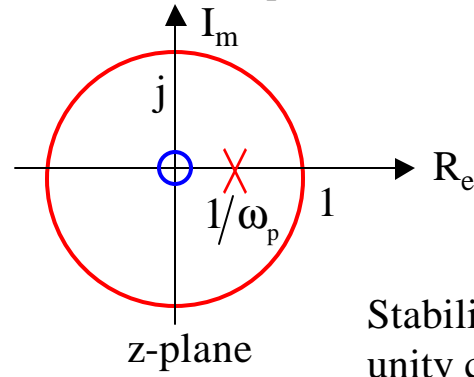

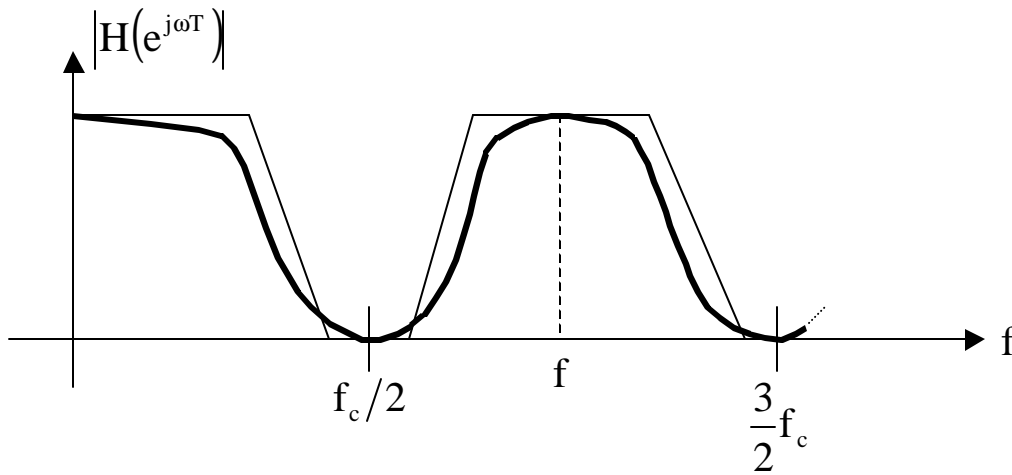
Stability implies poles inside
unity circle



Frequency Response (A periodic transfer function!)

$$H(z) = \frac{K_1 \omega_{p1} Z}{\omega_{p1} Z - 1} \bigg|_{z = e^{j\omega}} = \frac{K_1 \omega_{p1} (\cos \omega T + j \sin \omega T)}{(\omega_{p1} \cos \omega T - 1) + j \sin \omega T}$$
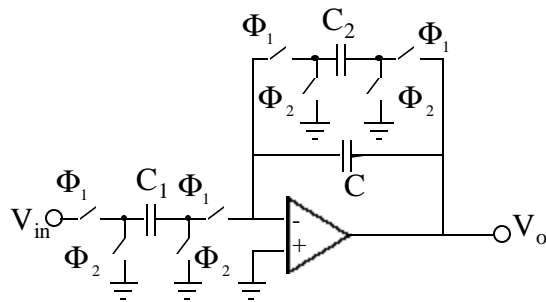
$$H(e^{j\omega}) = \frac{K_1 \omega_{p1}}{\{(\omega_{p1} \cos \omega T - 1)^2 + \sin^2 \omega T\}^{1/2}} \left[\overbrace{\omega T - \tan^{-1} \frac{\sin \omega T}{\omega_{p1} \cos \omega T - 1}}^{\text{phase}} \right]$$



where

$$K_1 \omega_{p1} = \frac{C_1}{C}$$

$$\omega_{p1} = 1 + \frac{C_2}{C}$$

What are the relationships between the s-plane and z-plane?

- There are a number of mappings between the two planes. All these mappings require frequency prewarping to yield quasi identical transfer functions in both planes. That is magnitude and phase of the two transfer functions should be as close as possible.
- The most popular and exact is the bilinear mapping.


$$s = \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}} = \frac{2}{T} \frac{z - 1}{z + 1} \quad \text{or} \quad z = \frac{1 + (T/2)s}{1 - (T/2)s} \quad \text{Pre-warping is needed:}$$
$$W = (2/T) \arctan(\omega T/2)$$

- The commonly used mapping from s - to z-plane, for high-sampling rate is the **forward mapping** :

$$s = \frac{1}{T} \frac{1 - z^{-1}}{z^{-1}} = \frac{1}{T} \frac{z - 1}{1}$$


or

$$z = sT + 1$$

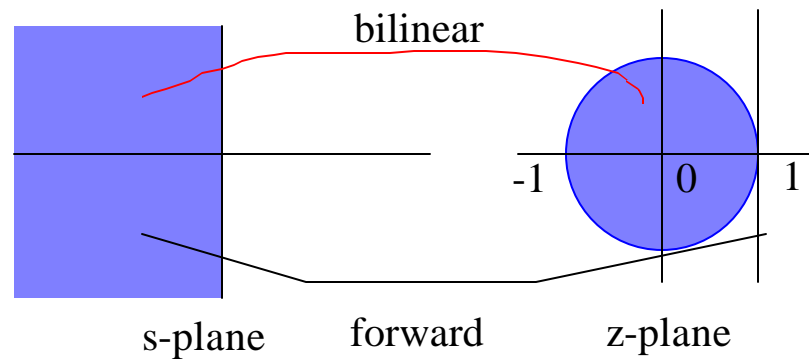


Example. Approximate a first-order low-pass continuous-time to a discrete-time low-pass under high-sampling conditions. ($f_s/f \gg 1$)

$$H(s) = \frac{K}{1 + s/\omega_p} = \frac{K\omega_p}{s + \omega_p} \quad \left| \quad s = \frac{1}{T}(z - 1) \right.$$

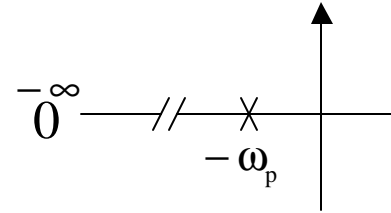
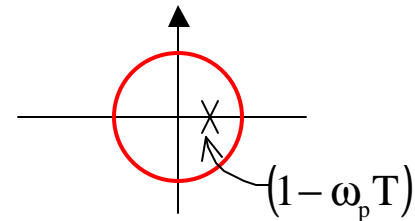
$$H(z) = \frac{K\omega_p T}{z - 1 + \omega_p T} = \frac{K\omega_p T}{z - (1 - \omega_p T)}$$



What is the 3dB cut-off frequency in both domains?

$$f_{3dB} = \omega_p \quad \text{CT}$$

For $H(z)$ is more complex than the computation of f_{3dB} .

$$H(e^{j\omega T}) = \frac{K\omega_p T}{\cos \omega T + j \sin \omega T - (1 - \omega_p T)}$$

$$\left| H(e^{j\omega T}) \right| = \left| H(e^{j\omega_{3dB} T}) \right| / \sqrt{2}$$

$$\omega = \omega_{3dB}$$

$$\omega_{3dB} = \frac{1}{T} \cos^{-1} \frac{2 - 2\omega_p T - (\omega_p T)^2}{2(1 - \omega_p T)}$$

Numerical example. Low-Pass (First Order)

$$\omega_p = 2\pi \times 10^3 \text{ r/s}$$

$$f_c = f_s = 20\text{KHz} \quad ; \quad T = 1/f_s \quad ; \quad \omega_p T = \frac{2\pi \times 10^3}{20 \times 10^3} = 0.1\pi$$

$$K = 2$$

For the continuous-time

$$f_{3\text{dB}} = 1\text{KHz}$$

$$H(j\omega) \Big|_{\omega = \omega_{3\text{dB}}} = \frac{2}{\sqrt{2}} = 1.4142$$

For the sample-data

$$f_{3\text{dB}} = \frac{f_s}{2\pi} \cos^{-1} \frac{2 - 2\omega_p T - (\omega_p T)^2}{2(1 - \omega_p T)}$$

$$f_{3\text{dB}} \cong 1.16\text{KHz}$$

Switched - Capacitor Filters

- Use Z-transform mathematics
- Are described by difference equations
- Time constants are proportional to capacitor ratios
- There are well defined mappings between the s- and z-plane which involve some frequency warping
- Originally the basic goal was to replace resistors by switches and capacitors. Now we focus on how to implement $H(z)$
- This design approach is one of the most popular in the industry. Basic components are switches, capacitors and Op Amp (usually OTAs)

$$H(z) = \frac{b_2 z^{-2} + b_1 z^{-1} + b_0}{1 - a_1 z^{-1} + a_2 z^{-2}} \bigg|_{z = \hat{z} + 1} = \frac{\beta_2 \hat{z}^{-2} + \beta_1 \hat{z}^{-1} + \beta_0}{1 + \alpha_1 \hat{z}^{-1} + \alpha_2 \hat{z}^{-2}}$$

$$\beta_0 = b_0, \quad \beta_1 = 2b_0 + b_1, \quad \beta_2 = b_1 + b_2 + b_0$$

$$\alpha_1 = 2 - a_1, \quad \alpha_2 = 1 + a_2 - a_1$$

Table Generic Biquadratic Transfer Function in the \hat{z} - and z -domains, $a_1 = 2r \cos Q$ and $a_2 = r^2$, $a_1 = a$ and $a_2 = b$.


| Generic Form | Numerator $N(z)$ | Numerator $N(\hat{z})$ |
|----------------------------|---|--|
| LP 20 (bilinear transform) | $K(1 + z^{-1})^2$ | $K(1 + 4\hat{z}^{-1} + 4\hat{z}^{-2})$ |
| LP 11 | $Kz^{-1}(1 + z^{-1})$ | $K(2\hat{z}^{-1} + 1)\hat{z}^{-1}$ |
| LP 10 | $K(1 + z^{-1})$ | $K(2\hat{z}^{-2} + 3\hat{z}^{-1} + 1)$ |
| LP 02 (forward transform) | Kz^{-2} | $K\hat{z}^{-2}$ |
| LP 01 | Kz^{-1} | $K(1 + \hat{z}^{-1})\hat{z}^{-1}$ |
| LP 00 (backward transform) | K | $K(1 + \hat{z}^{-1})^2$ |
| BP 10 (bilinear transform) | $K(1 - z^{-1})(1 + z^{-1})$ | $K(1 + 2\hat{z}^{-1})$ |
| BP 01 (forward) | $Kz^{-1}(1 - z^{-1})$ | $K\hat{z}^{-1}$ |
| BP 00 (backward) | $K(1 - z^{-1})$ | $K(1 + \hat{z}^{-1})$ |
| HP | $K(1 - z^{-1})^2$ | K |
| LPN | $K(1 + ez^{-1} + z^{-2}), e > a\sqrt{b}, b > 0$ | $K[1 + \hat{z}^{-1}(2 + e) + (2 + e)\hat{z}^{-2}]$ |
| HPN | $K(1 + ez^{-1} + z^{-2}), e < a\sqrt{b}, b > 0$ | $K[1 + \hat{z}^{-1}(2 + e) + (2 + e)\hat{z}^{-2}]$ |
| AP | $K(b + az^{-1} + z^{-2})$ | |

Advantages



- Have different transfer functions in the z-plane for one transfer function in s-plane.
- Good accuracy. Time constants are implemented with capacitor ratios ($\sim 0.1\%$)
- Don't require a low-impedance output stage (OTA's could be used)
- Could be implemented using digital circuit process technology
- Very useful in the audio range.

NOTATION

Switches

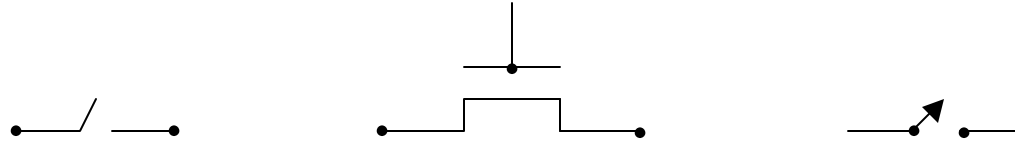


Representation

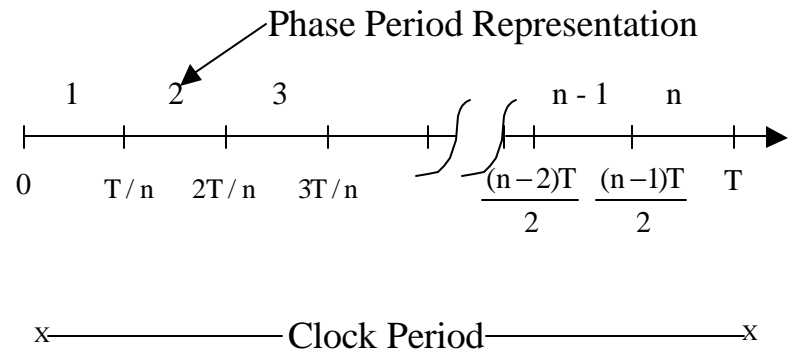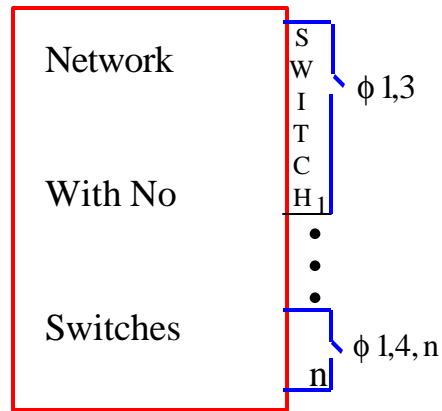


EXAMPLE $n=2$

NON-OVERLAPPING

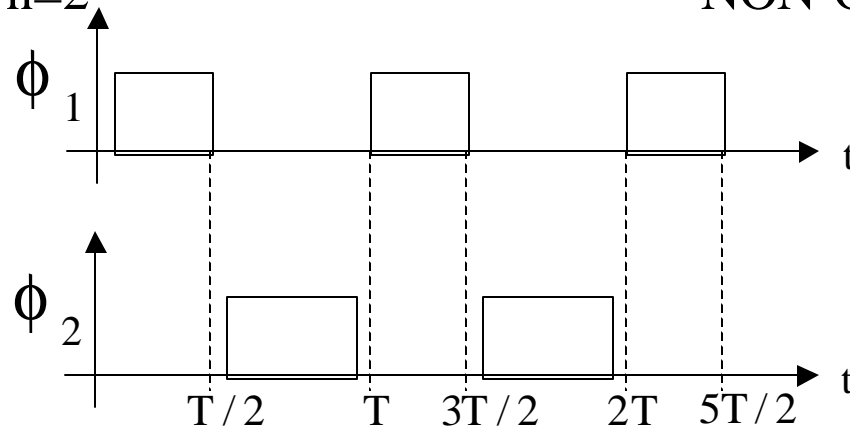

PHASE PERIODS OF A CLOCK SEQUENCE

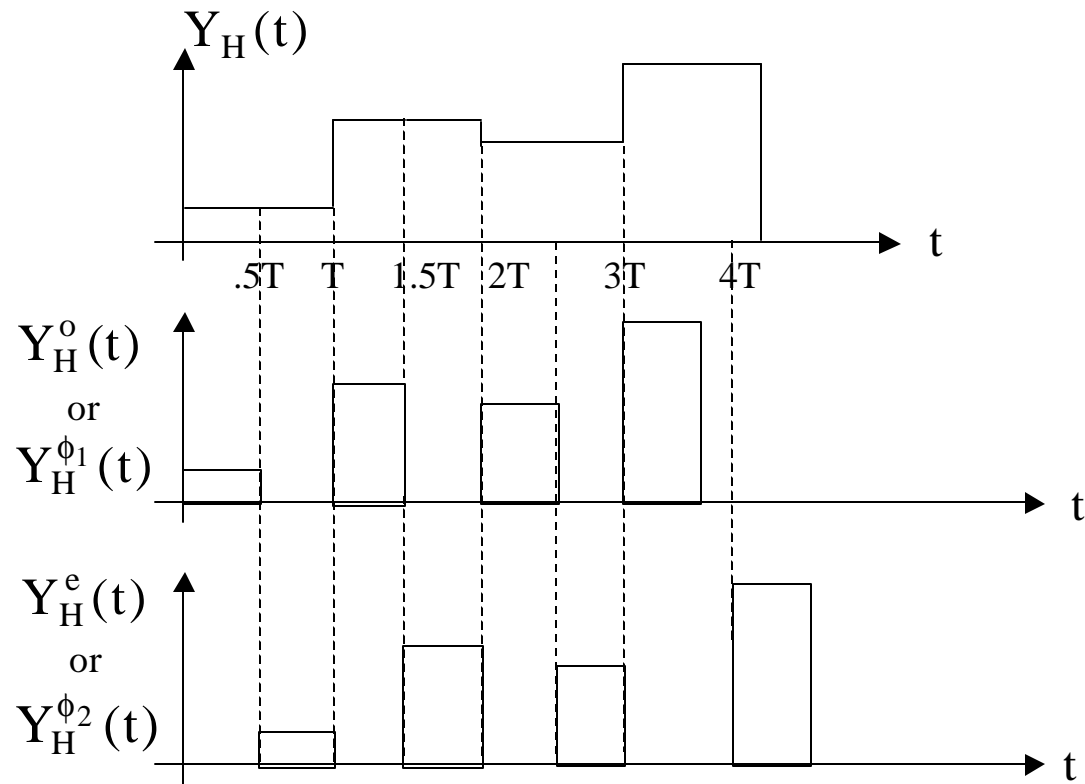


S/H and its respective odd and even components

$$y_H(t) = y_H^o(t) + y_H^e(t)$$

or

$$Y_H(Z) = Y_H^o(Z) + Y_H^e(Z)$$

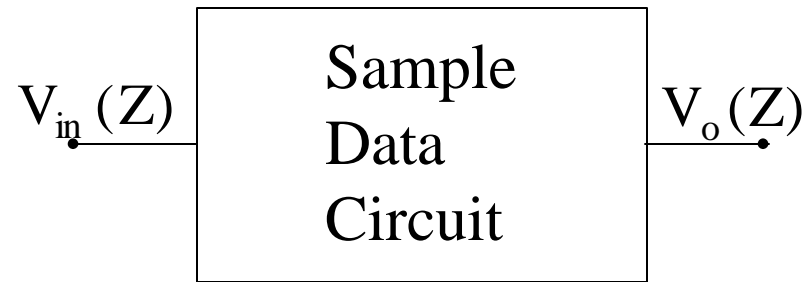

$$V_{in}(Z) = V_{in}^e(Z) + V_{in}^o(Z)$$

$$V_o(Z) = V_o^e(Z) + V_o^o(Z)$$

$$H(Z) = \frac{V_o(Z)}{V_{in}(Z)}$$



CONVENTIONAL NOTATION FOR TRANSFER FUNCTION IS:

$$H^{ij}(Z) = \frac{V_o^j(Z)}{V_{in}^i(Z)}$$


i and j can be either "e" or "o". i.e.,

$$H^{eo}(Z) = \frac{V_o^o(Z)}{V_{in}^e(Z)}$$

TWO-PHASE CLOCK GENERATOR

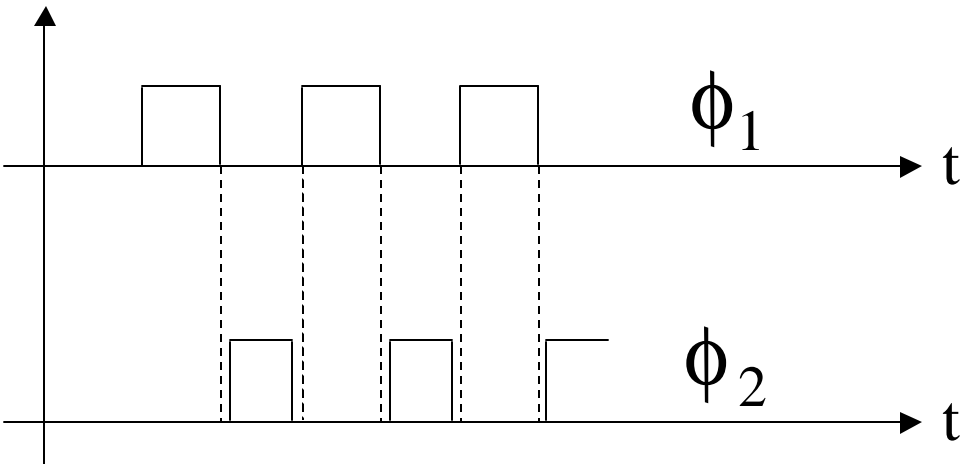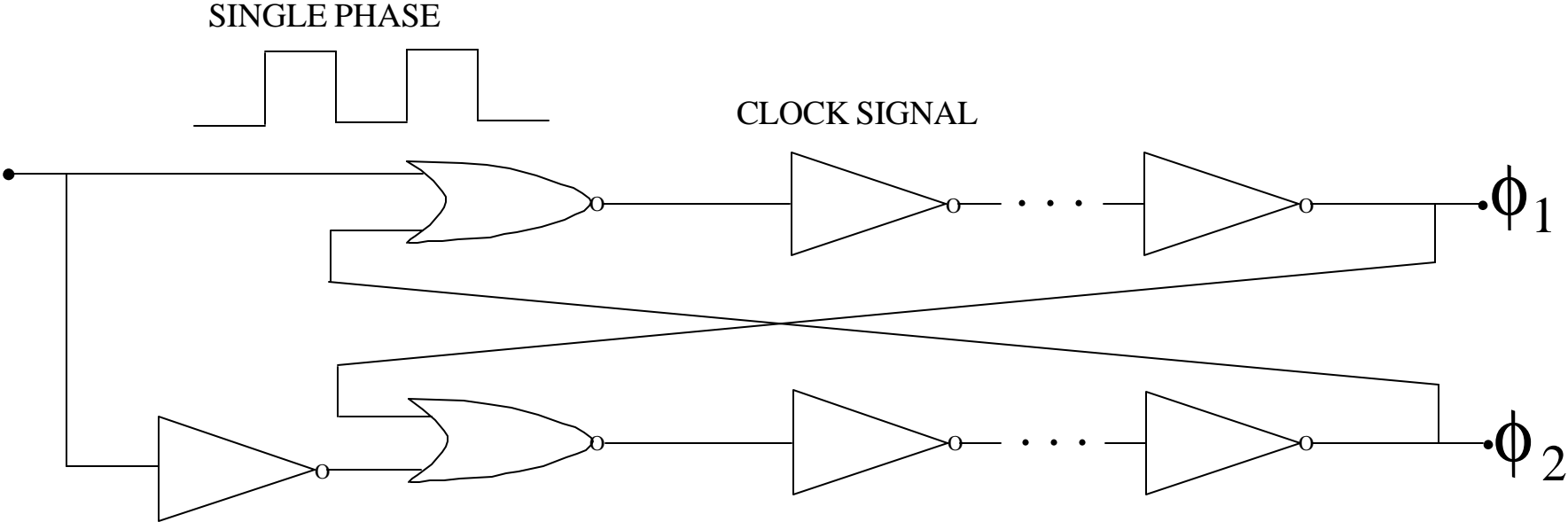



SWITCHED-CAPACITOR EQUIVALENT RESISTOR

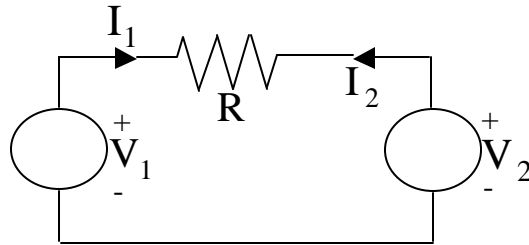

Continuous (Conventional) Resistor


$$R = \frac{V_1 - V_2}{I_1} = \frac{V_2 - V_1}{I_2} \Rightarrow I_2 = \frac{V_2 - V_1}{R}$$

V_1 and V_2 are constant voltage sources

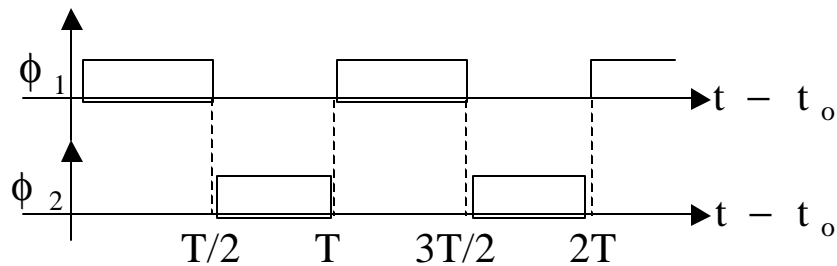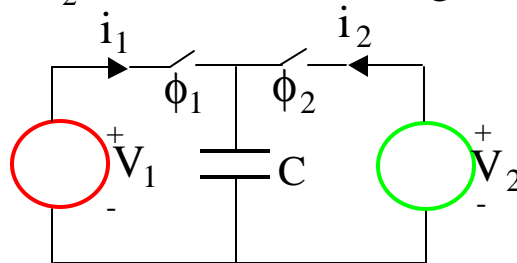


At time $t = t_0$ we apply the clocks.

At ϕ_1

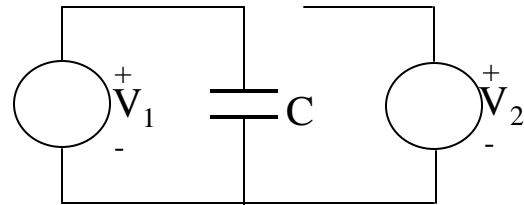

$$Q(t_0 + T/2) = CV_1$$


At ϕ_2

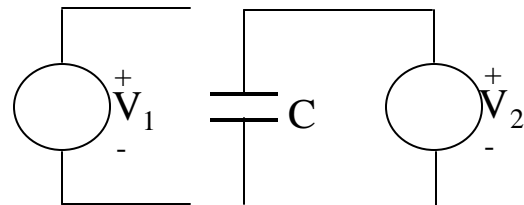

$$Q(t_0 + T) = CV_2 - CV_1$$

$$Q(t_0 + T) = C(V_2 - V_1)$$

For the next period, at ϕ_1

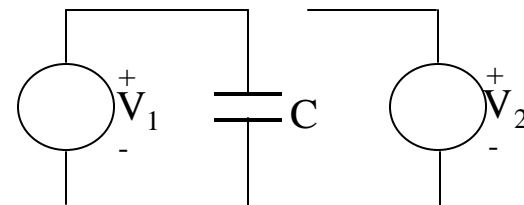

$$Q(t_0 + \frac{3T}{2}) = C(V_1 - V_2)$$

$$i = \frac{dQ}{dt}$$

$$Q_1 = \int_{t_0 + T}^{t_0 + 3T/2} i_1(t) dt = \int_{t_0 + T/2}^{t_0 + 3T/2} i_1(t) dt$$

The average current I_1 (aver) becomes

$$I_1 \text{ (aver) } = \frac{Q \left(t_o + \frac{3T}{2} \right)}{T}$$

$$I_1 \text{ (aver) } = \frac{1}{T} \int_{t_o + 3T/2}^{t_o + 3T/2} i_1(t) dt$$

$$I_1 \text{ (aver) } = \frac{C (V_1 - V_2)}{T} = \frac{\Delta Q}{\Delta t}$$

or

$$\frac{T}{C} = \frac{V_1 - V_2}{I_1 \text{ (aver)}}$$

Comparing with the continuous time resistor

$$\text{Blue Arrow} \rightarrow R_{eq} = \frac{T}{C} = \frac{1}{f_C C} \leftarrow \text{Grey Arrow}$$

EXAMPLE. $R = 250K\Omega$, $f_C = 128KHz$

$$\left(\frac{A_R}{A_C} \cong 32 \right) \leftarrow \text{Grey Arrow} \quad C = \frac{1}{R_{eq} f_C} = \frac{1}{250 \times 128 \times 10^6} = 31.25pF$$

| | | |
|------|--------------|--------------------------|
| | Continuous R | “SC-R” |
| AREA | 5,776 | 178.57 mils ² |

ACCURACY OF TIME CONSTANTS

● CONTINUOUS TIME:

$$\tau = R_1 C_2$$

$$\frac{d\tau}{\tau} = \frac{dR_1}{R_1} + \frac{dC_2}{C_2} \rightarrow \pm 40\% \rightarrow \pm 65\%$$

where $\frac{d\tau}{\tau}$ is interpreted as the accuracy of τ .

TEMPERATURE DEPENDANT!

● DISCRETE TIME:

$$\tau = \frac{1}{f_C C_1} \cdot C_2 = T \left(\frac{C_2}{C_1} \right)$$

$$\frac{d\tau}{\tau} = \frac{dT}{T} + \frac{dC_2}{C_2} - \frac{dC_1}{C_1}$$


$$\frac{d\tau}{\tau} \cong \frac{dC_2}{C_2} - \frac{dC_1}{C_1} \rightarrow 0.1\%$$



KC_HL KIRCHOFF "CHARGE" LAW

$$\sum_{i=1}^n Q_i = 0$$

$$Q_j = C_j V_{C_j}$$

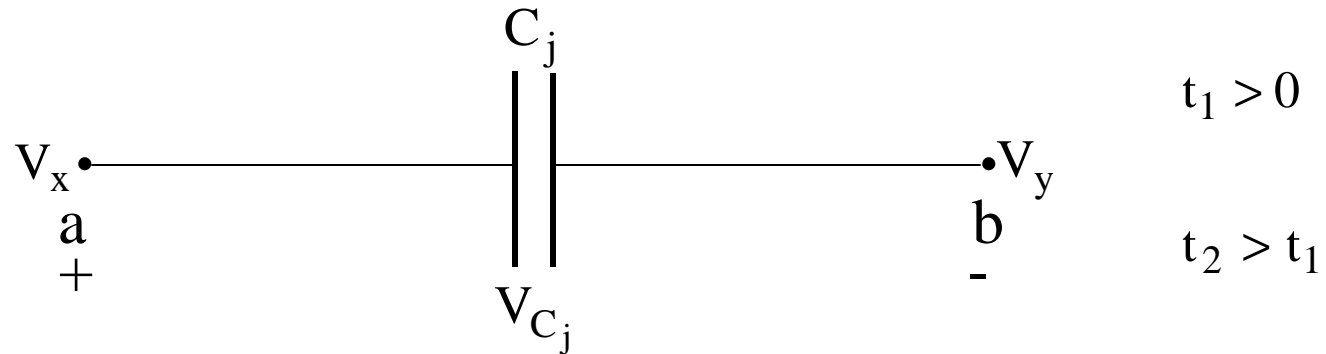


at $t = t_2$

$$V_{C_j} = V_x(t_2) - V_y(t_2) - (V_x(t_1) - V_y(t_1))$$


Voltage across the capacitor V_{C_j} = voltage difference (at present time) across the capacitor minus initial condition (at past time).

CHARGE CONSERVATION ANALYSIS METHOD

$$q_L(n) = q_M(n-1) + \hat{q}_C(n)$$

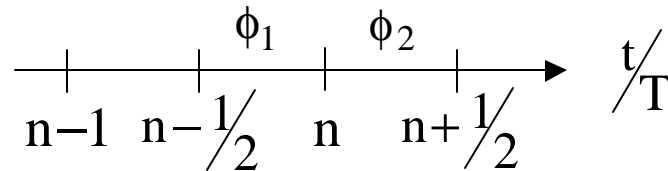

Example

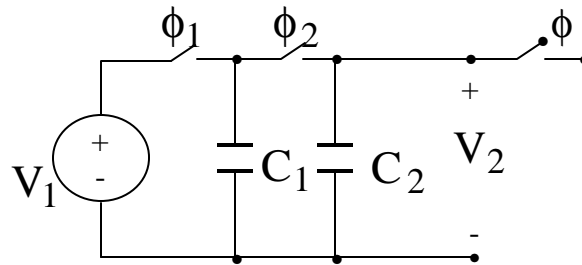

for ϕ_2

$$C_2[V_2^e(n) - V_2^o(n - \frac{1}{2})] + C_1[V_2^e(n) - V_1^o(n - \frac{1}{2})] = 0$$

for ϕ_1

$$C_2[V_2^o(n - \frac{1}{2}) - V_2^e(n-1)] = 0 \Rightarrow V_2^o(n - \frac{1}{2}) = V_2^e(n-1)$$

THEN

$$C_1 v_2^o(n) + C_2 v_2^o(n) = C_2 v_2^o(n-1) + C_1 v_1^o(n-1)$$

$$(C_1 + C_2) V_2^o(Z) - C_2 Z^{-1} V_2^o(Z) = C_1 V_1^o(Z) Z^{-1}$$

$$H^{oo}(Z) = \frac{\frac{C_1}{C_1} Z^{-1}}{\frac{C_1 + C_2}{C_1} - \frac{C_2}{C_1} Z^{-1}} = \frac{Z^{-1}}{1 + \alpha - \alpha Z^{-1}}$$

$$H^{oo}(Z) = \frac{\frac{C_1}{C_1} Z^{-1}}{\frac{C_1 + C_2}{C_1} - \frac{C_2}{C_1} Z^{-1}} = \frac{Z^{-1}}{1 + \alpha - \alpha Z^{-1}}$$

$$H^{oo}(Z) = \frac{V_o^o(Z)}{V_{in}^o(Z)} = \frac{V_o^e(Z) Z^{-1/2}}{V_{in}^o(Z)}$$

$$V_2^e(n) = V_2^e(n + 1/2)$$

$$C_2[V_2^o(n + 1/2) - V_2^o(n - 1/2)] + C_1[V_2^o(n + 1/2) - V_1^o(n - 1/2)]$$

$$C_2[V_2^o(Z)][Z^{1/2} - Z^{-1/2}] + C_1V_2^o(Z)Z^{1/2} = C_1V_1^o(Z)Z^{-1/2}$$

$$C_2(1 - Z^{-1})V_2^o(Z) + C_1V_2^o(Z) = C_1V_1^o(Z)Z^{-1/2}$$

$$\frac{V_2^o(Z)}{V_1^o(Z)} = \frac{C_1Z^{-1}}{C_2(1 - Z^{-1}) + C_1} = \frac{C_1Z^{-1}}{C_2 + C_1 - C_2Z^{-1}}$$

$$\frac{V_2^o(Z)}{V_1^o(Z)} = \frac{C_1}{(C_2 + C_1)Z - C_2} \bigg|_{Z \cong 1 + ST} = \frac{C_1}{(C_2 + C_1) + (C_2 + C_1)ST - C_2}$$

For high-sampling rate $\omega T \ll 1$

$$\frac{V_2^o(Z)}{V_1^o(Z)} \bigg|_{Z = 1 + sT} = \frac{C_1}{C_1 + (C_2 + C_1)sT} = \frac{1}{1 + \left(\frac{C_2 + C_1}{C_1}\right)sT} = \frac{1}{1 + \frac{s}{\frac{C_1}{(C_2 + C_1)T}}}$$

$$f_{3dB} \cong \frac{1}{2\pi} \cdot \frac{C_1}{(C_2 + C_1)T} = \frac{1}{2\pi} \cdot \frac{f_c}{1 + \frac{C_2}{C_1}}$$


Aside:

$$f_{3dB} \cong \frac{1}{2\pi} \cdot \frac{1}{R_1C_2} \cong \frac{1}{2\pi} \cdot \frac{1}{\frac{TC_2}{C_1}} = \frac{1}{2\pi} \cdot \frac{f_c}{\frac{C_2}{C_1}}$$


Switched-Capacitor (SC) Filters

How to design SC Filters ?

- Two basic approaches

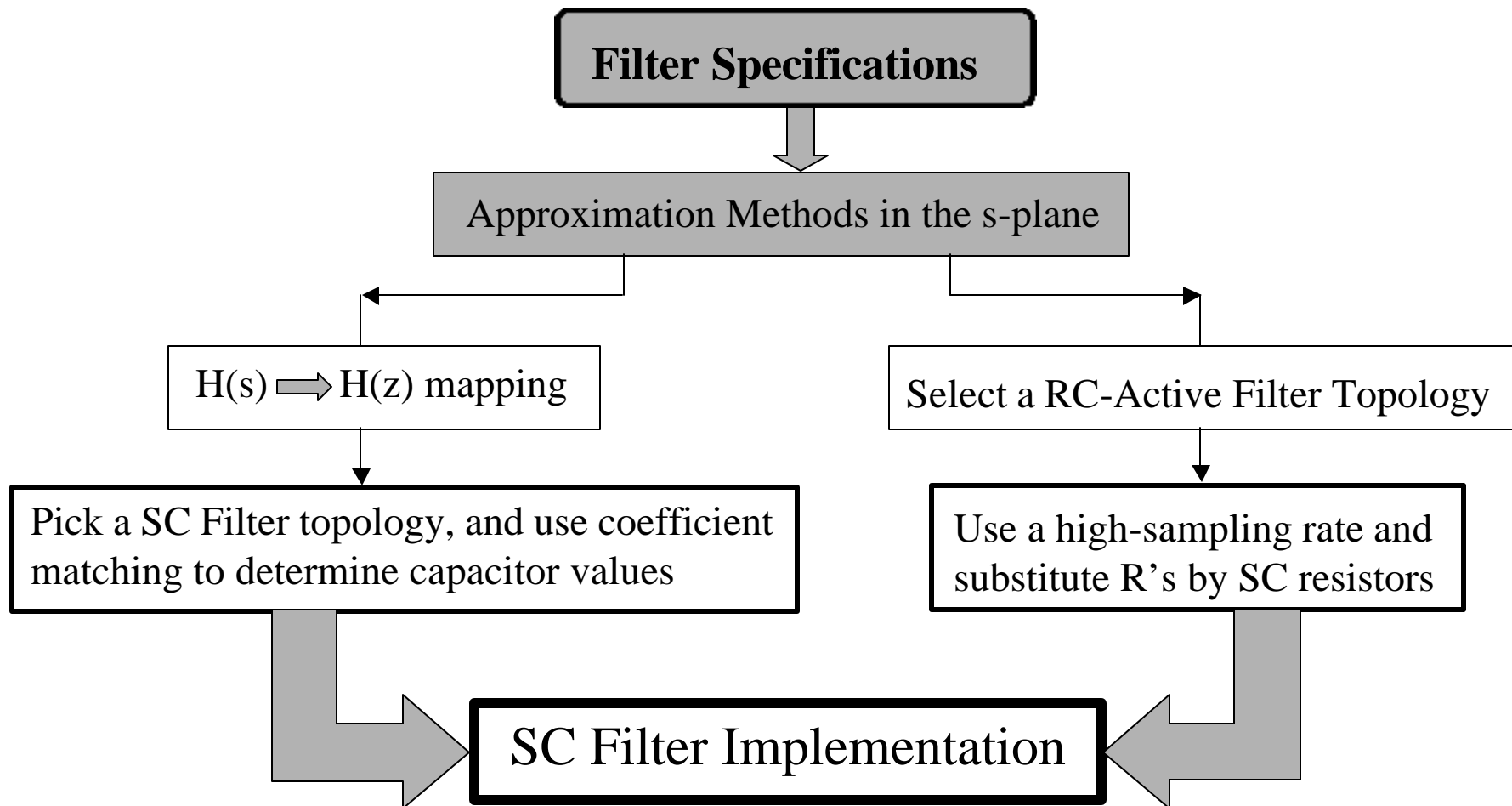

Systematic SC Filter Design

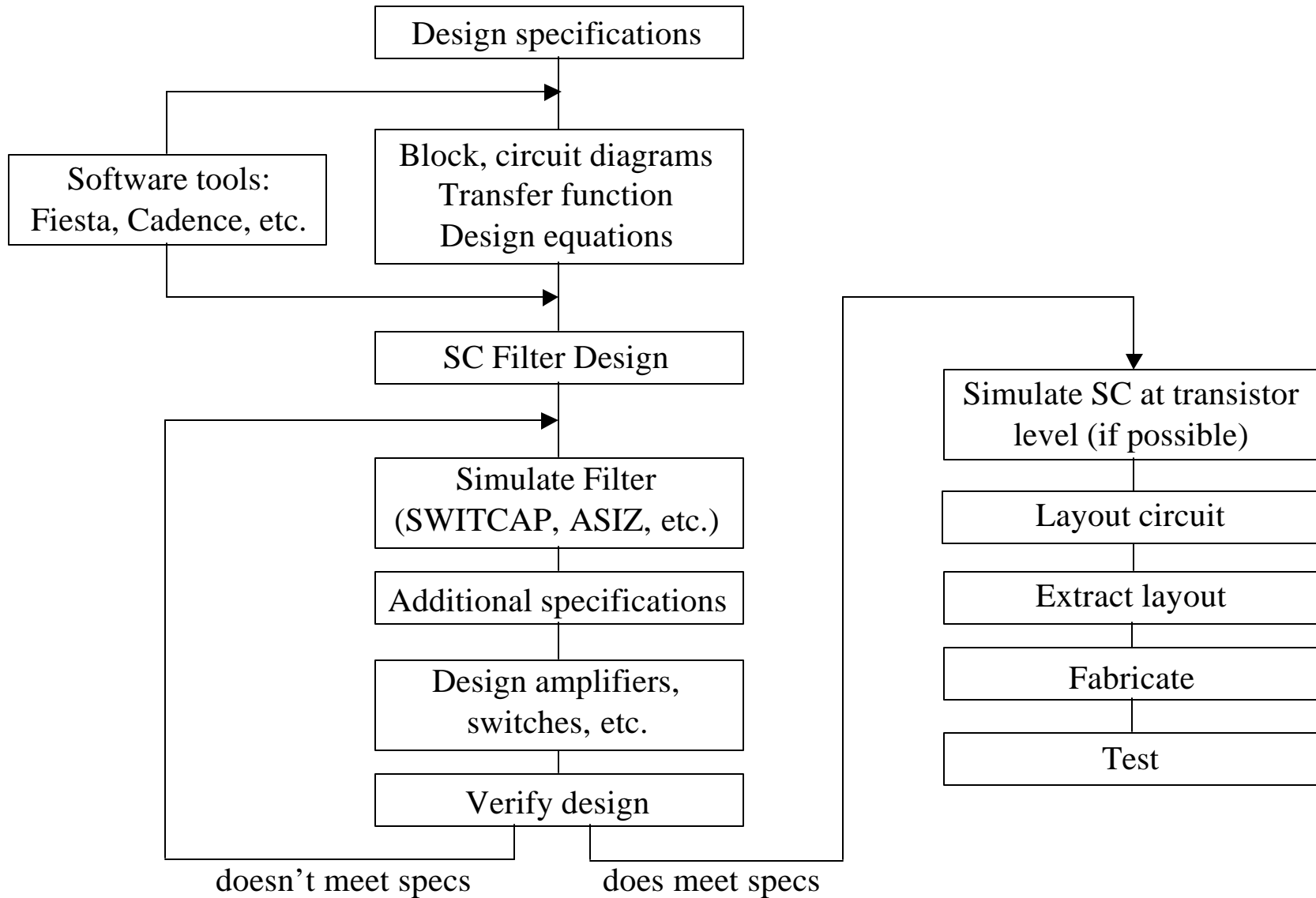

What are the advantages and disadvantages of the two filter design procedures ?

- Mapping Techniques

- + Systematic and well documented (see FIESTA-2)
- + It can use any sampling rate, including the (minimum) Nyquist rate.
- Difficult to implement by hand calculation

- Transforming R to SC resistors


- + It is, conceptually, easier to follow for analog designer
- + Its design is straightforward
- Yields not an optimal design for area, imposed high sampling rate involves larger capacitor ratios.

BASIC BUILDING BLOCKS

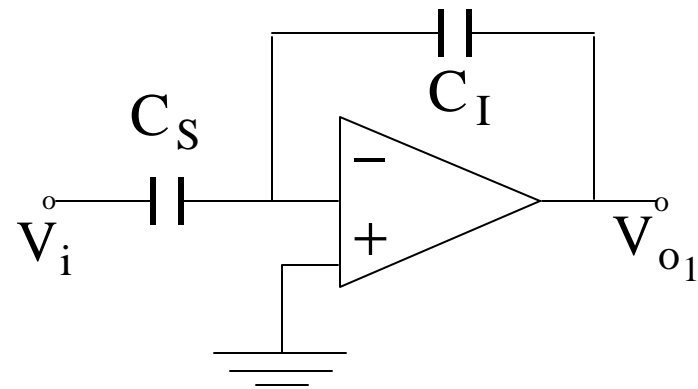A. GAIN AMPLIFIERS

Basic Configuration:


- Compact, versatile & time continuous
- Lacks dc feedback
 - Op amp is not stabilized
 - Leakage current saturates the circuit



$$\text{Gain} = -\frac{C_S}{C_I}$$

Improved Gain Amplifier

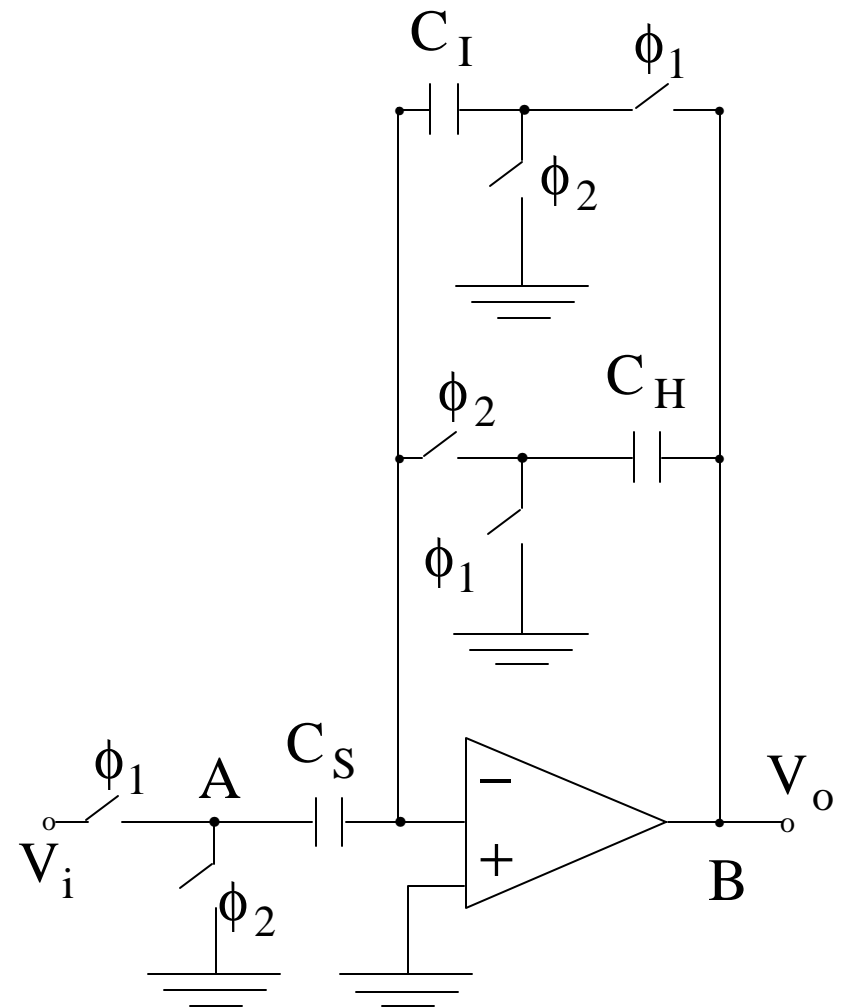- Low sensitivity to the op amp offset voltage and open loop gain (due to charge cancellation)
- Additional capacitor (not shown in Fig.) between nodes A and B eliminates the “spikes” during the non-overlapping clock phases




$$\text{gain} = -\frac{C_S}{C_I}$$


B. Integrators

Conventional stray-insensitive integrators:


• Non-inverting:

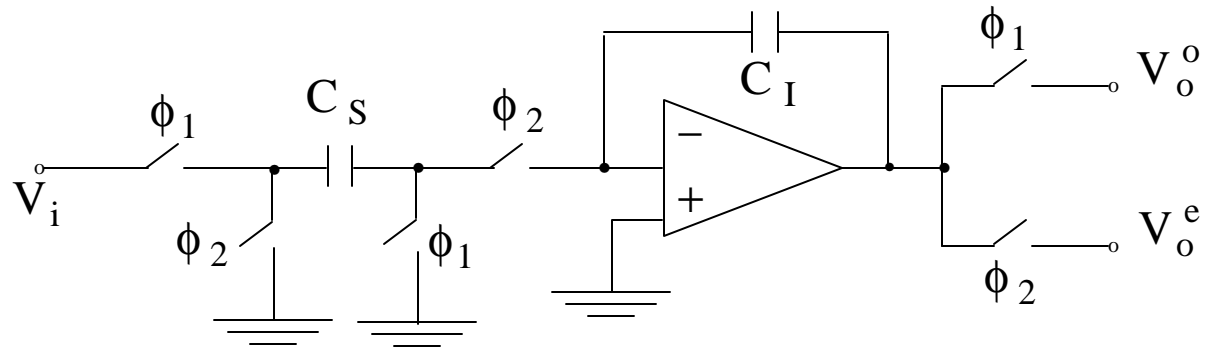


• Inverting:

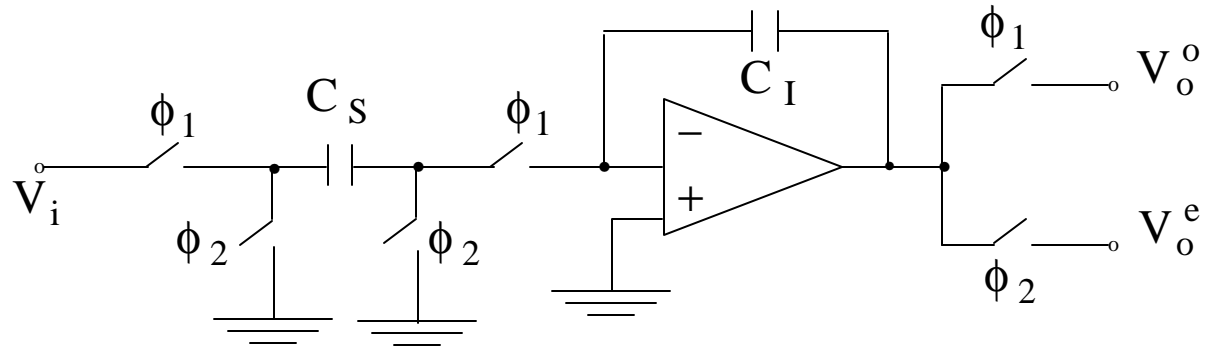

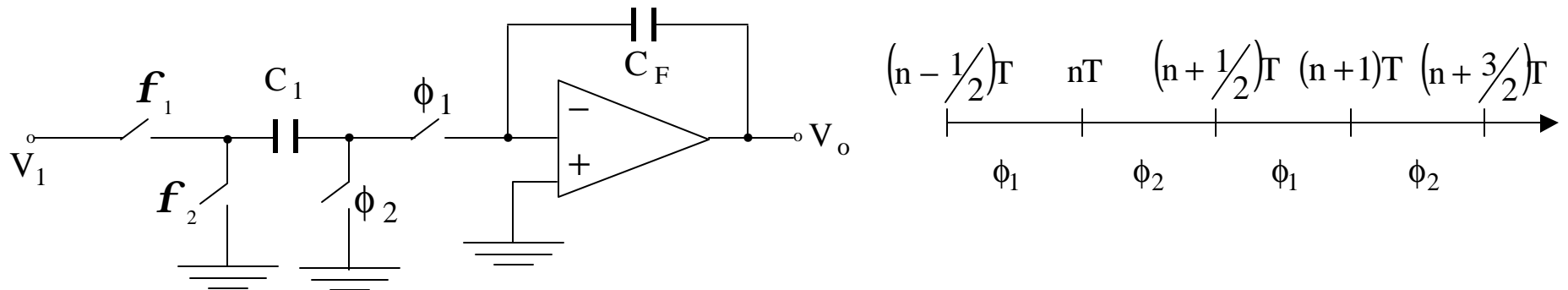Example of SC Analysis: An Inverting Integrator



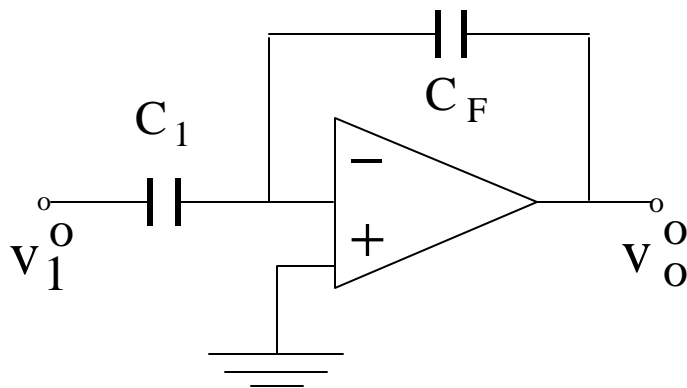During f_1 (odd clock phase) at $(n-1/2) \leq t/T < n$




$$v_{C_1} = v_1^o \left(n - \frac{1}{2} \right) T - 0$$

$$v_{C_F} = v_o^o \left(n - \frac{1}{2} \right) T - v_o^e (n-1) T$$

$$C_1 v_{C_1} + C_F v_{C_F} = C_1 v_1^o \left(n - \frac{1}{2} \right) T + C_F v_o^o \left(n - \frac{1}{2} \right) T - C_F v_o^e (n-1) T = 0 \quad (1)$$

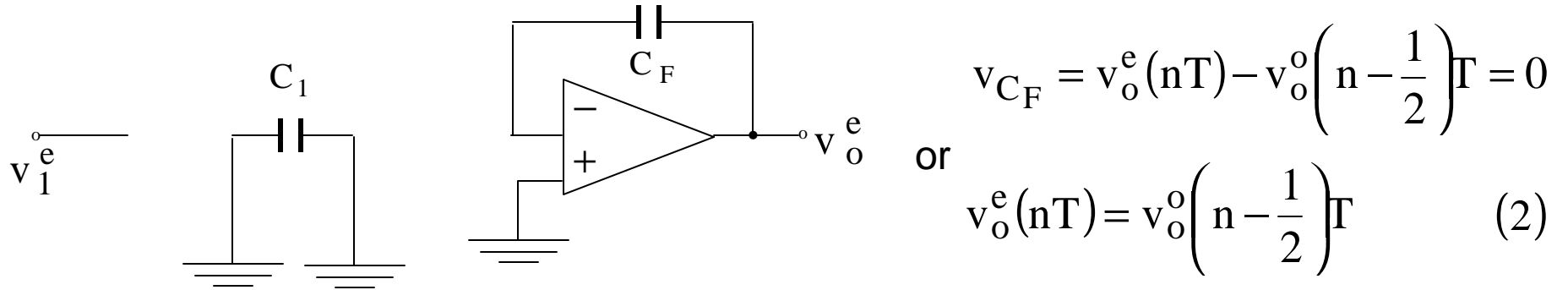During f_2 (even clock phase) at $n \leq t/T < n + 1/2$



Applying z- transform to both (1) and (2) one obtain





$$C_1 z^{-1/2} V_1^o(z) + C_F z^{-1/2} V_o^o(z) - C_F V_o^e(z) z^{-1} = 0 \quad (3)$$

$$V_o^e(z) = z^{-1/2} V_o^o(z) \quad (4)$$


Solving (3) and (4)

$$C_1 V_1^o(z) + C_F V_o^o(z) - C_F z^{-1} V_o^e(z) = 0$$

$$H^{oo}(z) = \frac{V_o^o(z)}{V_1^o(z)} = \frac{-C_1/C_F}{1 - z^{-1}} \quad ; \quad H^{oe}(z) = \frac{V_o^e(z)}{V_1^o(z)} = \frac{-C_1/C_F z^{-1/2}}{1 - z^{-1}}$$
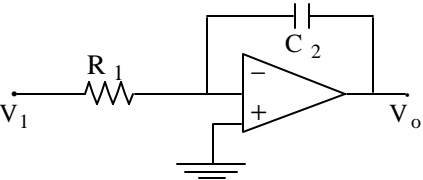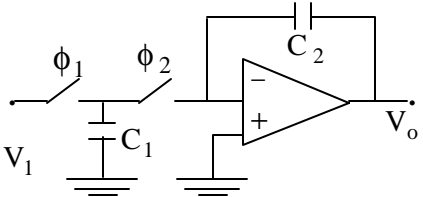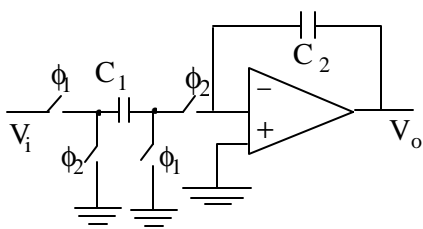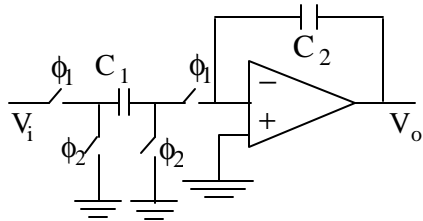
| Type of Integrator | Magnitude, $ H(e^{j\omega T}) $ | Phase, $A_{RG}H(e^{j\omega T})$ | Mapping (Equivalent) | Transfer Function |
|--|---|---------------------------------------|----------------------|--|
|  | $\frac{\omega_o}{\omega}$ | $\frac{\pi}{2}$ | In the s-Plane | i.e. $H(S) = \frac{1}{SR_1C_2} = -\frac{\omega_o}{S}$ |
|  <p>Inverting Stray-sensitive (Forward)</p> | For V_o at ϕ_2 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$ | $\frac{\pi}{2}$ | LDI | $H(Z) = -\frac{C_1}{C_2} \left(\frac{Z^{-1/2}}{1-Z^{-1}} \right)$ |
| | For V_o at ϕ_1 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$ | $\frac{\pi}{2} - \frac{\omega T}{2}$ | Forward | $H(Z) = -\frac{C_1}{C_2} \left(\frac{Z^{-1}}{1-Z^{-1}} \right)$ |
|  <p>Non-Inverting</p> | For V_o at ϕ_2 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$ | $-\frac{\pi}{2}$ | LDI | $H(Z) = \frac{C_1}{C_2} \left(\frac{Z^{-1/2}}{1-Z^{-1}} \right)$ |
| | For V_o at ϕ_1 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$ | $-\frac{\pi}{2} - \frac{\omega T}{2}$ | Forward | $H(Z) = \frac{C_1}{C_2} \left(\frac{Z^{-1}}{1-Z^{-1}} \right)$ |
|  <p>Inverting (Backward)</p> | For V_o at ϕ_1 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$ | $\frac{\pi}{2} + \frac{\omega T}{2}$ | Backward | $H(Z) = -\frac{C_1}{C_2} \left(\frac{1}{1-Z^{-1}} \right)$ |
| | For V_o at ϕ_2 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$ | $\frac{\pi}{2}$ | LDI | $H(Z) = -\frac{C_1}{C_2} \left(\frac{Z^{-1/2}}{1-Z^{-1}} \right)$ |

DC OPEN LOOP GAIN A_o EFFECTS

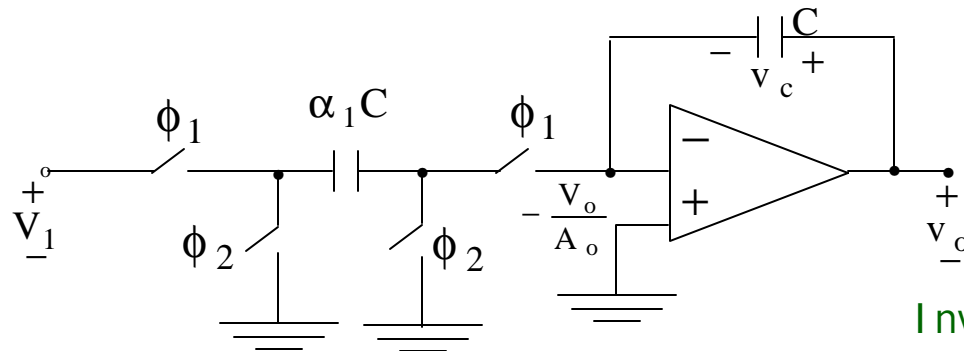

f_1 Odd Phase f_2 Even Phase i) During $f_1 \left(n - \frac{1}{2} \right) < \frac{t}{T} \leq n$:

$$v_C^o(n) = v_o^o(n) + \frac{v_o^o(n)}{A_o} \quad (1)$$

Furthermore $\sum_{i=1}^2 Q_i = 0$

$$\alpha_1 C v_{\alpha_1 C}^o + C v_C^o = 0$$

$$\alpha_1 \left[v_1^o(n) + \frac{v_o^o(n)}{A_o} \right] + v_C^o(n) - v_C^e \left(n - \frac{1}{2} \right) = 0 \quad (2)$$

ii) During $f_2 \left(n - 1 \right) < \frac{t}{T} \leq \left(n - \frac{1}{2} \right)$

$$v_C^e \left(n - \frac{1}{2} \right) = v_o^e \left(n - \frac{1}{2} \right) + \frac{v_o^e \left(n - \frac{1}{2} \right)}{A_o} \quad (3)$$

Eqs (3) and (1) into (2) yields

$$\alpha_1 \left[v_1^o(n) + \frac{v_o^o(n)}{A_o} \right] + v_o^o(n) \left(1 + \frac{1}{A_o} \right) - v_o^e \left(n - \frac{1}{2} \right) \left(1 + \frac{1}{A_o} \right) \quad (2')$$

Note that

$$v_o^e \left(n - \frac{1}{2} \right) = v_o^o(n-1) \quad (4)$$

Substituting (4) into (2') and taking the Z- Transform we obtain


$$-\alpha_1 V_1^o(Z) = \frac{\alpha_1 V_o^o(Z)}{A_o} + \left(1 + \frac{1}{A_o} \right) (1 - Z^{-1})$$

$$H^{oo}(Z) = \frac{V_o^o(Z)}{V_1^o(Z)} = \frac{-\alpha_1}{\frac{\alpha_1}{A_o} + \left(1 + \frac{1}{A_o} \right) (1 - Z^{-1})} = \frac{-\alpha_1}{\frac{\alpha_1}{A_o} + \frac{1}{A_o} + 1 - Z^{-1} \left(1 + \frac{1}{A_o} \right)}$$


$$H^{oo}(Z) = \frac{V_o^o(Z)}{V_1^o(Z)} = \frac{\frac{-\alpha_1}{1 + \frac{1}{A_o} (1 + \alpha_1)}}{1 - Z^{-1} \frac{1 + \frac{1}{A_o}}{\frac{\alpha_1}{A_o} + \frac{1}{A_o} + 1}} \Bigg|_{A_o \rightarrow \infty} = \frac{-\alpha_1}{1 - Z^{-1}}$$

Actual pole located at

$$Z_p = \frac{1 + \frac{1}{A_o}}{1 + \frac{1}{A_o}(\alpha_1 + 1)} \Big|_{A_o \rightarrow \infty} = 1$$

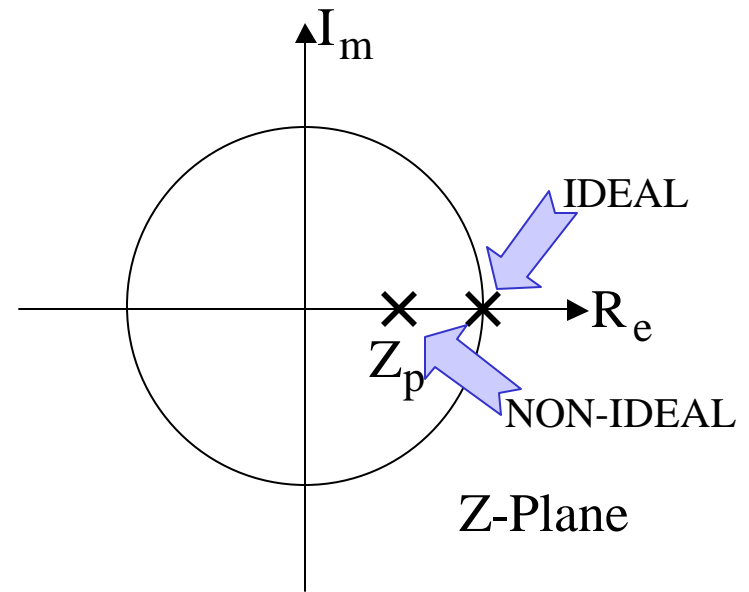


$$|H^{oo}(Z)| = \left| \frac{\alpha_1 e^{\omega T/2}}{2j \text{sen}(\omega T/2)} \frac{1}{1 + \frac{1}{A_o} \left(1 + \frac{\alpha}{2}\right) - j \frac{\alpha}{A_o \tan(\omega T/2)}} \right|$$

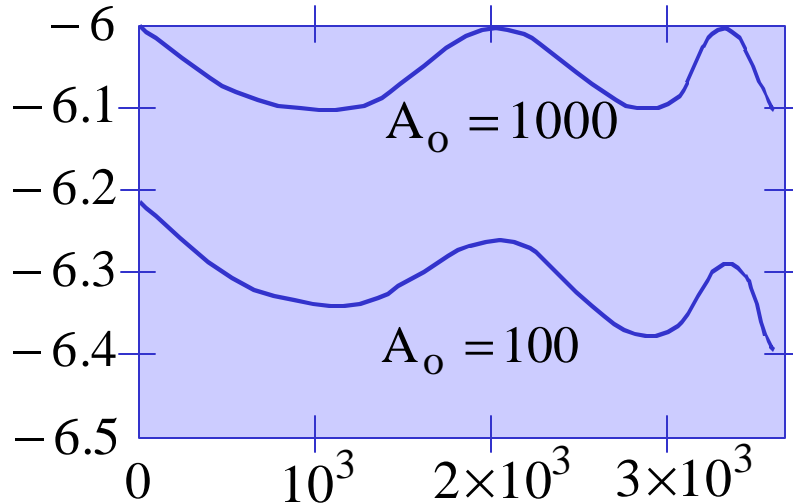


EXAMPLE
5th Order
Chebyshev

Basic SC first-order low-pass

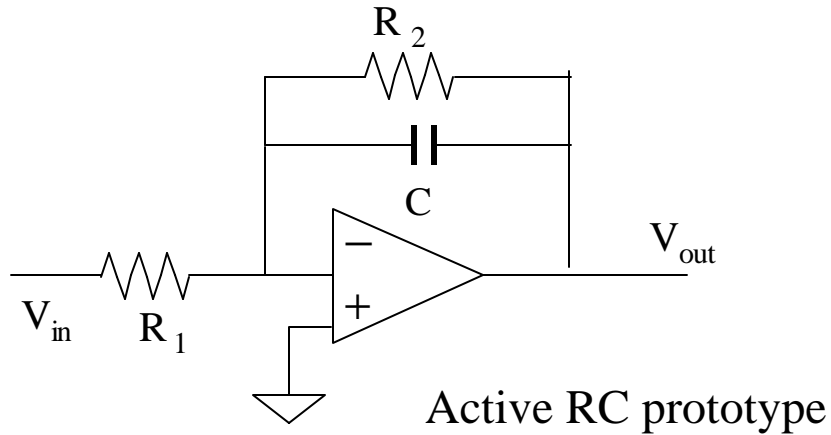

$$H(s) = \frac{-R_2/R_1}{1 + sCR_2}$$

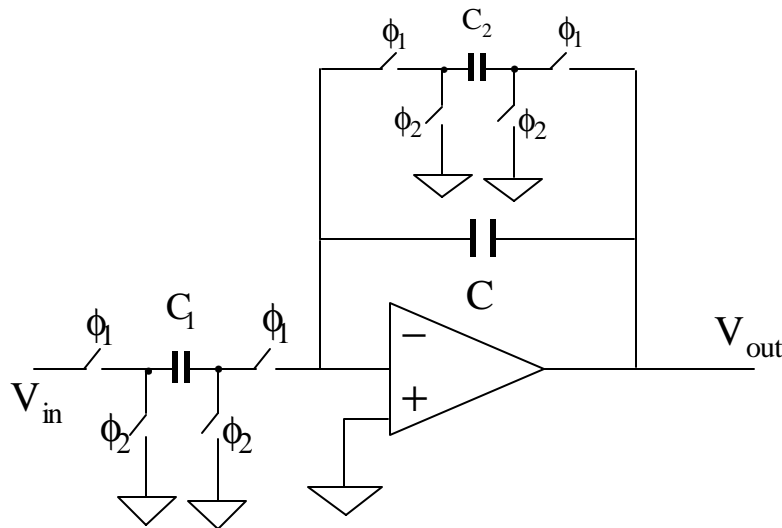


$$R_{eq} = T / C_i = 1 / C_i f_S, \quad i = 1, 2$$

$$H(z) = \frac{-(C_1 / C)z}{z(1 + C_2 / C) - 1}$$

$$Z_{zero} = 0$$


$$Z_{pole} = 1 / (1 + C_2 / C)$$

Block Diagram representation

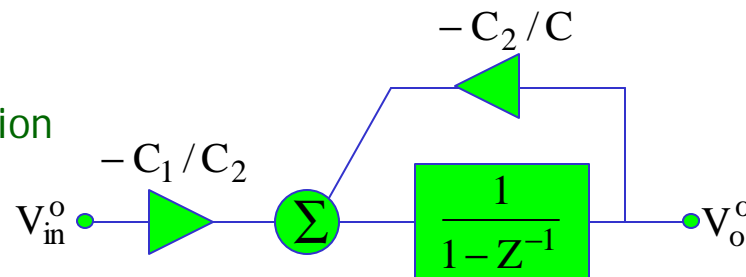

Offset and gain compensated Integrator

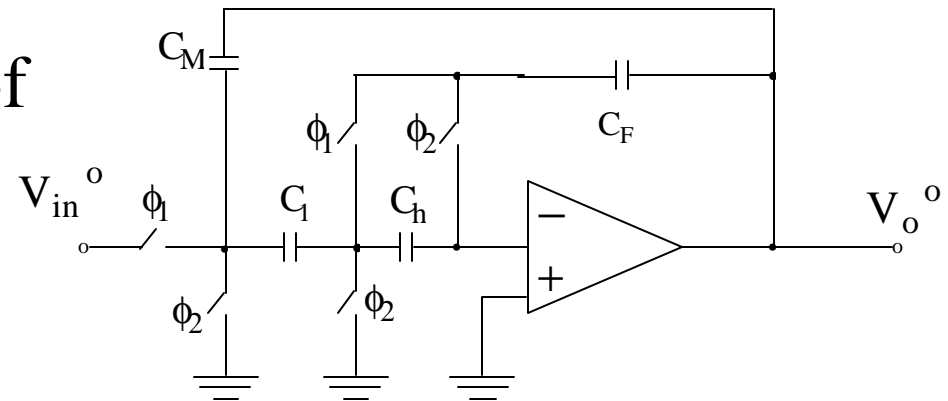
- C_h compensates the offset voltage and dc gain error of the op amp
- C_M eliminates spikes (providing continuous feedback to the op amp)




$$H^{oo}(z) = \frac{V_o^o(z)}{V_{in}^o(z)} = -\frac{C_1}{C_F} \frac{1}{1-z^{-1}}$$

Biquad Circuits & Block Diagrams

Circuit Diagram

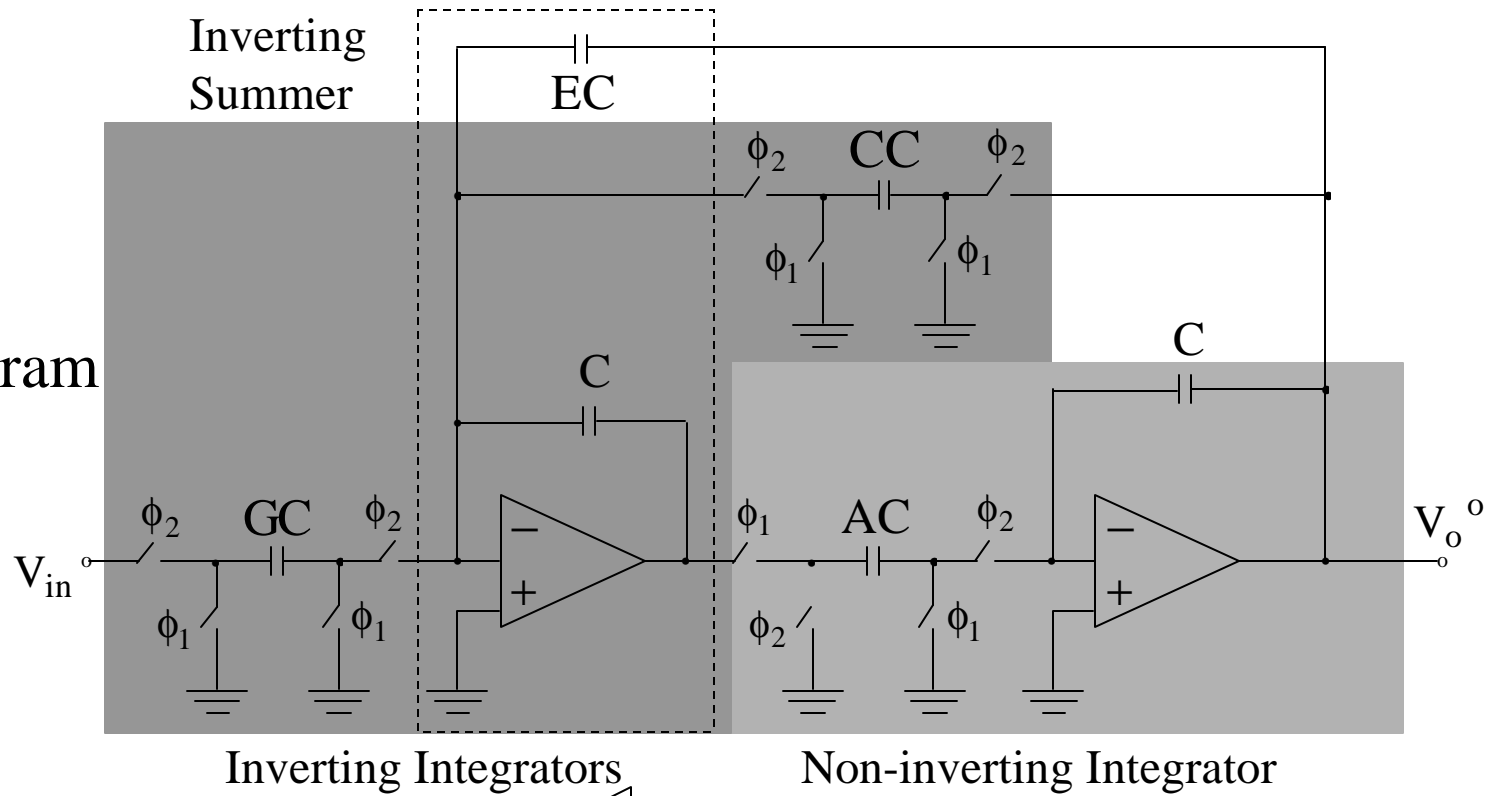


Block Diagram

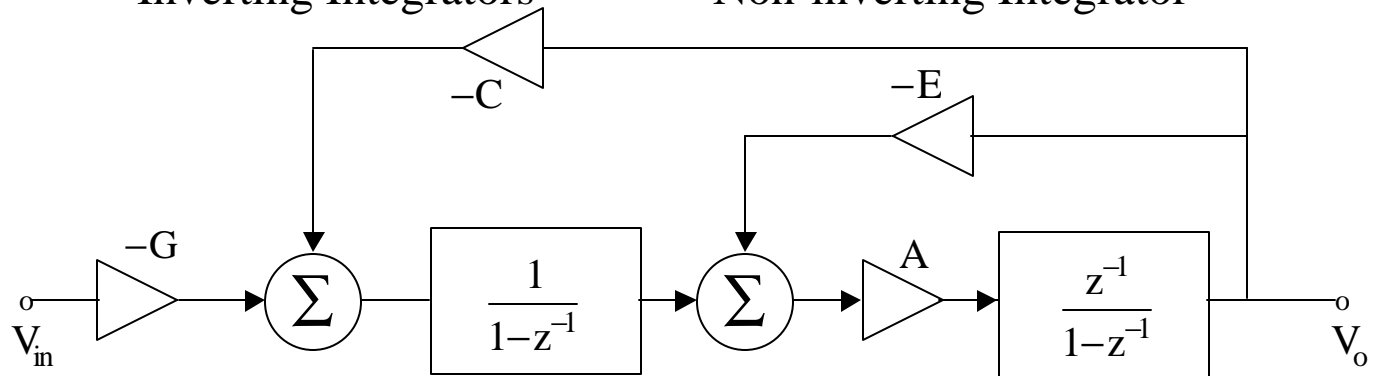

Biquad Circuit 1

Circuit Diagram

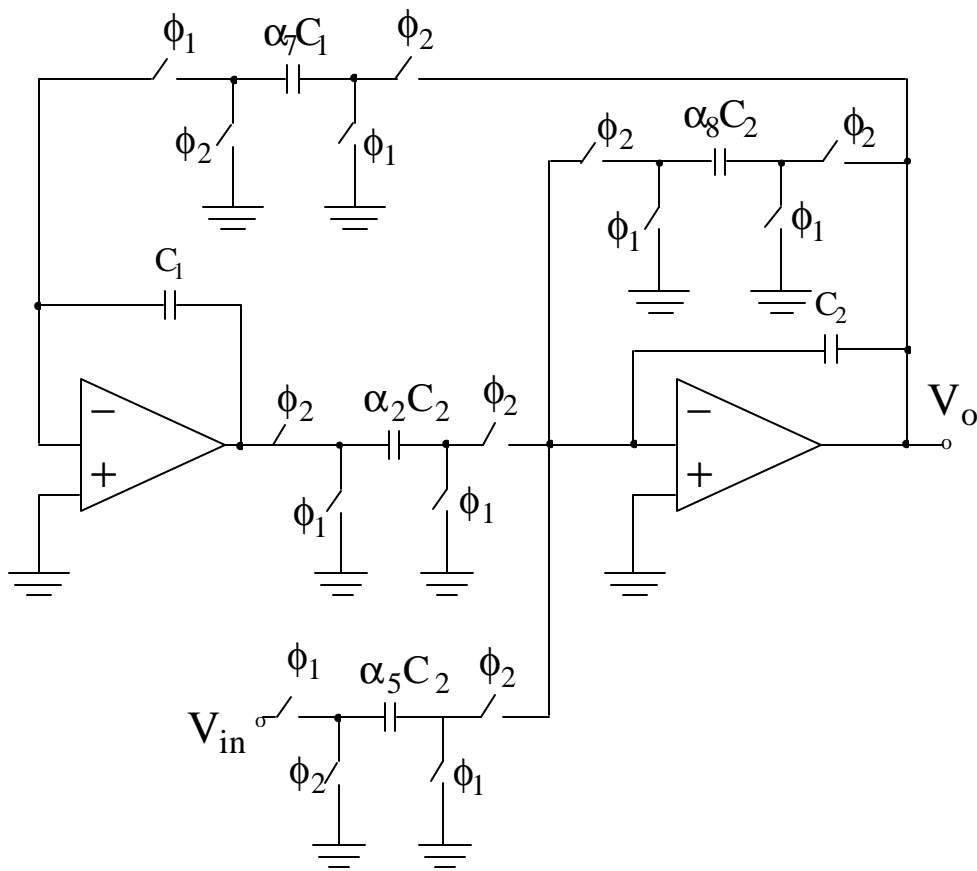


Block Diagram


Biquad Circuit 2

Block Diagram


Circuit Diagram

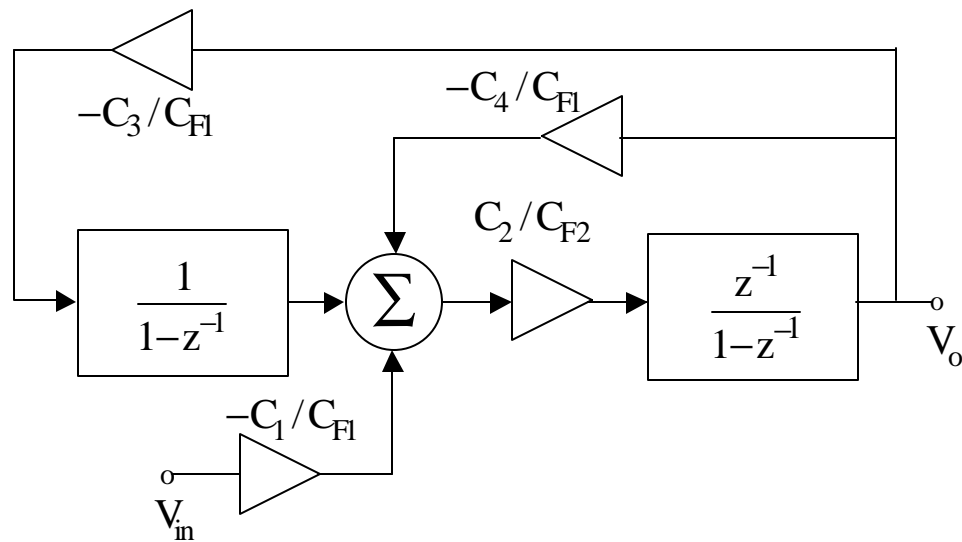

?

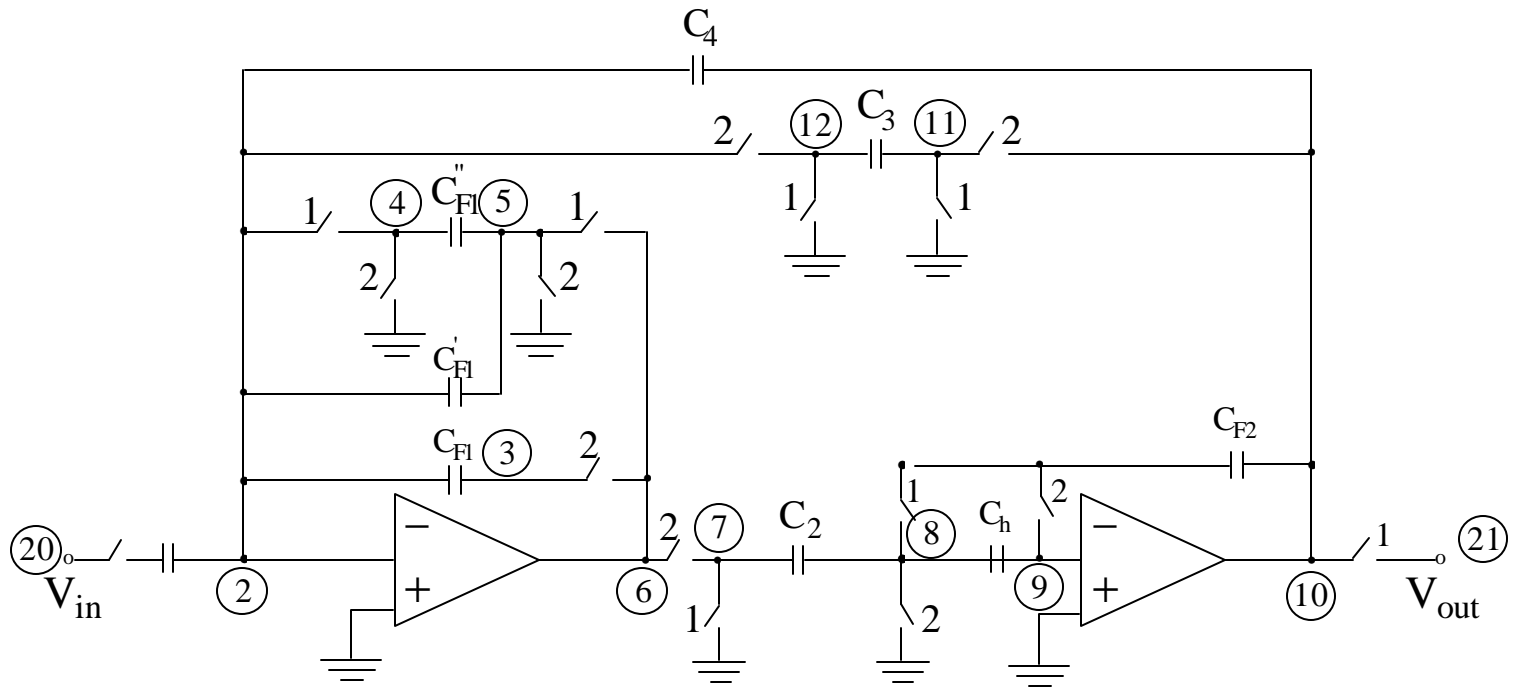

SC Bandpass Diagram

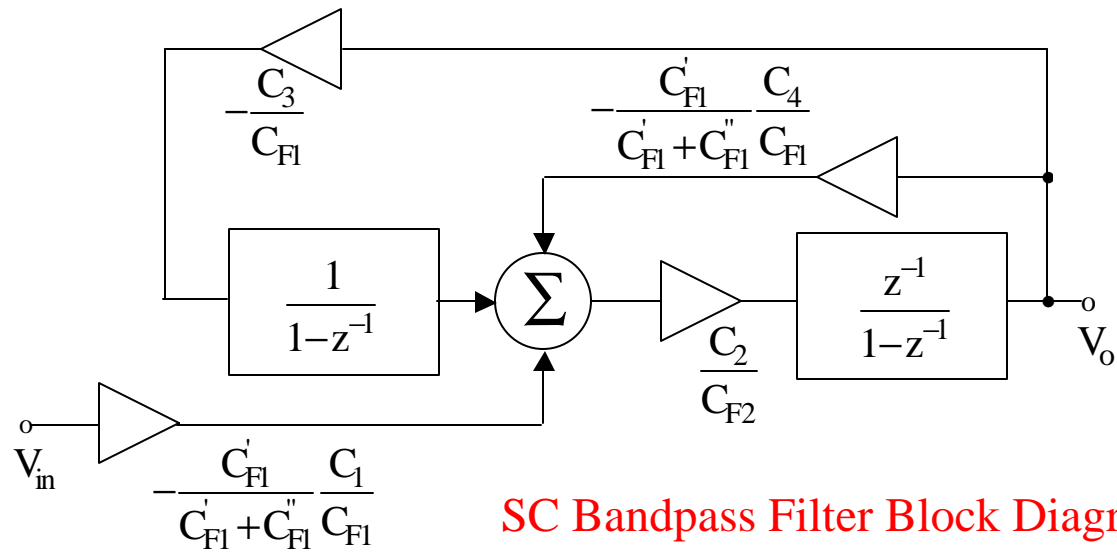

SC Bandpass Filter Block Diagram

SWITCAP INPUT FILE

```
timing;
period 2e-5;
clock clk 1 (0
1/2);
clock rq 1/100 (0
1/200);
end;

subckt (1 2 3 4)
opamp (P:a0);
e1 (5 0 3 4) 1;
e2 (1 2 8 0) a0;
s1a (5 6) rq;
s1b (8 6) #rq;
s2a (8 7) rq;
s2b (5 7) #rq;
ceq (6 7) 14.03;
cp (8 0) 10000;
end;

circuit;
c1 (1 2) 2.2;
cf1 (2 3) 5.4;
cf11 (2 5) 1.1;
cf12 (4 5) 3;
c2 (7 8) 1;
c3 (11 12) 1;
c4 (2 10) 1;
cf2 (13 10) 5.4;
ch (8 9) 1;
xe1 (6 0 0 2)
opamp (28000);
xe2 (10 0 0 9)
opamp (28000);
s1 (20 1) clk;
s2 (3 6) #clk;
s3 (5 0) #clk;
s4 (5 6) clk;
s5 (4 0) #clk;
s6 (2 4) clk;
s7 (6 7) #clk;
s8 (7 0) clk;
s9 (8 0) #clk;
s10 (8 13) clk;
s11 (9 13) #clk;
s12 (21 10) clk;
s13 (11 10) #clk;
s14 (11 0) clk;
s15 (12 2) #clk;
s16 (12 0) clk;
v1 (20 0);
end;

analyze sss;
infreq 1 3000 lin
300;
set v1 ac 1.0 0.0;
print vm (21);
plot vm (21);
end;

end;
```


Capacitor Values for the SC Filter


| f_o (Hz) | Capacitor Values | |
|------------|------------------|------------------------|
| | C'_{F1} (Cu) | $C_{F1} = C_{F2}$ (Cu) |
| 697 | 4 | 11.4 |
| 852 | 2.6 | 9.3 |
| 1209 | 1.5 | 6.6 |
| 1477 | 1.1 | 5.4 |

Where: $C_2 = C_3 = C_4 = C_h = 1 \text{ Cu}$, $C_1 = 2.2 \text{ Cu}$,
 $C''_{F1} = 3 \text{ Cu}$ and $f_c = 1/T = 50 \text{ kHz}$


Specifications vs. Simulated Results for the SC Filter

| Design Specifications | | | Simulated Results | | |
|-----------------------|------------|----|-------------------|------------|-------|
| Gain (v/v) | f_o (Hz) | Q | Gain (v/v) | f_o (Hz) | Q |
| 1 | 697 | 20 | 0.998 | 699.00 | 19.92 |
| 1 | 852 | 20 | 0.999 | 857.25 | 20.02 |
| 1 | 1209 | 20 | 1.000 | 1209.00 | 19.83 |
| 1 | 1477 | 20 | 1.002 | 1479.00 | 20.11 |

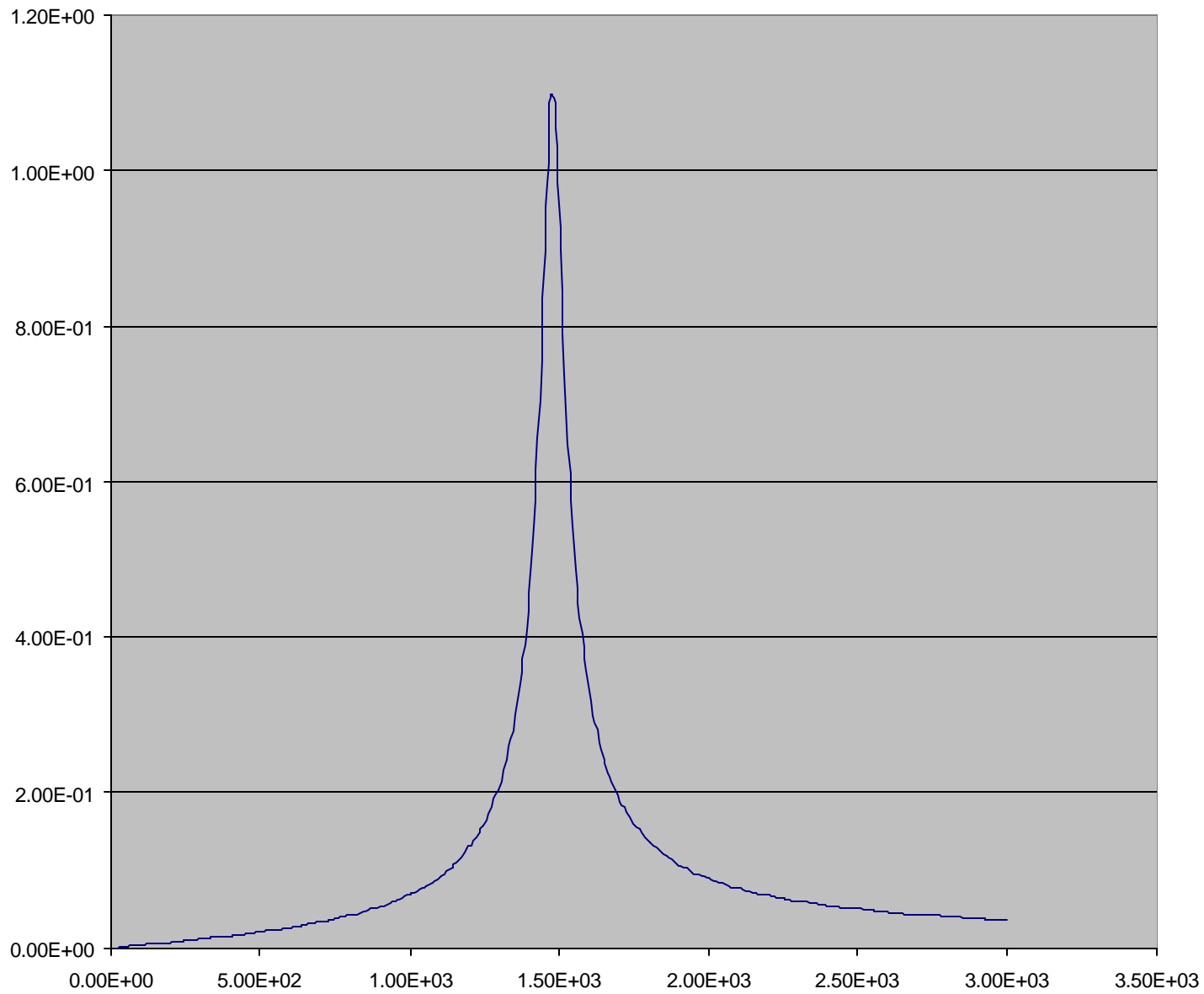


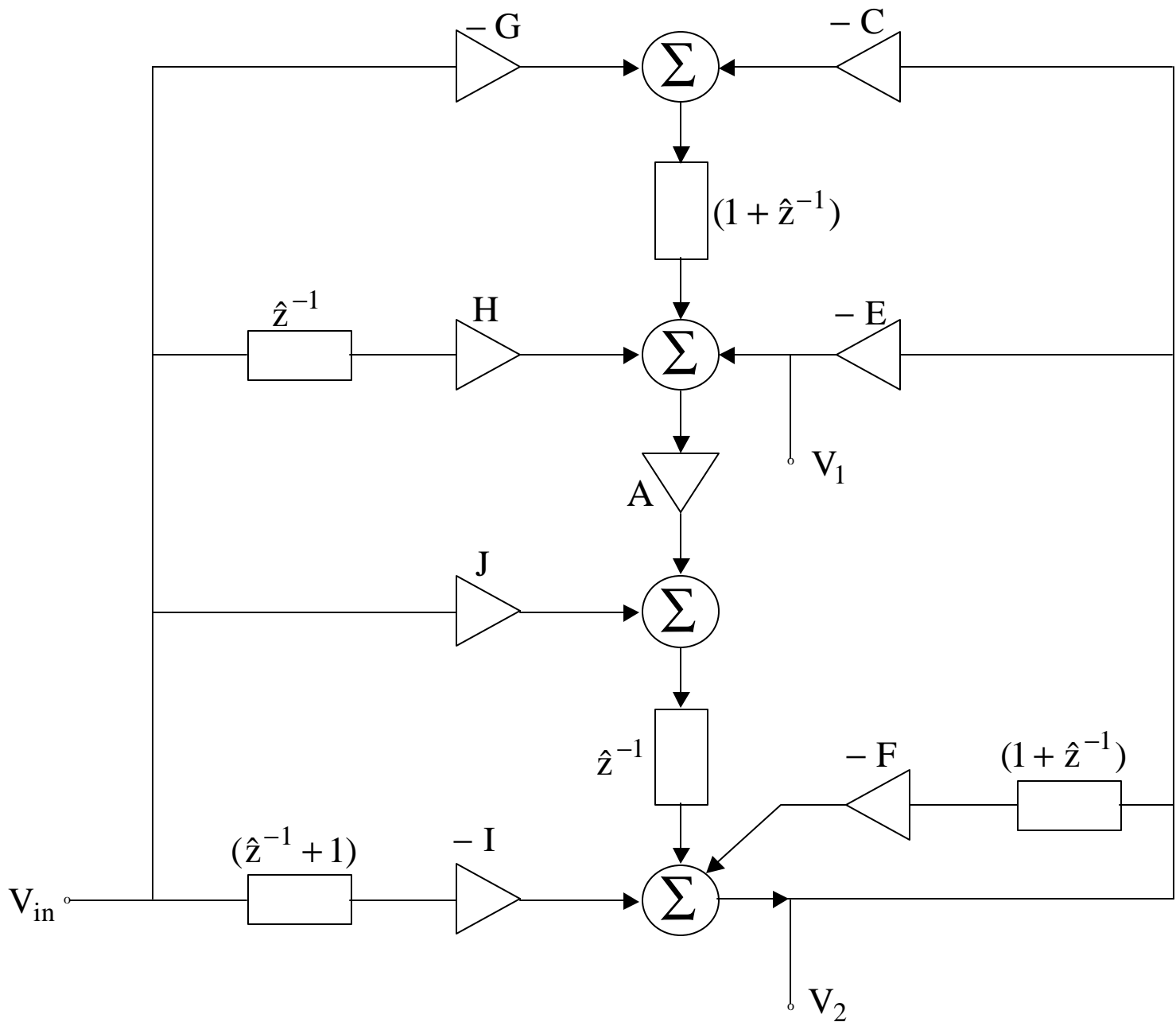

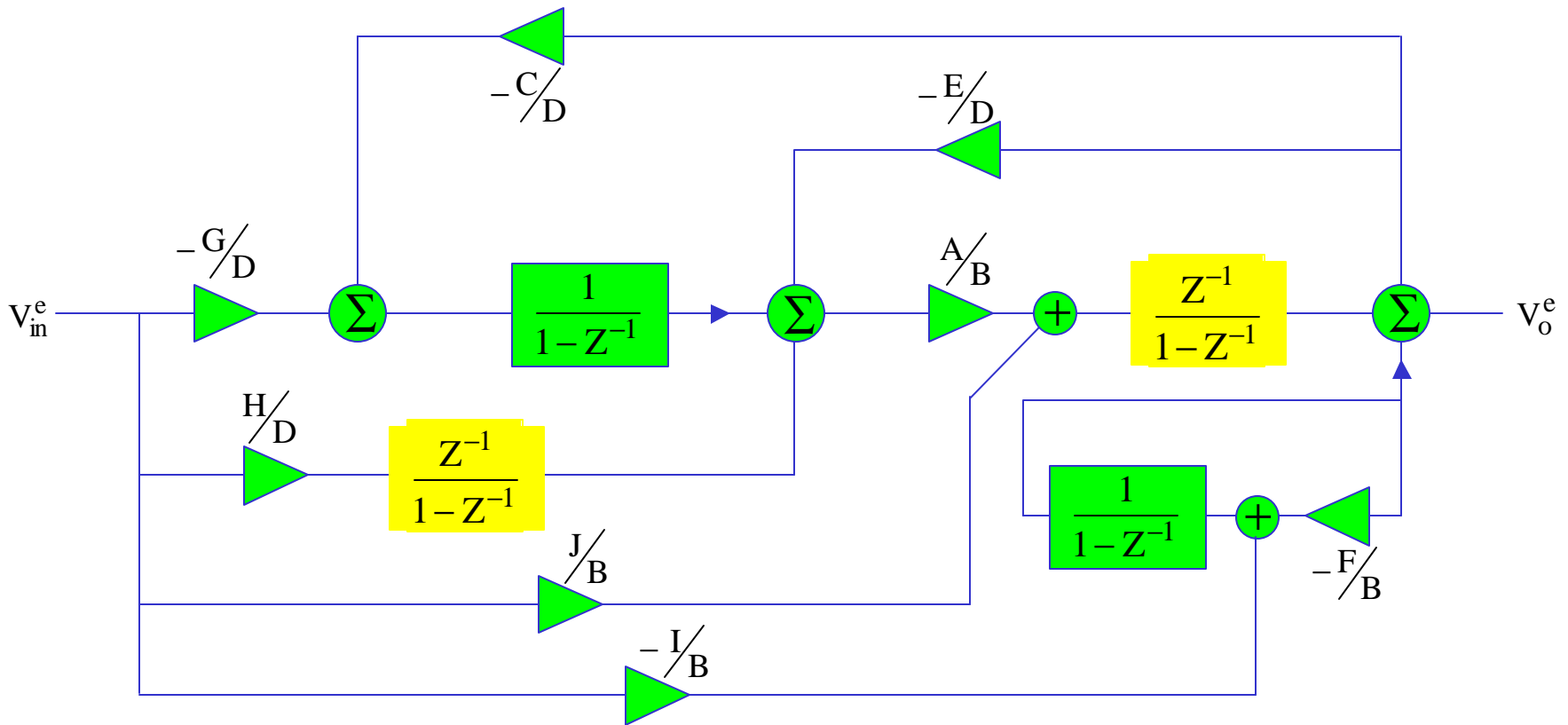
A general SC biquad flow diagram, for $B=D=1$, type 1. Note that $\hat{z}^{-1} = z^{-1}$.



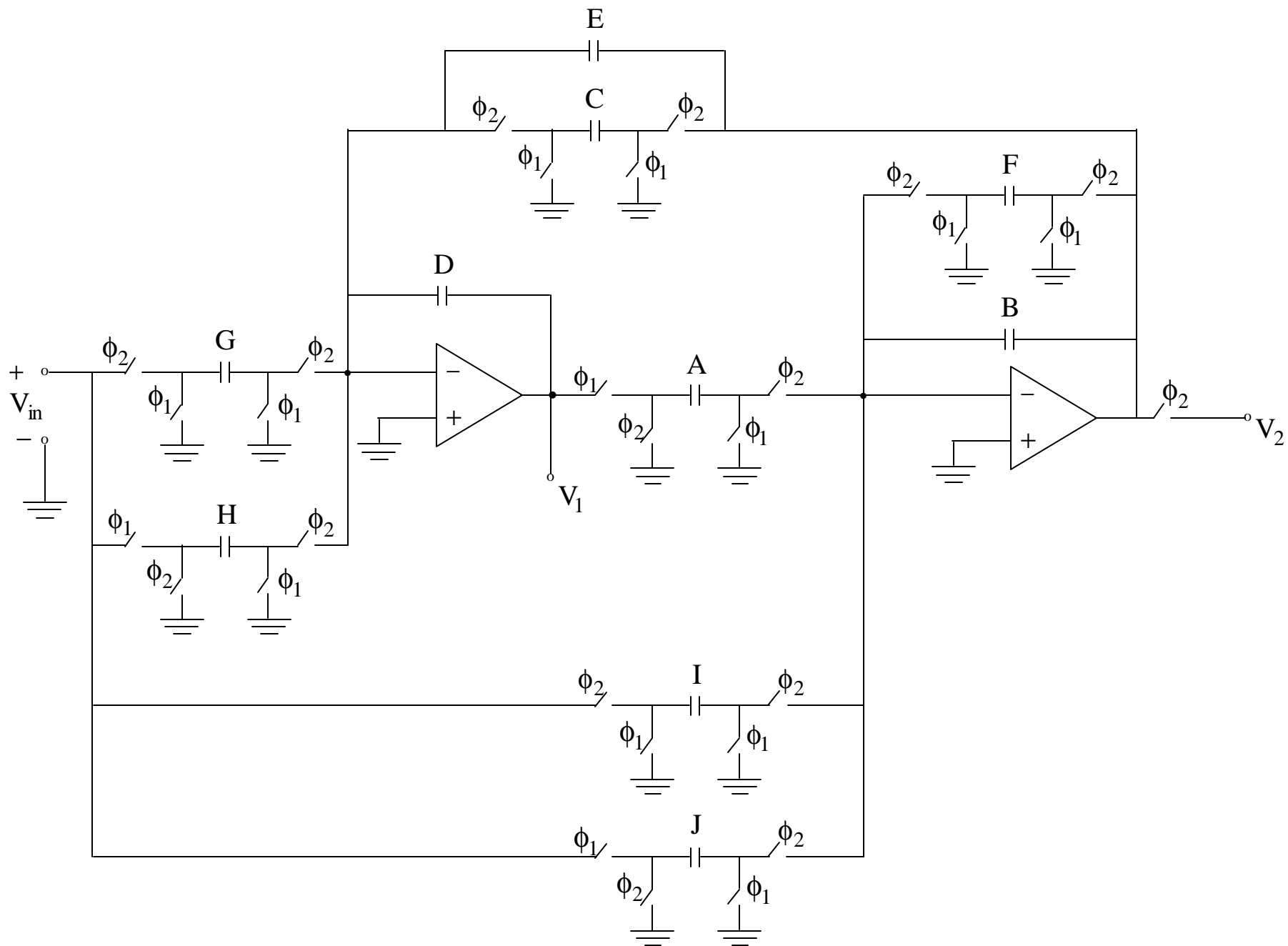An Alternative Block Diagram Representation



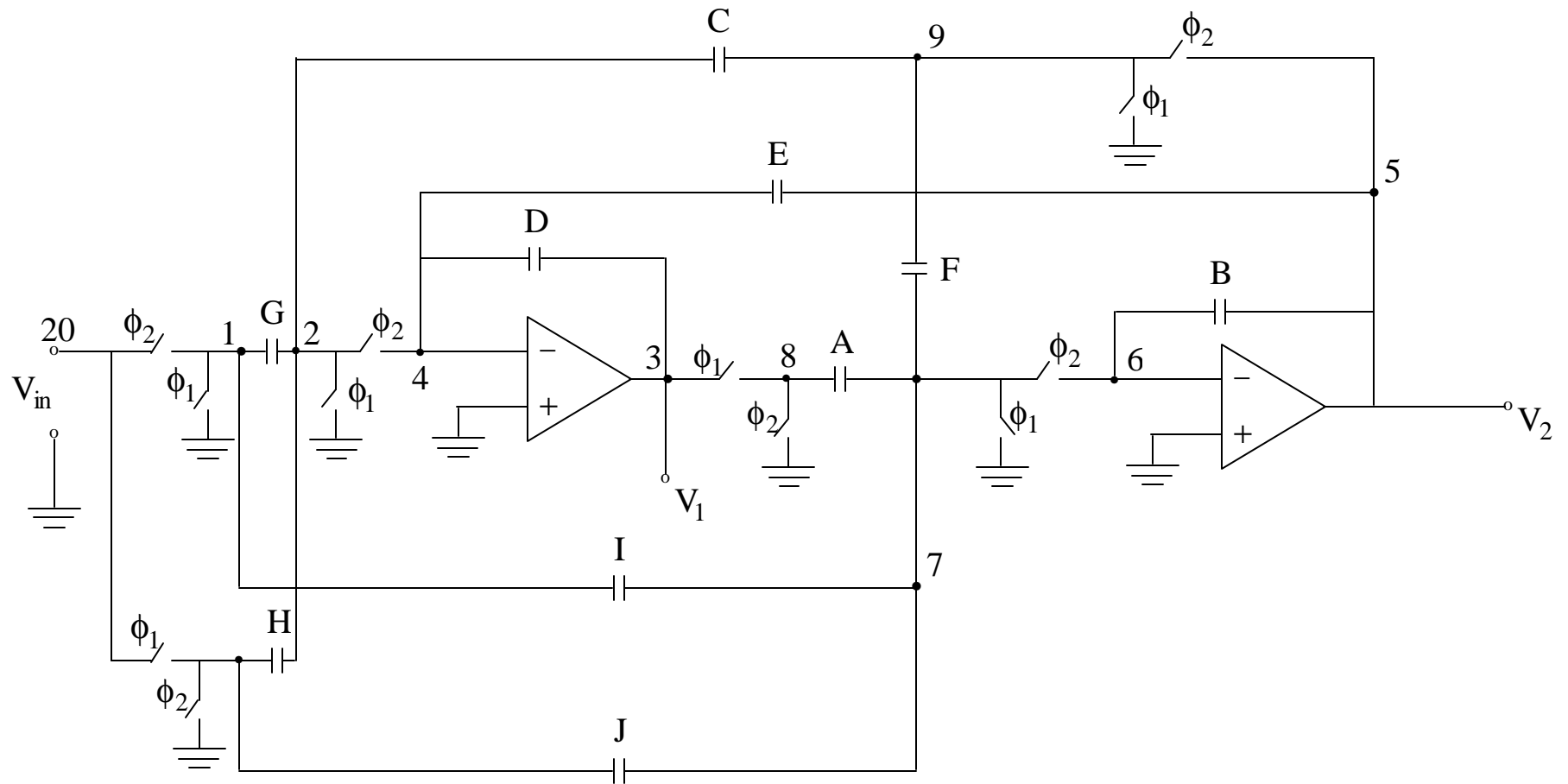SC implementation with maximum number of switches. Type E1 corresponds to $F=0$



SC implementation minimum switch configuration.

Design of 2nd-Order LP Notch Filter

Design a LP Notch Filter with $f_z=1,800$ Hz, $f_p= 1,700$ Hz, $Q_p=30$ and 0dB DC Gain.
The corresponding $H(s)$ yields:

$$H(s) = \frac{0.89195s^2 + (1.140926 \times 10^8)}{s^2 + 356.0475s + (1.140926 \times 10^8)}$$

By using the bilinear mapping

$$s = K \frac{1 - z^{-1}}{1 + z^{-1}}$$

where $K = \omega_a / \tan(\omega_d T / 2)$

For $T= 1/128$ kHz, the corresponding transfer function becomes:

$$H(z) = 0.89093 \frac{1 - 1.99220z^{-1} + z^{-2}}{1 - 1.99029z^{-1} + 0.997232z^{-2}}$$

Next we will match the coefficients of $H(z)$, for $A=1$, with the ones of a SC Biquad Topology, i.e.,

$$H_{E_2}(\hat{z}) = - \frac{I + (I + G - J)\hat{z}^{-1} + (G - H)\hat{z}^{-2}}{1 + (E + C)\hat{z}^{-1} + C\hat{z}^{-2}} \quad \text{Output taken at node } V_2$$

where $\hat{z}^{-1} = \frac{z^{-1}}{1 - z^{-1}}$; $\hat{z} = z - 1$

$$H(\hat{z}) = 0.89093 \frac{1 + 0.0078\hat{z}^{-1} + 0.0078\hat{z}^{-2}}{1 + 0.0097\hat{z}^{-1} + 0.000694\hat{z}^{-2}}$$


| CAPACITOR (PF) | E-CIRCUIT | | |
|-------------------|------------------|----------|---------|
| | DYNAMIC RANGE | | |
| | INITIAL | ADJUSTED | FINAL |
| A | 1.0000 | 0.08308 | 1.0000 |
| B | 1.0000 | 1.0000 | 12.0365 |
| C | 0.00694 | 0.00694 | 2.5035 |
| D | 1.0000 | 0.08308 | 29.9613 |
| E | 0.00277 | 0.00277 | 1.0000 |
| F | --- | --- | --- |
| G | 0.00694 | 0.00694 | 2.5035 |
| H | --- | --- | --- |
| I | --- | --- | --- |
| J | --- | --- | --- |
| K(I=J) | 0.89093 | 0.89093 | 10.7238 |
| Σ C(pF) | --- | --- | 59.7 |

SWITCAP Input file

```
timing;
period 7.8125e-06;
clock clk 1 (0 1/2);
end;

circuit;
cg (1 2) 2.5935;
ca (8 7) 1.0000;
cd (4 3) 29.9613;
cb (6 5) 12.0365;
ce (4 5) 1.00000;
cc (2 9) 2.5035;
e1 (3 0 0 4) 28000;
e2 (5 0 0 6) 28000;
s1 (20 1) #clk;
s4 (2 4) #clk;
s5 (9 5) #clk;
s9 (8 0) #clk;
s10 (7 6) #clk;
s2 (1 0) clk;
s3 (2 0) clk;
s6 (9 0) clk;
s7 (3 8) clk;
s8 (7 0) clk;
v1 (20 0);
end;
analyze sss;
infreq 1 4000 lin 300;
set v1 ac 1.0 0.0;
print vm(5);
plot vm(5);
```

Low-pass notch SC

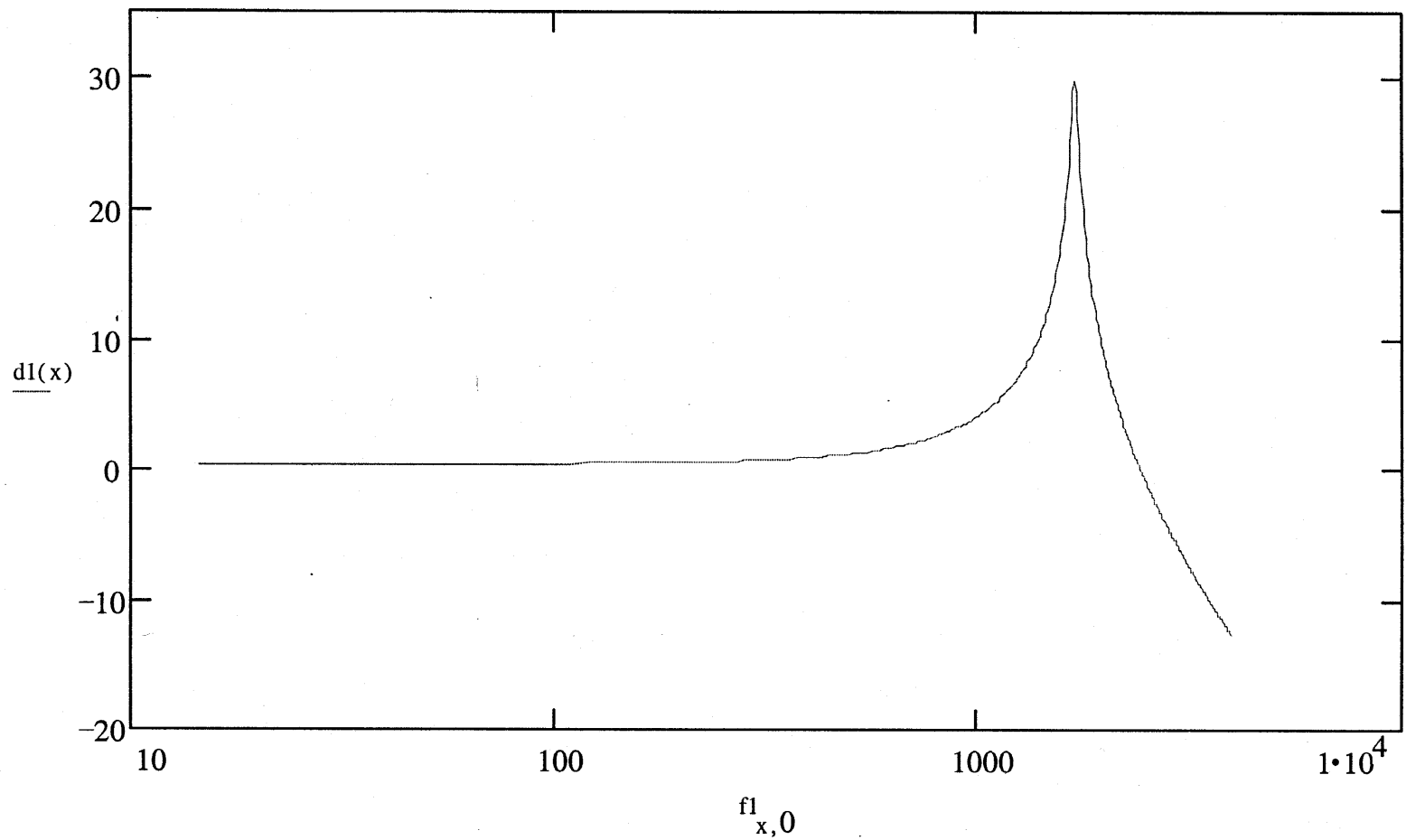


$$f_p = 1,700 \text{ Hz}, \quad f_z = 1,800 \text{ Hz}, \quad Q_p = 30, \quad \text{DC Gain} = 0 \text{ dB}$$

PRACTICAL CONSIDERATIONS FOR OP AMPS

Key op amp specifications:

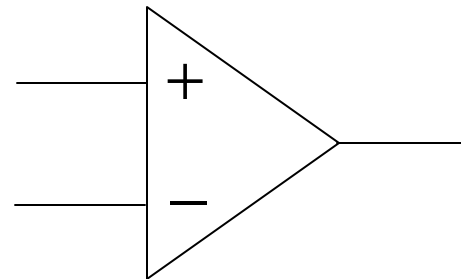- Gain, output impedance
- Speed (BW)
- Supply voltages
- Output swing
- Noise
- Power



Alternatives ?



NON-IDEAL EFFECTS OF OP AMPS

A. FINITE DC GAIN

For a two integrator biquadratic filter:

$$\omega_{oA} = \frac{A_o}{1 + A_o} \omega_o \quad Q = \frac{1}{\frac{1}{Q} + \frac{2}{A_o}} \cong \left(1 - \frac{2Q}{A_o}\right)Q$$

Therefore:

- ω_o deviations are negligible
- Q deviations can be significant

B. FINITE BANDWIDTH

- Bandwidth is very critical for high frequency applications

Consider A Biquadratic Function

* A_o Effects on w_o and Q

If $Q \uparrow$ then $A_o \uparrow$ High Q requirements imply high A_o

The actual Q_A is given by

$$Q_A = Q \left[\frac{1}{2Q + A_o} \right] \left[1 + A_o^2 + \frac{A_o}{Q} \right]^{\frac{1}{2}}$$

$$Q_A \approx \left(1 - \frac{2Q}{A_o} \right) Q$$

and the actual center frequency w_A is

$$\omega_A = \omega_O \left[\frac{1}{1 + A_o} \right] \left[A_o^2 + \frac{A_o}{Q} + 1 \right]^{\frac{1}{2}} \approx \omega_O \frac{A_o}{A_o + 1}$$

In fact in a LP function:

$$\omega_{\text{peak}} = \omega_o \left[1 - \frac{1}{2Q^2} \right]^{\frac{1}{2}}$$

and the change of magnitude of denominator $|D|$ is

$$\Delta|D| = 20 \log \frac{Q}{Q_A} \cong 20 \log(1 + 2Q / A_o)$$

Examples

$$A_o = 10^3$$

i) $Q = 1$ then

$$\omega_{\text{peak}} = 0.707 \omega_A$$

$$Q_A = 0.998$$

ii) $Q = 10$

$$\omega_{\text{peak}} = 0.997 \omega_A$$

$$Q_A = 1.00125Q = 9.8$$

iii) $Q = 15$

$$\Delta|D| \cong 0.257 \text{dB}$$

$$Q_A \cong 14.56$$

How to determine the GB of an Op Amp?

- The required GB is a function of the clock frequency and the feedback topology around the Op Amp.
- A rule of thumb to select GB requires to satisfy the following inequality:

$$a \text{ GB } T > 5$$

where T is the period of the clock frequency, **a** is the capacitor ratio between the sum of all the feedback capacitors divided by the sum of all the capacitors connected to the input terminal of the Op Amp

Architectures Styles and Pros and Cons

A. SINGLE-ENDED CONFIGURATION

- High gain
- CMRR = 0
- Nested compensation trades BW for stability

B. FULLY DIFFERENTIAL CONFIGURATION

- High gain
- Good CMRR
- Rail-to-rail output swing
- Higher bandwidth (less compensation)
- Requires an additional CMFB and dynamic reset

C. FULLY BALANCED FULLY DIFFERENTIAL

- Use single ended amplifiers
- Excellent CMRR

References

- E. Sánchez-Sinencio, J. Silva-Martínez, *The Circuits and Filters Handbook: Switched Capacitor Filters*, CRC Press Inc., section XV, pp. 2491-2520, 1995.
- A. H. Reyes, "A Wireless Volume Control Receiver for Hearing Aids" Master of Science", Texas A&M University, Electrical Engineering. August 1993
- E. Sánchez-Sinencio, R.L. Geiger and J. Silva-Martínez, "Tradeoffs between Passive Sensitivity, Output Voltage Swing and Total Capacitance in Biquadratic SC Filters," *IEEE Trans. Circuits and Systems*, Vol. CAS-31, No. 11, pp. 984-987, November 1984.
- E. Sanchez-Sinencio, J. Silva-Martínez, and R.L. Geiger, "Biquadratic SC Filters with Small GB Effects," *IEEE Trans. Circuits and Systems*, Vol. CAS-31, No. 10, pp.876-884, October 1984
- R. Castello, F. Montecchi, F. Rezzi and A. Baschiroto, "Low-Voltage Analog Filters," *IEEE Trans. on Circuits and Systems I*, Vol. 42, No. 11, pp. 827-840, November 1995.
- A. Abo, "Low Voltage, High-Speed, High-Precision Switched-capacitor Circuits," *Qualifying Exam*, University Of California at Berkeley, May 1996.
- D. A. Johns and K. Martin, "*Analog Integrated Circuit Design*" New York, John Wiley & Sons 1997