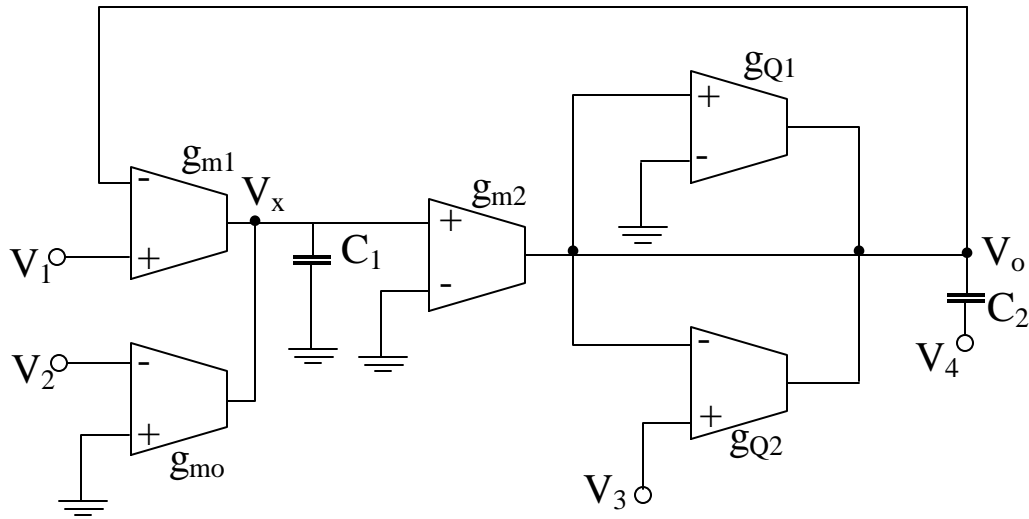



**EXAM #2**

This is a closed book exam. Only one page summary is allowed. This exam is worth 15% of your total grade.


Prob. 1. (3 p) Assume ideal OTAs and obtain the simplified expression of  $V_o$  as a function of  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$ . Also indicate the input values yielding a notch filter.



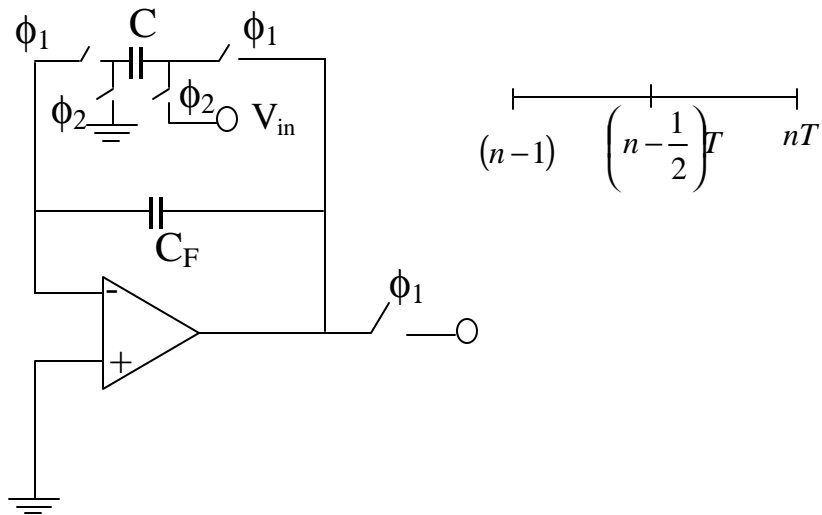
Prob. 2 (4 p) Obtain the transfer function of the SC circuit shown below. You could use charge conservation and then the Z-transform, or you can use block diagrams and Mason Rule.



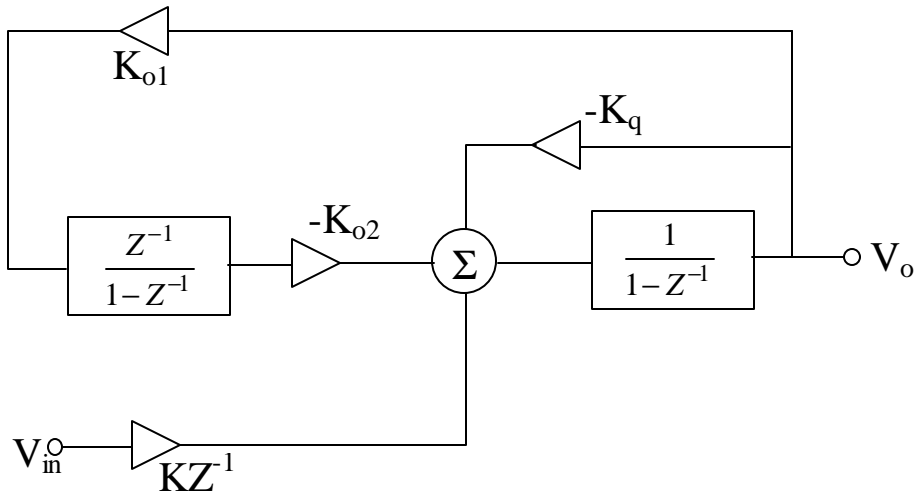Prob. 3 (4p) Given the block diagram obtain the corresponding SC Filter implementation. Also obtain the transfer function.



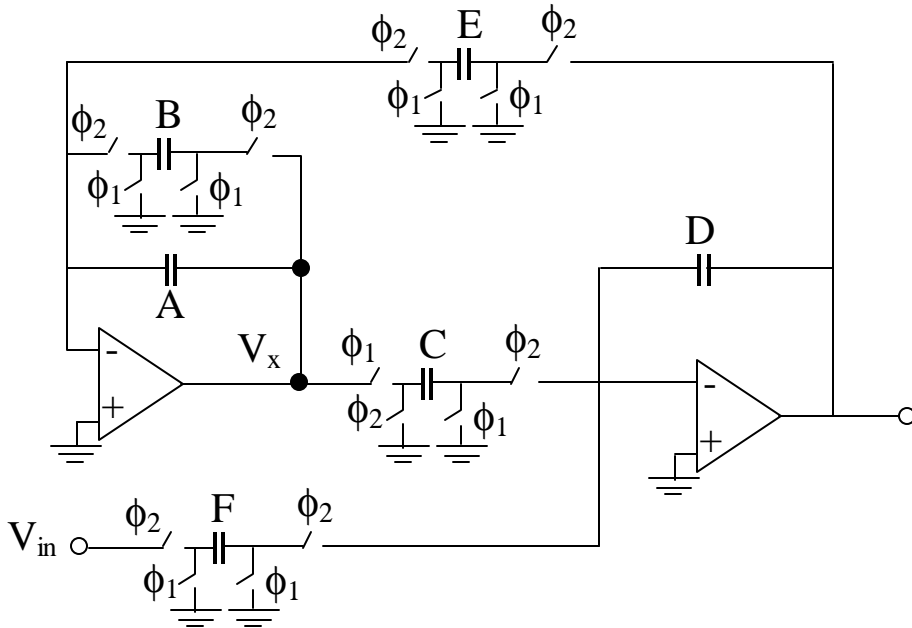Prob. 4 (4p) Assume that the SC filter has been designed and its capacitor values are known (see below). However, the value of  $V_x$  must be reduced by 0.75. Modify  $V_x$  to be reduced by 0.75 by changing the suitable capacitors. Finally normalize the capacitor values such that the smallest capacitor is 1 per group.



Capacitor (p F)	Initial	Dynamic Range Adjusted	Final
A	1.0		
B	8		
C	.66		
D	1.0		
E	0.0333		
F	2.0		
Total Capac.			

**Extra Credit (2 p)** No partial credit

A LP first-order can be expressed as

$$H(Z) = \frac{-(C_1/C)Z}{Z(1 + C_2/C) - 1}$$

We want to approximately determine the 3dB cut-off frequency. By using a mapping from the  $Z$  to  $S$ - plane *under high-sampling rate* conditions, determine an expression for the cut-off frequency.