
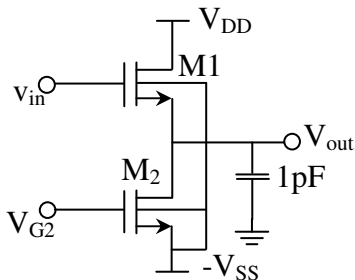


HOMWORK ASSIGNMENT #1

- Prob. 1. Use any size technology and generate the equivalent plot (see page 21 Lect. #1) of various parameters versus the inversion level. i.e. f_T , power consumption, (W/L) vs i_f . Also in another graph plot f_{max} vs i_f for at least two different W/L families, i.e. $(W/L) = (100\mu/0.6\mu, 100\mu/3\mu)$. Make comments.
- Prob. 2. Extract the parameters of transistor PMOS and NMOS for the ACM model, that is one equation all regions. See Ref. 6 on Lect. #1. Consider the $0.5\mu\text{m}$ CMOS technology and $i_f = 8$. Discuss how the parameters are extracted. Provide a table summarizing results of the extracted parameters. Discuss results.
- Prob. 3 Design two low impedance buffer using the circuits shown below. Use $i_f = 8$ and $0.5\mu\text{m}$ CMOS technology, $V_{DD} = -V_{SS} = 1.65\text{V}$. Provide design procedures.

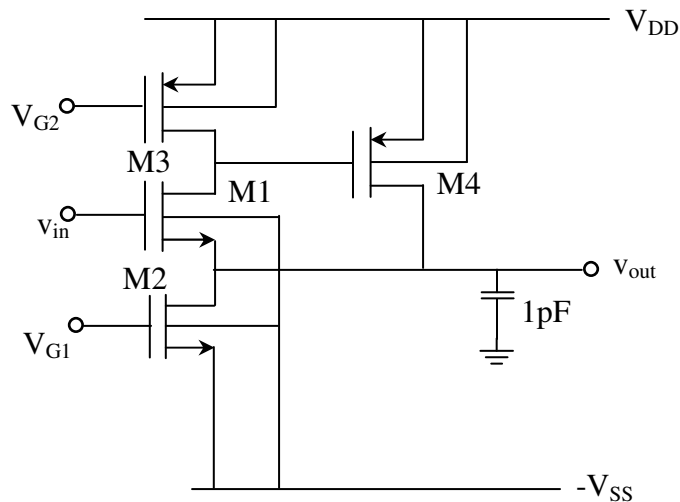

Buffer 1



Buffer 2

Include a summarizing table with at least, Max v_{out} , Max I_{out} , voltage gain, output impedance, f_{3dB} , $PSRR^+$, $PSRR^-$, settling time 0.1%, power consumption, C_{in} , input referred noise, CMRR and CMR. Discuss how they compare.