
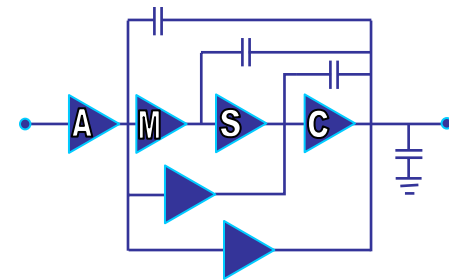


# MACROMODELS OF AMPLIFIERS

- Why do we need a macromodel?
- What properties of the real model can be included in the macromodel?
- What are the trade-offs of simplicity versus completeness?  
i.e., how many poles and zeros should be included in the linear model?

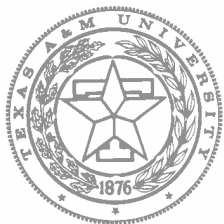

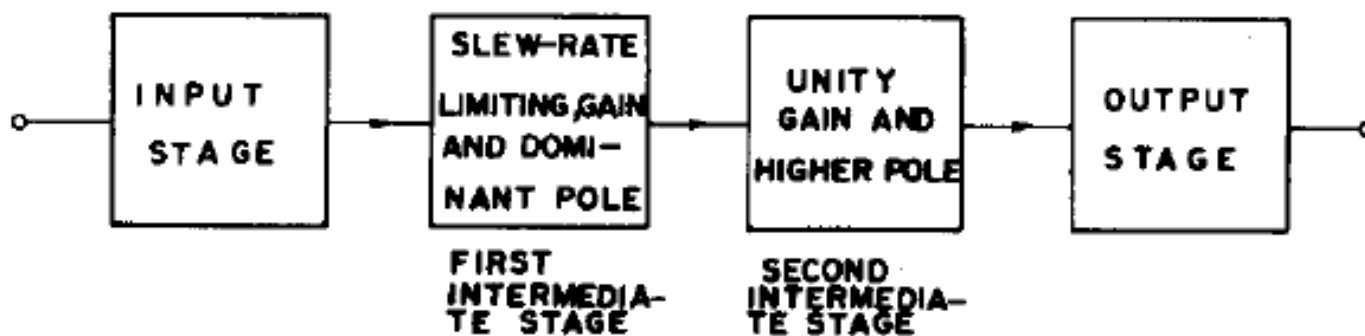


Fig. 1. Block diagram of the OA macromodel.

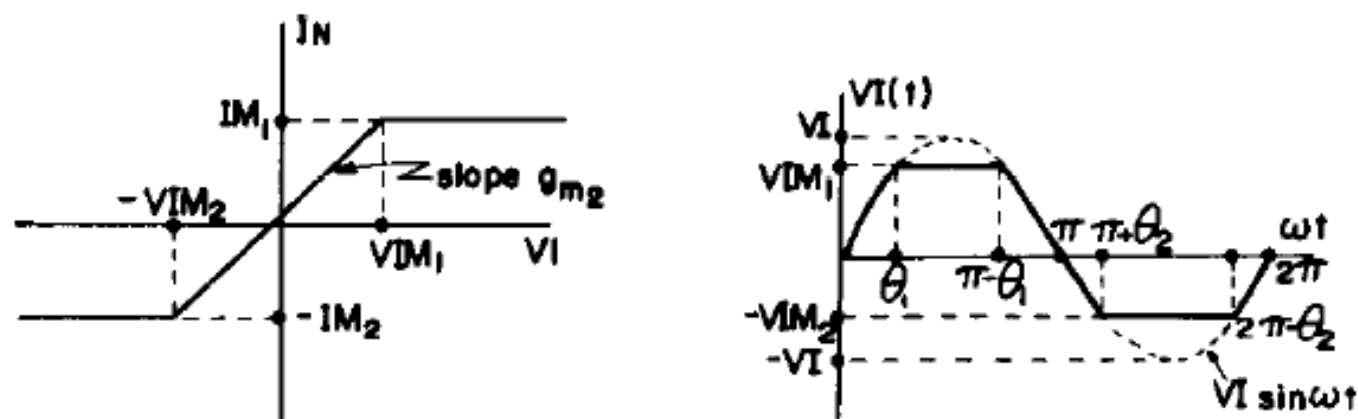


Fig. 2. Transfer characteristics including saturation characteristics of the VCCS,  $I_N$  of Fig. 3.

$$I_N(\omega t) = \begin{cases} IM, & \text{for } (\theta, \pi - \theta) \text{ and } (\pi + \theta, 2\pi - \theta) \\ g_{m2} VI \sin(\omega t), & \text{otherwise.} \end{cases}$$

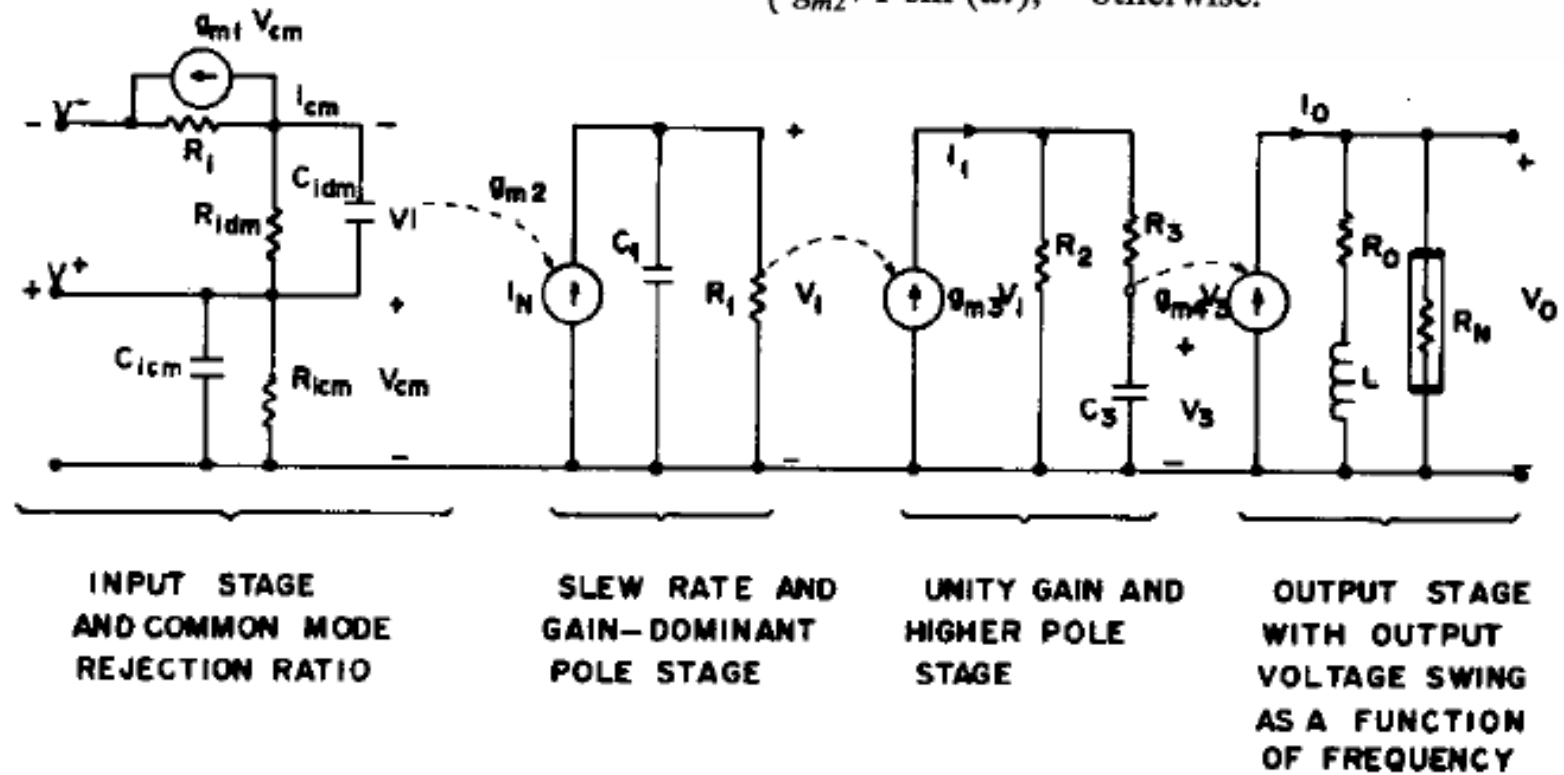


Fig. 3. Macromodel equivalent circuit.

First stage.-

$$I_{cm} = g_{m1} V_{cm} \quad (1)$$

$$g_{m1} = \frac{1}{CMRR(\omega) \cdot R_i} \quad (2)$$

$$CMRR(\omega) = \frac{CMRR_o}{\left(1 + j \frac{f}{f_{CMRR}}\right)} \quad (3)$$

$$C_{icm} = \frac{1}{2\pi R_{icm} f_{CMRR}} \quad (4)$$

$$\frac{V_{cm}}{CMRR} = I_{cm} R_i \quad (5)$$

$$R_i \ll R_{idm}$$

$$VI = \frac{V^+ - V^- + g_{m1} V^+ R_i}{R_i + Z_{idm}} Z_{idm} \quad (6)$$

Second Stage.-

$$g_{m2} = \frac{I_N}{VI} \quad (7)$$

$$I_N = \begin{cases} g_{m2} VI, & \text{for } |VI| \leq VIM \\ IM, & \text{for } |VI| > VIM. \end{cases} \quad (8)$$

$$I_{o,swing} = IM = S_r C_1 \quad (9)$$

$$C_1 = \frac{IM}{S}. \quad (9a)$$

$$R_1 = \frac{1}{\omega_1 C_1}. \quad (10)$$

$$g_{m2} = \frac{A_{dm}}{R_1}. \quad (11)$$

$$VIM = \frac{S_r}{A_{dm} \omega_1} = \frac{S_r C_1}{g_{m2}}. \quad (12)$$

$$I_{Ni} = \frac{1}{2\pi} \int_0^{2\pi} I_N(\omega t) \sin(n\omega t) d(\omega t),$$

$$i, n = 0, 1, 2, \dots \quad (13)$$

$$I_{Ni} = g_{m2} VI \cdot N_i \left( \frac{VIM}{VI} \right), \quad i = 1, 3, 5, \dots \quad (14)$$

$$VI^i = VI \cdot N_i \left( \frac{VIM}{VI} \right), \quad i = 1, 3, 5, \dots \quad (15)$$

$$V_{out} = A_{dm1}(VI' \sin \omega t) + A_{dm3}(VI''' \sin 3\omega t) + A_{dm5}(VI^v \sin 5\omega t) + \dots \quad (16)$$

$$g_{m2}^{non} = g_{m2} \left[ N_1 \left( \frac{VIM}{VI} \right) + N_3 \left( \frac{VIM}{VI} \right) + N_5 \left( \frac{VIM}{VI} \right) + \dots \right] \quad (17)$$


$$C_3 = \frac{1}{\omega_2 R_3} \quad (20)$$

$$g_{m3} = \frac{1}{R_2}. \quad (21)$$

$$L = \frac{R_o}{\omega_n}. \quad (22)$$

$$g_{m4} = \frac{1}{R_o + j\omega L}. \quad (23)$$

$$R_N = \begin{cases} \infty, & \text{if } |V_{out}| \leq \max |V_{o, swing}| \\ 0, & \text{if } |V_{out}| > \max |V_{o, swing}| \end{cases}$$

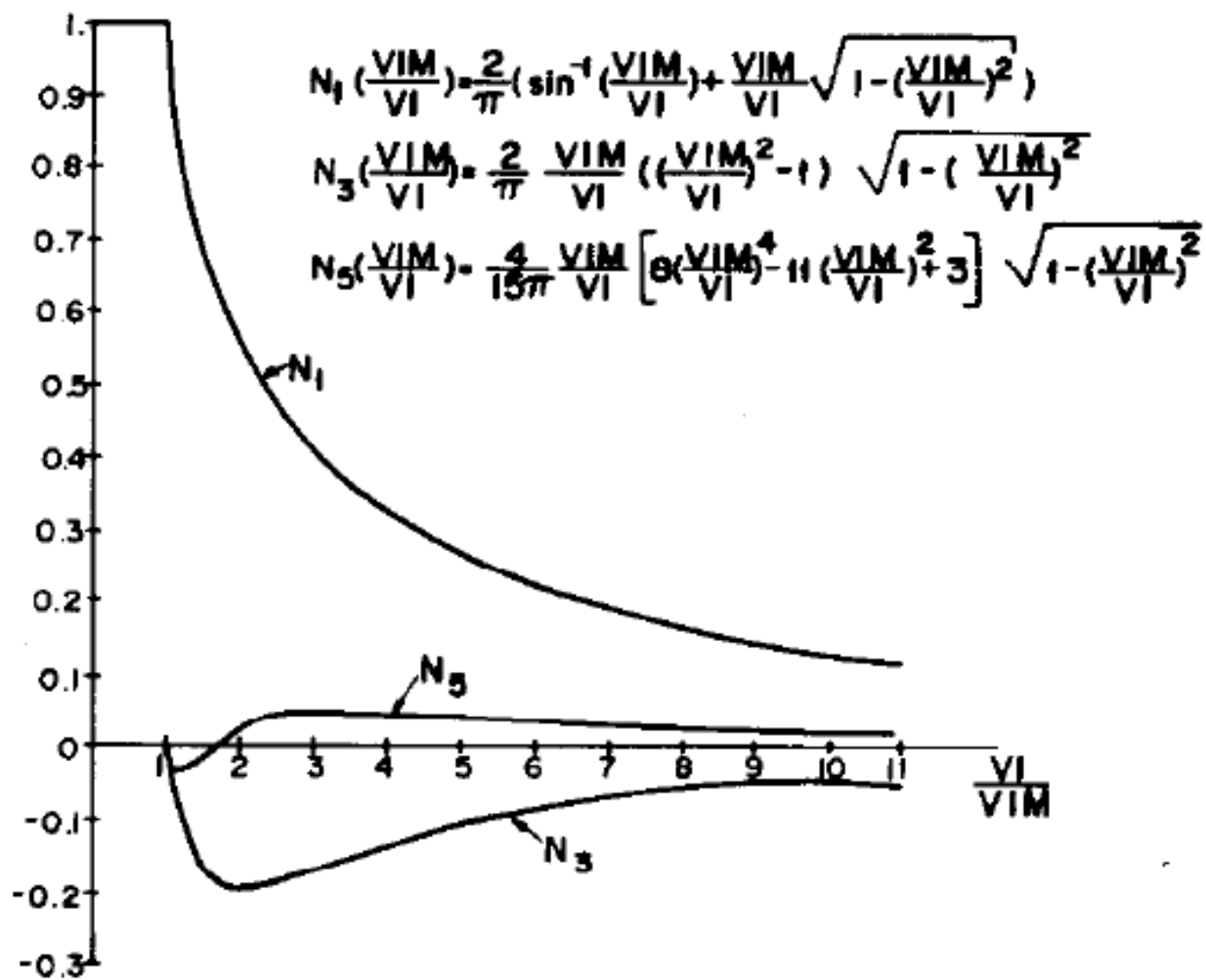

Nonlinear characteristics of  $N_1$ ,  $N_3$ ,  $N_5$  versus  $|VI/VIM|$  for the symmetric case.

$$VI^i = VI \cdot N_i \left( \frac{VIM}{VI} \right), \quad i = 1, 3, 5, \dots \quad (15)$$

Therefore, the output voltage of this second stage becomes

$$V_{\text{out}} = A_{dm1}(VI' \sin \omega t) + A_{dm3}(VI''' \sin 3\omega t) \\ + A_{dm5}(VI^v \sin 5\omega t) + \dots \quad (16)$$

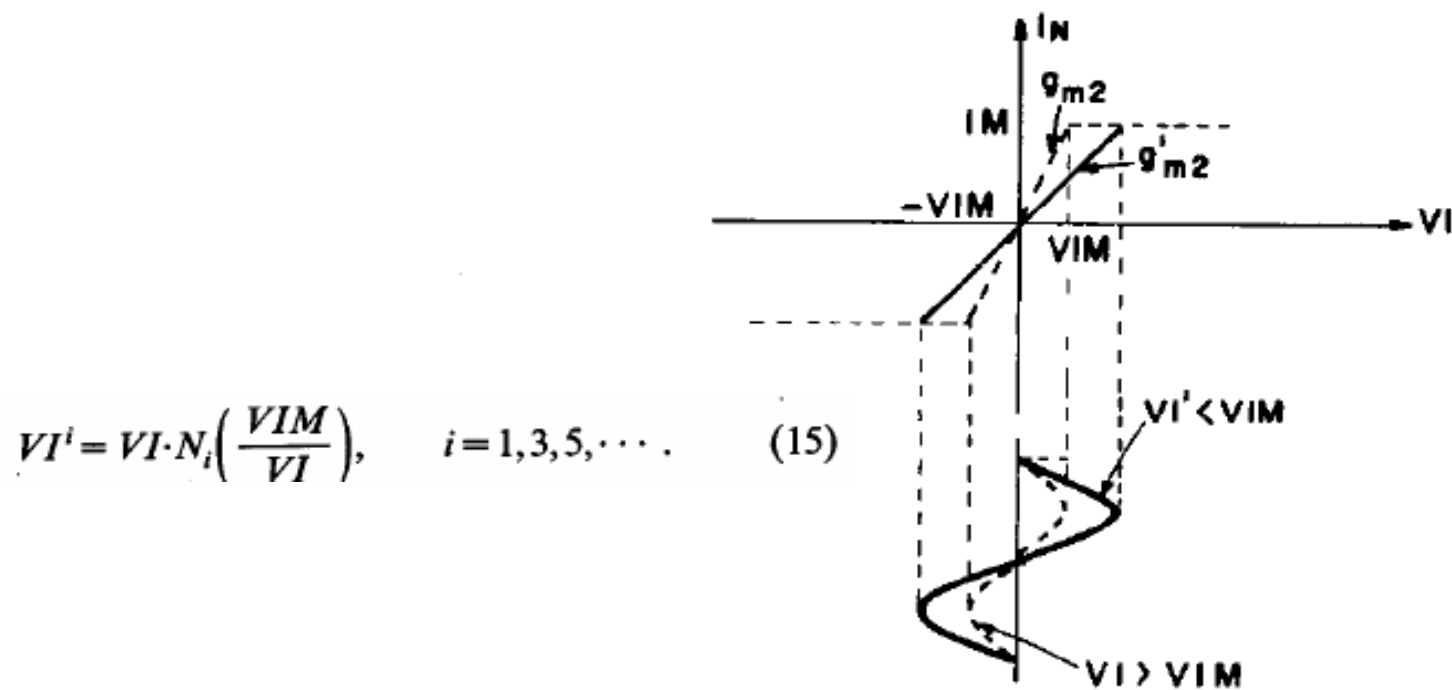


Fig. 5. Saturation characteristics of  $I_N$  when an OA is overdriven by a large input signal.

$$g_{m_2}^{\text{non}} = g_{m_2} \left[ N_1 \left( \frac{V_{IM}}{V_I} \right) + N_3 \left( \frac{V_{IM}}{V_I} \right) + N_5 \left( \frac{V_{IM}}{V_I} \right) + \dots \right] \quad (17)$$

and so

$$I_N = g_{m_2}^{\text{non}} \cdot V_I. \quad (18)$$

Stage 3

$$C_3 = \frac{1}{\omega_2 R_3} \quad (20)$$

$$g_{m_3} = \frac{1}{R_2} \quad (21)$$

$$L = \frac{R_o}{\omega_o} \quad (22)$$

$$g_{m_4} = \frac{1}{R_o + j\omega L} \quad (23)$$

$$R_N = \begin{cases} \infty, & \text{if } |V_{\text{out}}| \leq \max |V_{o, \text{swing}}| \\ 0, & \text{if } |V_{\text{out}}| > \max |V_{o, \text{swing}}| \end{cases}$$

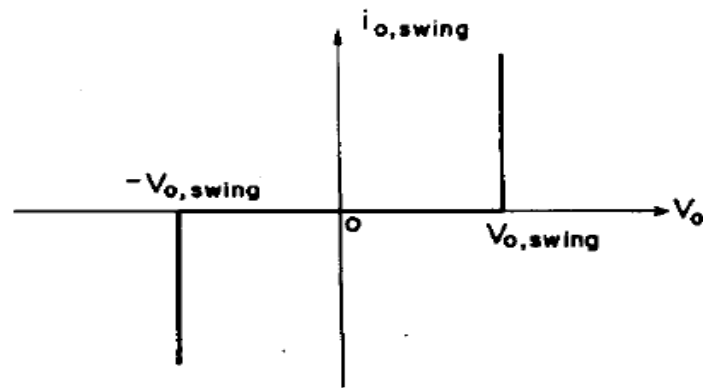


Fig. 6.  $V-I$  characteristic of the output nonlinear resistor  $R_N$ .

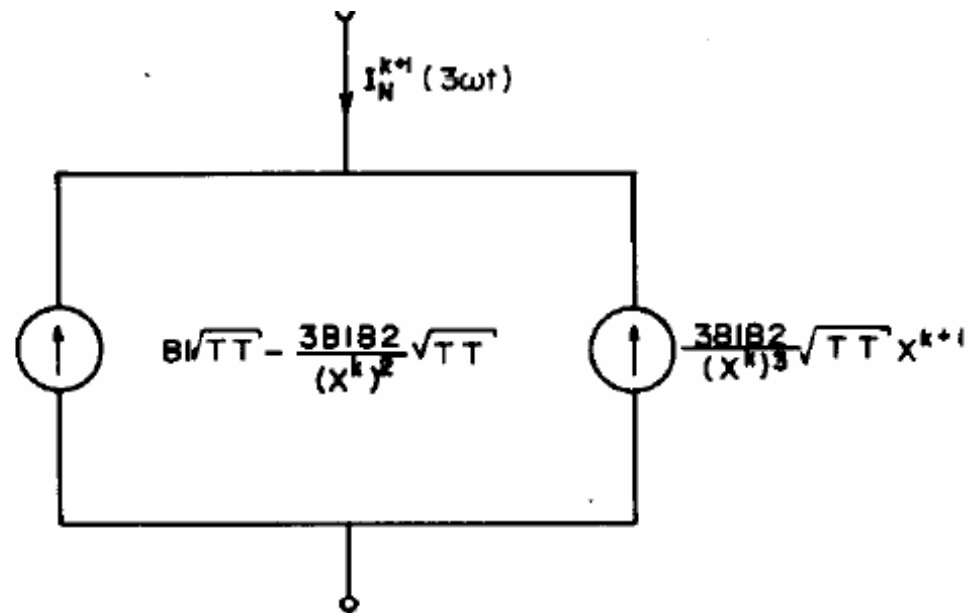


Fig. 7. Companion model of the third-harmonic component of  $I_N(3\omega t)$ .  
 $k$  is the iteration counter.

**TABLE II**  
**MODEL COMPONENTS AND AMPLIFIER PARAMETERS**

**Amplifier Parameters**

$A_{dm} = 2 \times 10^5$	$R_{idm} = 2 \times 10^6 \Omega$	$\omega_o = 2\pi \times 150 \times 10^3 \frac{\text{rad}}{\text{s}}$
$\omega_1 = 2\pi \times 5 \frac{\text{rad}}{\text{s}}$	$R_{icm} = 2 \times 10^9 \Omega$	$R_o = 75 \Omega$
$\omega_2 = 2\pi \times 2 \times 10^6 \frac{\text{rad}}{\text{s}}$	$C_{idm} = 1.4 \text{ pF}$	$S_V = 0.5 \text{ V}/\mu\text{s}$
$f_{\text{CHRR}} = 300 \text{ Hz}$	$\text{CMHRR}_o = 31622.77$	$\text{TM} = 133.3 \times 10^{-3} \text{ A}$
		$V_{\text{omax}} = \pm 10 \text{ V}$

**Model Components**

$R_1 = 10 \Omega$	$g_{m2} = 1.67551 \text{ mhos}$	$L = 79.5 \mu\text{H}$
$C_{icm} = 0.265 \text{ pF}$	$R_2 = 10 \Omega$	$V_{IM} = 79.5 \text{ mV}$
$R_1 = .11936 \text{ M}\Omega$	$R_3 = 1 \text{ k}\Omega$	$g_{m1} = 3.162 \times 10^{-6} \text{ mhos}$
$C_1 = 0.266 \mu\text{F}$	$C_3 = 79.6 \text{ pF}$	$g_{m3} = 0.1 \text{ mhos}$
	$g_{m4}$ given by Eqn. (23)	

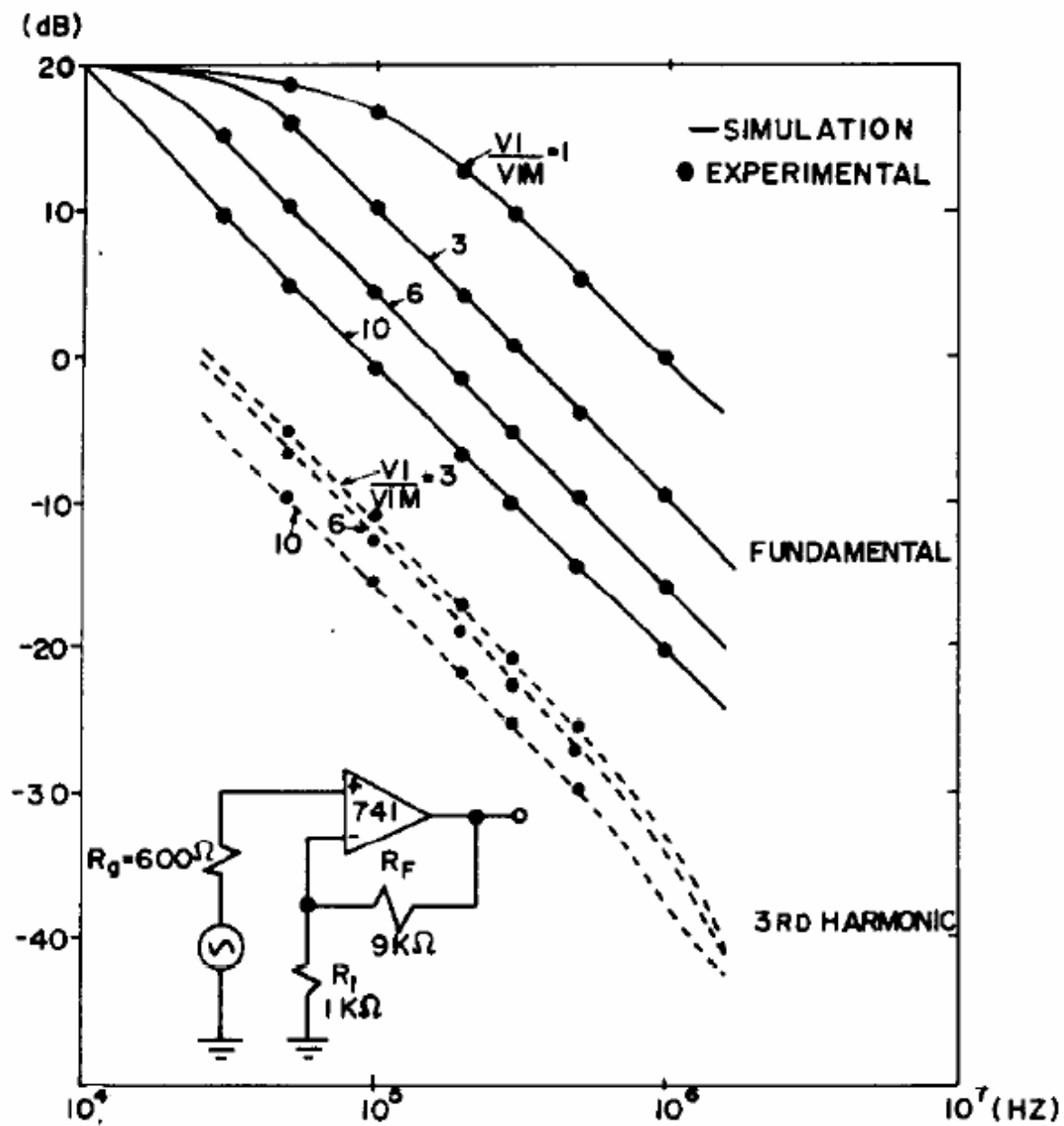


Fig. 8. Noninverting configuration. Simulation and experimental results.

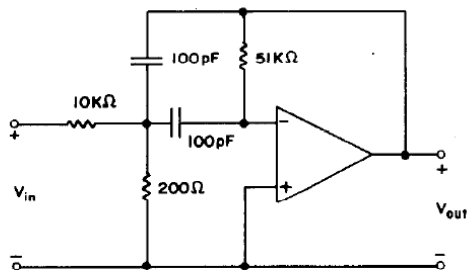


Fig. 9. RC-active bandpass filter.

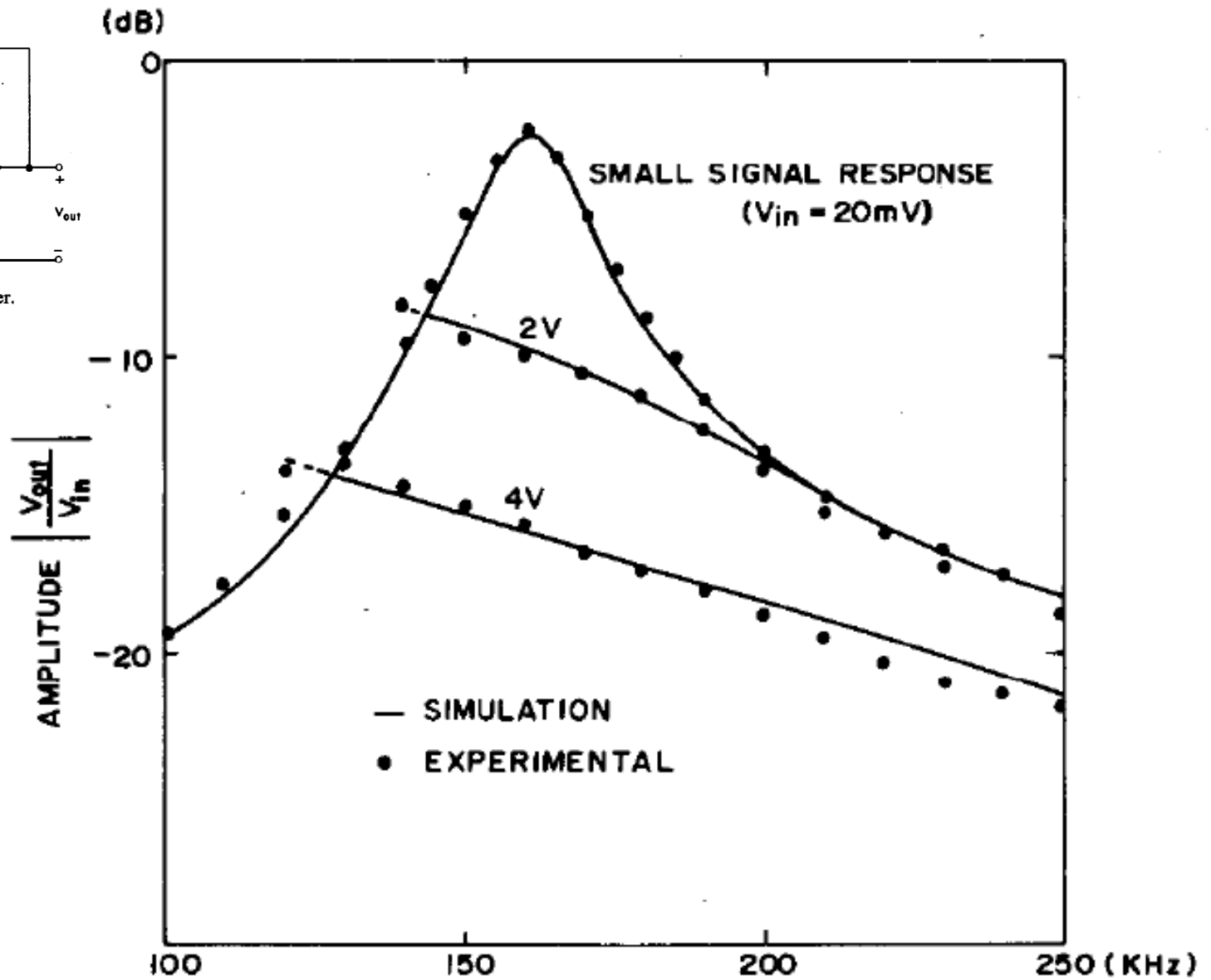


Fig. 10. Simulation and experimental results of the filter of Fig. 9.

RAO AND SRINIVASAN FILTER

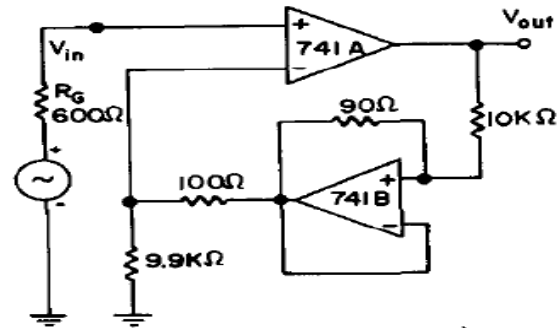


Fig. 12. A bandpass *R*-active filter.

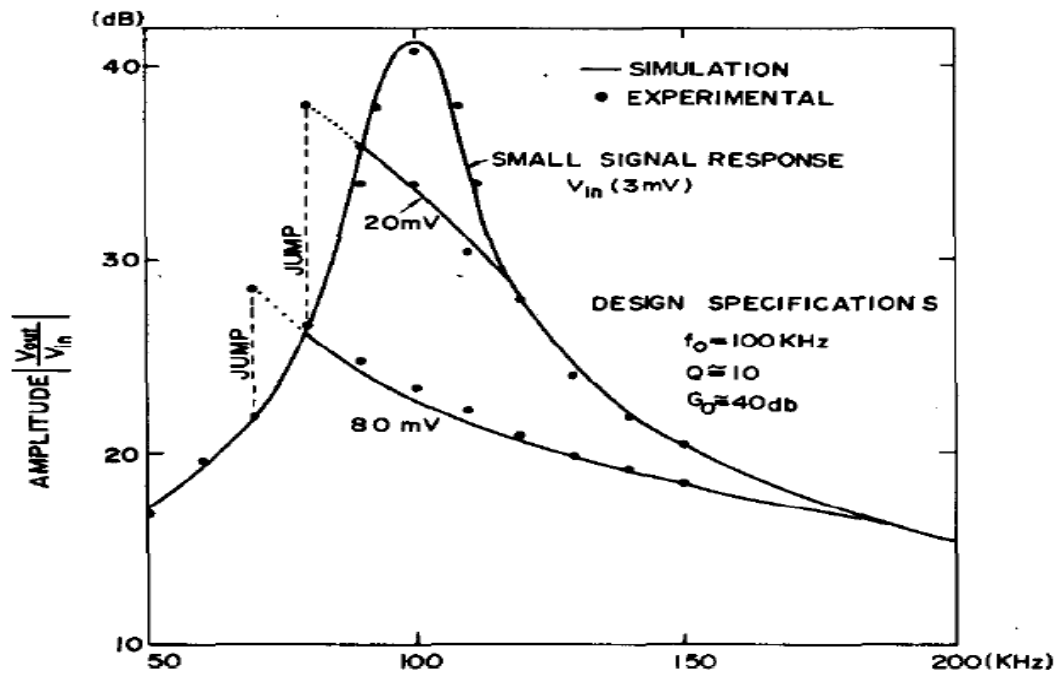


Fig. 13. Simulation and experimental results for different input signal amplitudes with the circuit of Fig. 12.