


**ELEN 689-608 (ESS)**  
**Spring 2000**  
**March 21, 2000**

**Name** \_\_\_\_\_
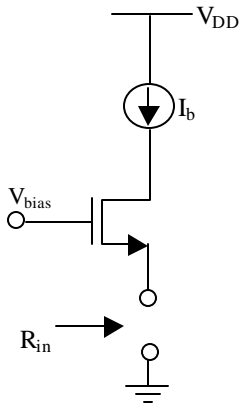
### **EXAM #1**


This exam is closed book, no notes, nor book can be used except one information page is allowed. This exam is worth 20% of your final grade.

Prob. 1 (a) (2p) Determine the input impedance of the circuit shown below for two cases, (i)  $I_b$  is an ideal current source, and (ii)  $I_b$  is substituted by a PMOS (M2) transistor with  $g_{ds2} = g_{ds1}$  (of transistor M1).






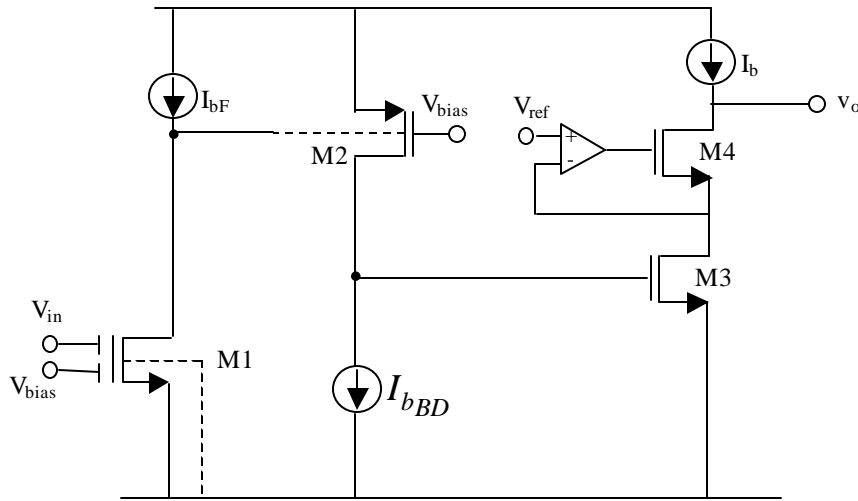Prob. 2 (3p) Obtain the approximated expression of the small signal voltage gain of the circuit show below. Assume the Op Amp is ideal of finite gain  $A_o$ .




Hint – Identify the effective transconductance and output impedance of each stage.

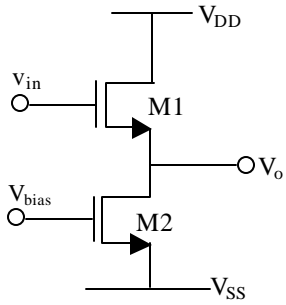
Prob. 3 (4p) (i) Determine the input referred thermal noise spectral. (ii) Indicate how to minimize the input referred thermal noise. Which  $g_{m1}$  or  $g_{m2}$  must be larger to minimize noise?



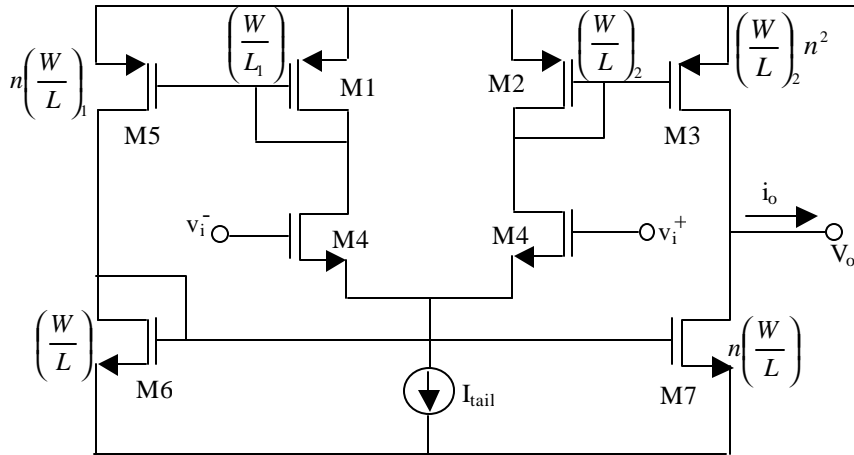Prob. 4 (4p) (a) Determine the (small signal) differential transconductance gain. (b) Also, obtain the output noise spectral density due to only M6 and M7. What is the CMRR(0) for an ideal  $I_{\text{tail}}$ . (c) Obtain the expressions for the dominant time constants of the OTA.




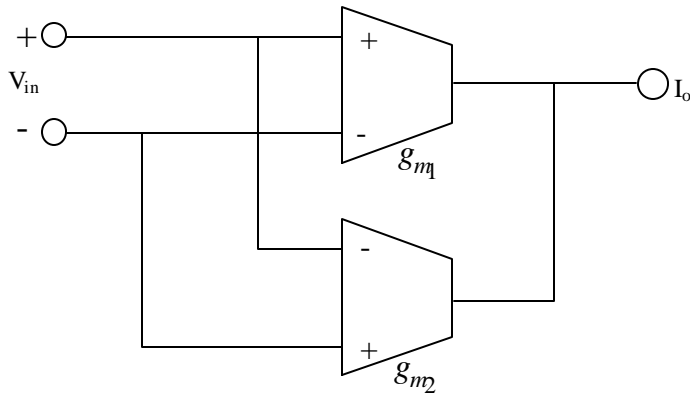Prob. 5 (3p) Assuming a one dominant pole for each OTA i.e.  $g_{m_i} = g_{m_{oi}} / (1 + S/\omega p_i)$ ,  $i = 1, 2$  obtain the effective  $G_m$  of the two OTA's combination. Is there any use of this composite OTA?



Extra Credit (2p) No partial credit.

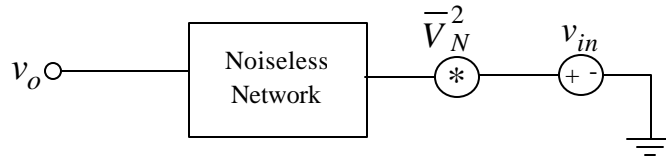For the system shown below, assume a dominant pole. Obtain the total input referred noise.



$$f_{3dB} = 0.636535 \text{ MHz} \quad \text{and} \quad \overline{V_N} = \frac{10^{-5}}{\sqrt{2}} \text{ V} / \sqrt{\text{Hz}}$$