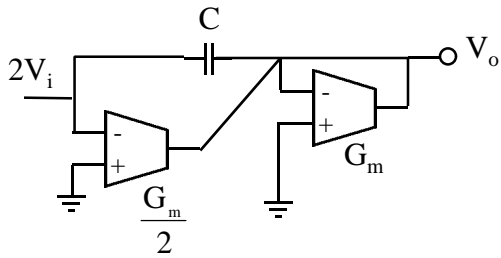


Quiz #2

Obtain the transfer function $\frac{V_o(s)}{V_i(s)}$ of the circuit shown below:



Identify the type of filter